



NPTEL ONLINE CERTIFICATION COURSES

DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING

Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR

Module 04: Modeling Techniques and Mode Validation using MATLAB


Lecture 35: Validation of Discrete-Time Large-Signal Models using MATLAB – Part I





CONCEPTS COVERED

- Recall of digital control architectures and MATLAB models
- Steps for simulation using MATLAB detailed switch models and discrete-time large-signal models
- MATLAB codes and step-by-step methods for model validation
- Validation case studies using a Buck Converter


Overall Plan for MATLAB based Validation

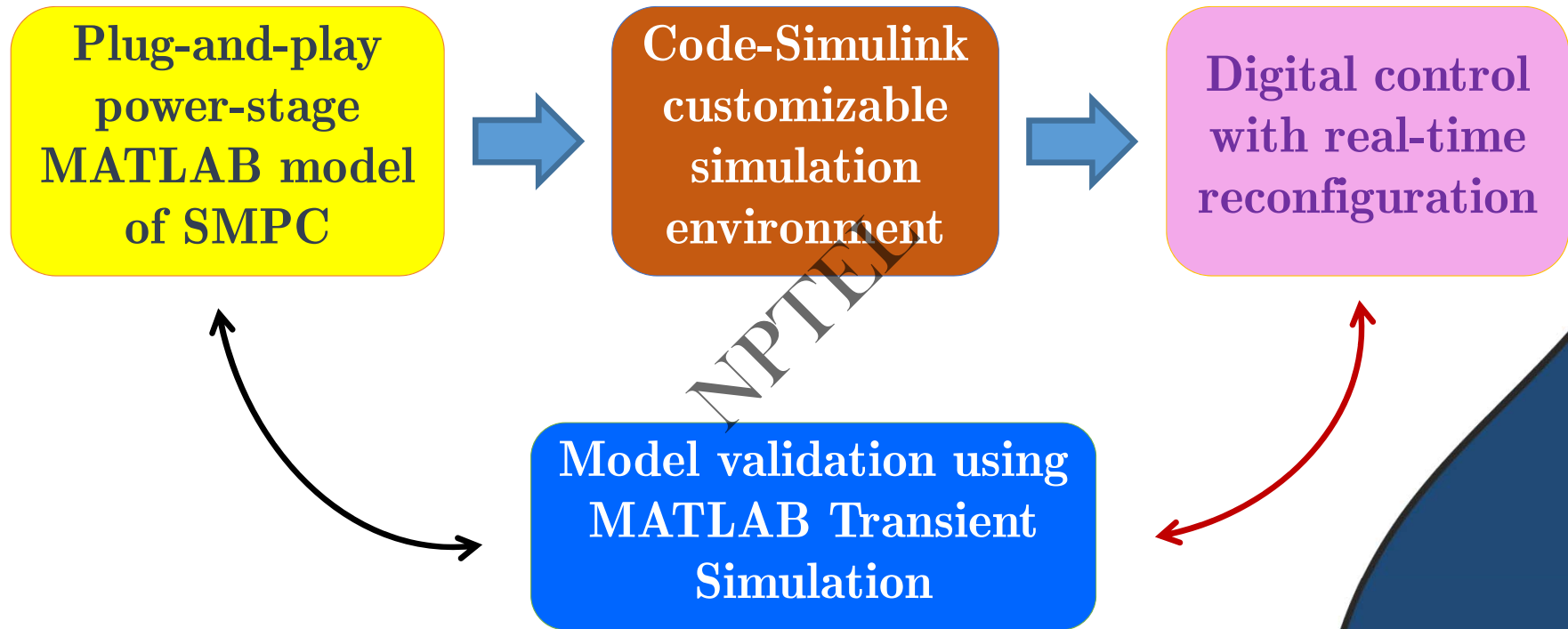

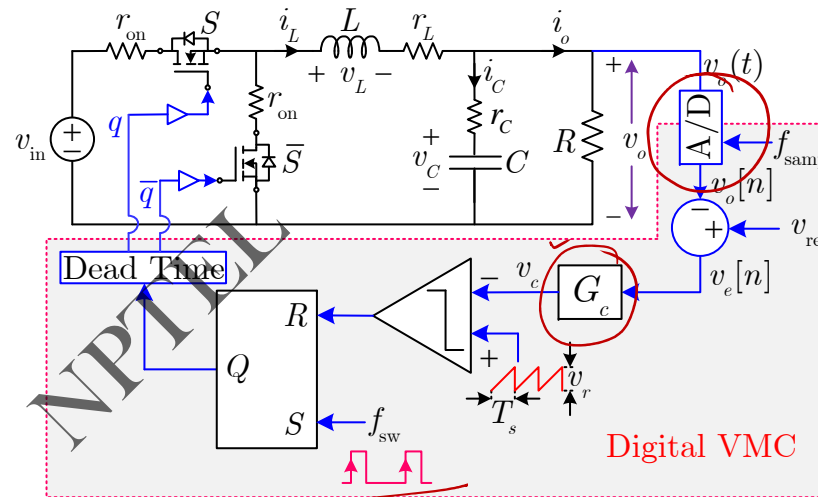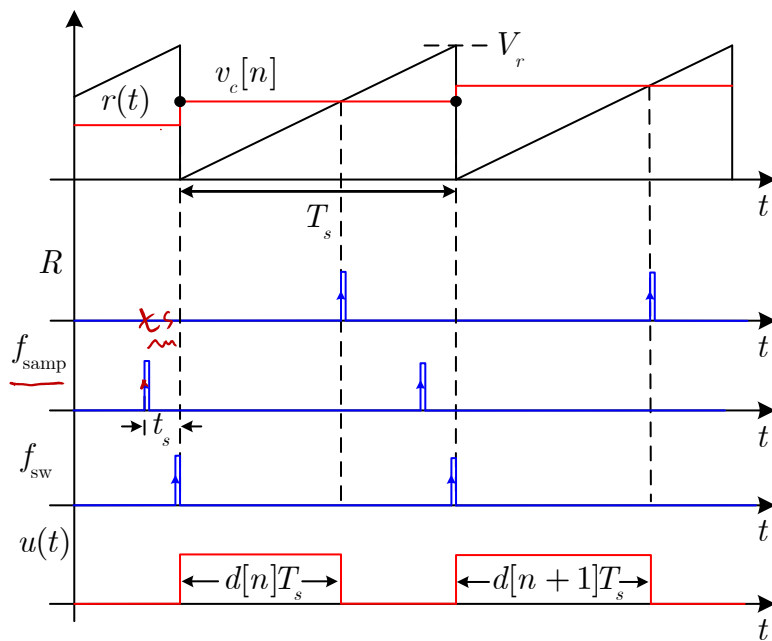Digital Voltage Mode Control (DVMMC) of Buck Converter



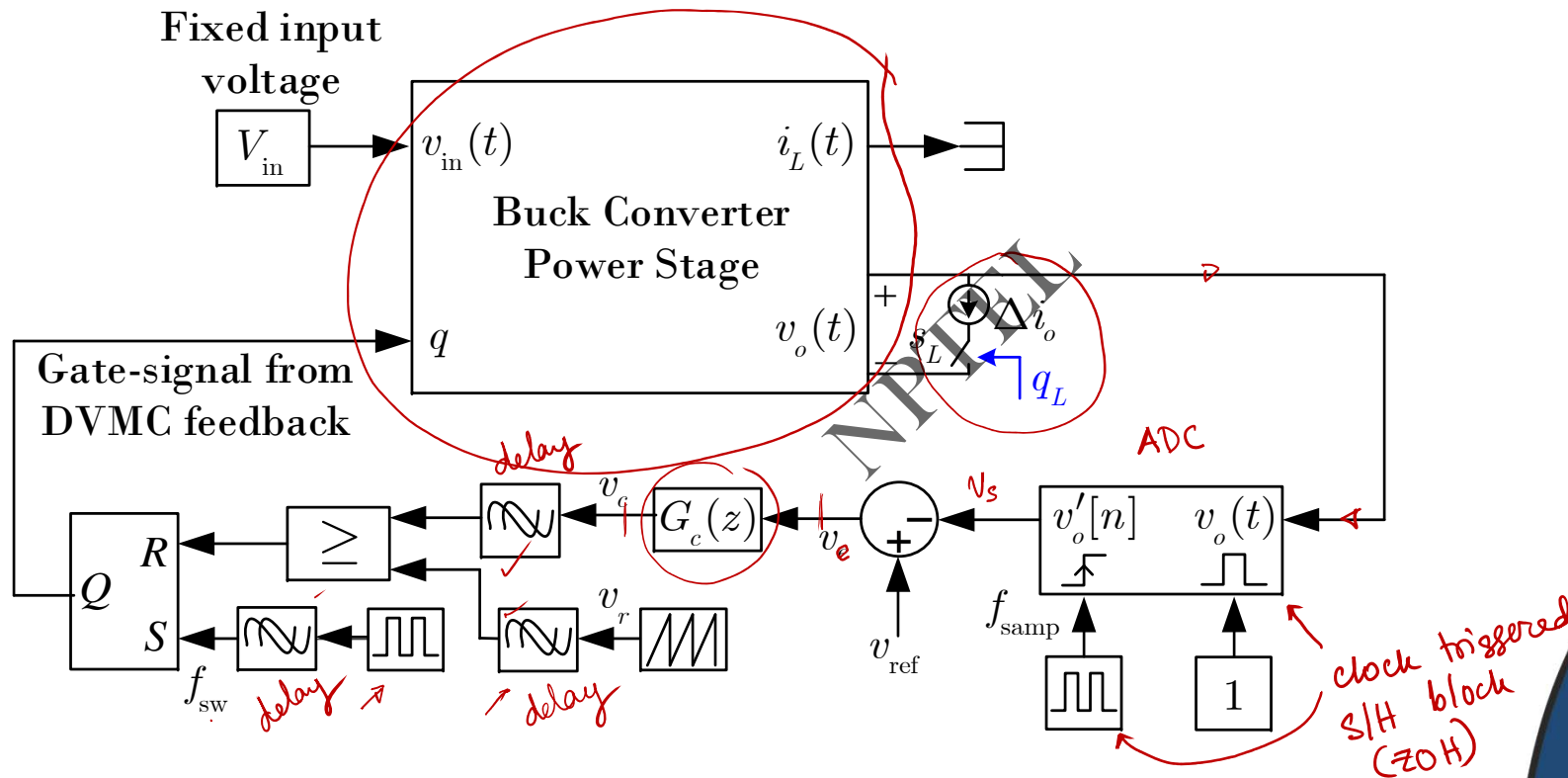Device Under Test (DUT) for Validation of DT Large-Signal Model



Validation of DT Large-Signal Model under Closed Loop

a) Using actual switch simulation

1. Provide initial conditions for $\underline{v_C}(t)$ and $\underline{i_L}(t)$
2. Do not turn on S_L for 1 ms and let the converter reach steady-state
3. Apply a load step
4. Capture time domain data and store as v_o and i_L

Validation of DT Large-Signal Model under Closed Loop (contd...)

b) Using DT large-signal model

1. Provide initial conditions for $v_C(t)$ and $i_L(t)$ same as those
in switch simulation
2. Let the DT large-signal model run for 1 ms
3. Capture $v_o(t)$ and $i_L(t)$ as the state variables throughout
the simulation time

Validation of DT Large-Signal Model under Closed Loop (contd...)

b) Using DT large-signal model

4. Change the load resistance at 1 ms to emulate a load step
5. Capture $v_o(t)$ and $i_L(t)$ as state variables for every sampling cycle throughout the simulation run time
6. Compare the captured data of v_o & i_L for DT large-signal validation

Steps to Verify Large-Signal DT Model using MATLAB


buck_conv_DVMC_simulation.m

```
clear; close all; clc;
%% Setting parameters
buck_parameter;
DCM_En=0;
N_tran=500; T_tran=2*N_tran*T;
t_start=0; t_sim=T_tran;
%% Controller parameters
Kp=10; Ki=0.3; Kd=20; t_s=0.1*T;
V_m=10; R1=1; R2=0.05; R=R1;

I_L_int=1; V_c_int=0.99;
V_s_int=V_c_int; V_integral=0;
.....
```

buck_parameter.m

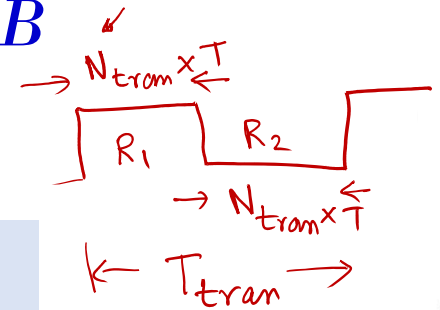
```
L=0.5e-6; % output inductance
C=200e-6; % output capacitance
T=2e-6; % switching time period
r_L=5e-3; % inductor DCR
v_d=0.55; % diode voltage drop
r_l=5e-3; % HS MOS on resistance
r_d=5e-3; % LS MOS on resistance
r_C=3e-3; % capacitor ESR
Vin=12; % input voltage
Vref=1; % ref. output voltage
Io_max=20; % max. load current
```



$$R_2 = 0.05 \Omega$$

$$I_{o2} = \frac{V_o}{R_2}$$

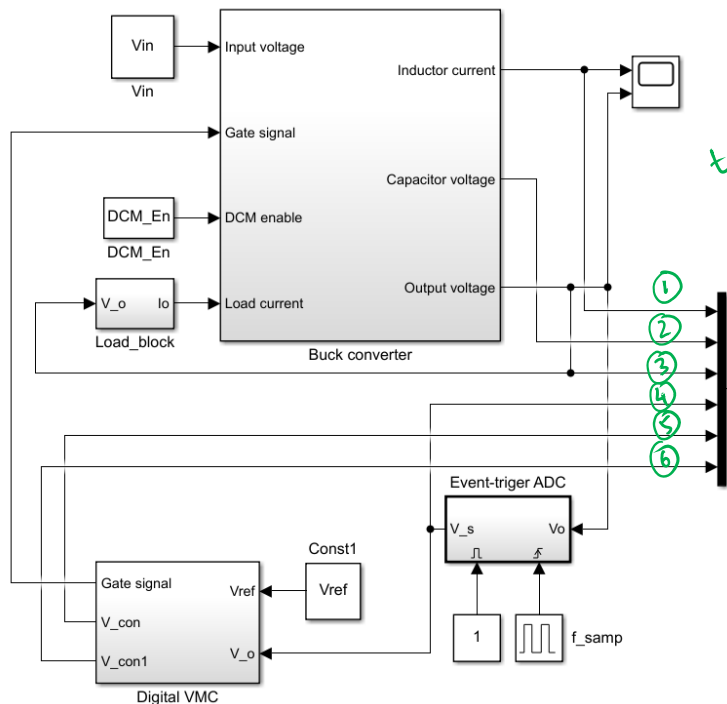Steps to Verify Large-Signal DT Model using MATLAB (contd...)



buck_conv_DVMC_simulation.m

```
.....
sim('buck_converter_DVMC.slx');

t=buck_result.time; t_scale=t*1e3;
x=buck_result.data; i_L=x(:,1);
V_cap=x(:,2); V_o=x(:,3);
V_s=x(:,4); V_n=x(:,5); Vr_d=x(:,6);
%% Plot subroutine
plot_buck_simulation;
```


t
 20000×1

structure

20000×6
 x

$i_L(t)$ $V_c(t)$
 $ch1$ $ch2$
 t
 $0 \rightarrow$
 Δt_1
 $\Delta t_1 + \Delta t_2$
 \vdots
 \vdots
 \vdots
 \uparrow

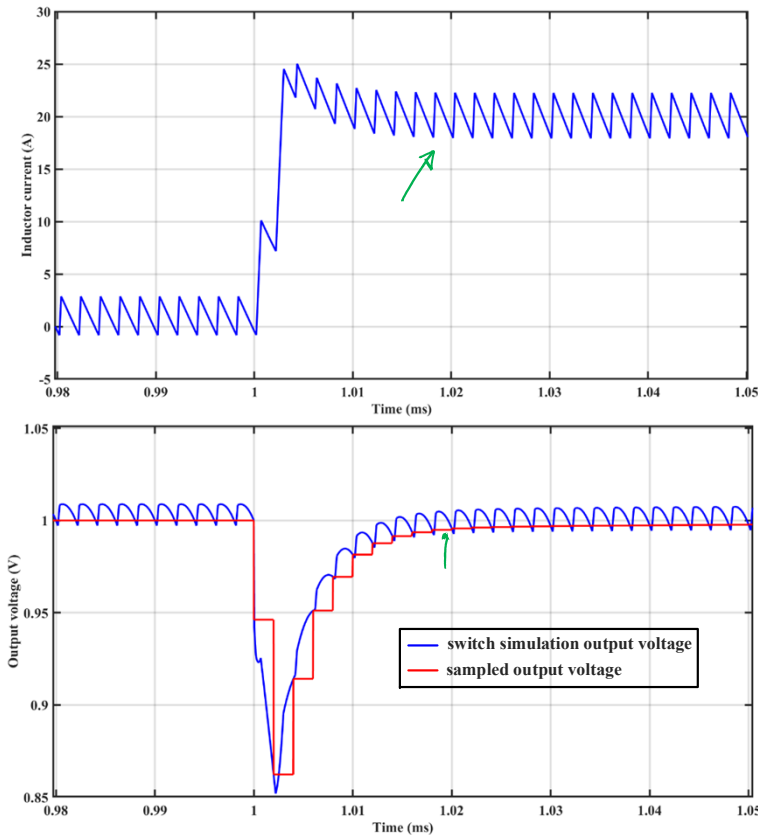Steps to Verify Large-Signal DT Model using MATLAB (contd...)



buck_conv_DVMC_simulation.m

```
.....
sim('buck_converter_DVMC.slx');

t=buck_result.time; t_scale=t*1e3;
x=buck_result.data; i_L=x(:,1);
V_cap=x(:,2); V_o=x(:,3);
V_s=x(:,4); V_n=x(:,5); Vr_d=x(:,6);
%% Plot subroutine
plot_buck_simulation;
```

Steps to Verify Large-Signal DT Model using MATLAB (contd...)

buck_DT_LSM_TE.m

```
clc;  
buck_parameter;  
Kp=10; Ki=0.3; Kd=20;  
t_s=0.1*T; V_m=10; R1=1;  
R2=0.05; R=R1; N_tran=500;  
  
buck_DT_model_matrices;  
  
.....
```

buck_DT_model_matrices.m

```
alpha=R/(R+r_C); r_e=(r_l+r_L);  
T_s=t_s; I_den=[1 0; 0 1];  
%% Define system, input and output matrices  
A_on=[-(r_e+(alpha*r_C))/L    -alpha/L;  
        alpha/C              -alpha/(R*C)];  
A_off=A_on; B=[1/L; 0];  
C_m=[r_C*alpha alpha];
```

$$A_{on} = A_{off} = \begin{bmatrix} -\frac{(r_e + \alpha r_C)}{L} & -\frac{\alpha}{L} \\ \frac{\alpha}{C} & -\frac{\alpha}{R C} \end{bmatrix}$$
$$C_0 = [\alpha r_C \quad \alpha]$$

Steps to Verify Large-Signal DT Model using MATLAB (contd...)

buck_DT_LSM_TE.m

```
.....  
i_L_n=I_L_int; v_cap_n=V_c_int;  
x_n=[i_L_n; v_cap_n];  
V_o_s=C_m*x_n; Vsam=v_cap_n;  
V_intg_int=0; Ve_int=0;  
t1=0; t1_scale=t1*1e3;  
  
figure(1)  
plot(t1_scale,x_n(1),'o','Linewidth', 2); hold on; grid on;  
  
figure(2)  
plot(t1_scale,Vsam,'o','Linewidth', 2); hold on; grid on;  
.....
```

Steps to Verify Large-Signal DT Model using MATLAB (contd...)

buck_DT_dynamics.m

```

for n=0:N_tran-1
    figure(2)
    plot(tl_scale,Vsam,'o','Linewidth', 2); hold on; grid on;
    Ve=(Vref-Vsam);
    V_intg=V_intg_int+(Ki*Ve); V_intg_int=V_intg;
    V_der=Kd*(Ve-Ve_int); Ve_int=Ve;
    Vcon=(Kp*Ve)+V_intg+V_der; D_temp=Vcon/V_m;

    if D_temp<0
        D=0;
    elseif D_temp>1
        D=1;
    end

    .....
    
```

N_{tran}
0 to $N_{tran}-1$

buck_DT_LSM_TE.m

```

.....
%% DT Large-Signal Model
buck_DT_dynamics;
R=R2; N_tran=500;
buck_DT_model_matrices;
V_o_s=C_m*x_n;
Vsam=V_o_s;
buck_DT_dynamics;
    
```

$$D = \frac{V_{con}}{V_m}$$



Steps to Verify Large-Signal DT Model using MATLAB (contd...)

buck_DT_dynamics.m

```

.....
    else
        D=D_temp;
    end

    A_LS=(expm(A_on*T));
    B_LS=(expm(A_on*(T-(D*T)-T_s)))*((expm(A_on*(D*T))-I_den)*(inv(A_on))*B;
    x_n1=A_LS*x_n+B_LS*Vin;
    t1=t1+T; t1_scale=t1*1e3;
    x_n=x_n1; V_o_s=C_m*x_n; Vsam= V_o_s;
    figure(1)
    plot(t1_scale,x_n(1),'o','Linewidth', 2); hold on; grid on;
end
    
```


$$x_{n+1} = A_{eq} x_n + B_{eq} V_{in}$$

$$A_{eq} = e^{A_{on} T}$$


expm(A_{on}T)

$$B_{eq} = e^{A_{on}(T-DT-t_s)} \cdot [e^{A_{on}DT} - I] A^{-1} B$$

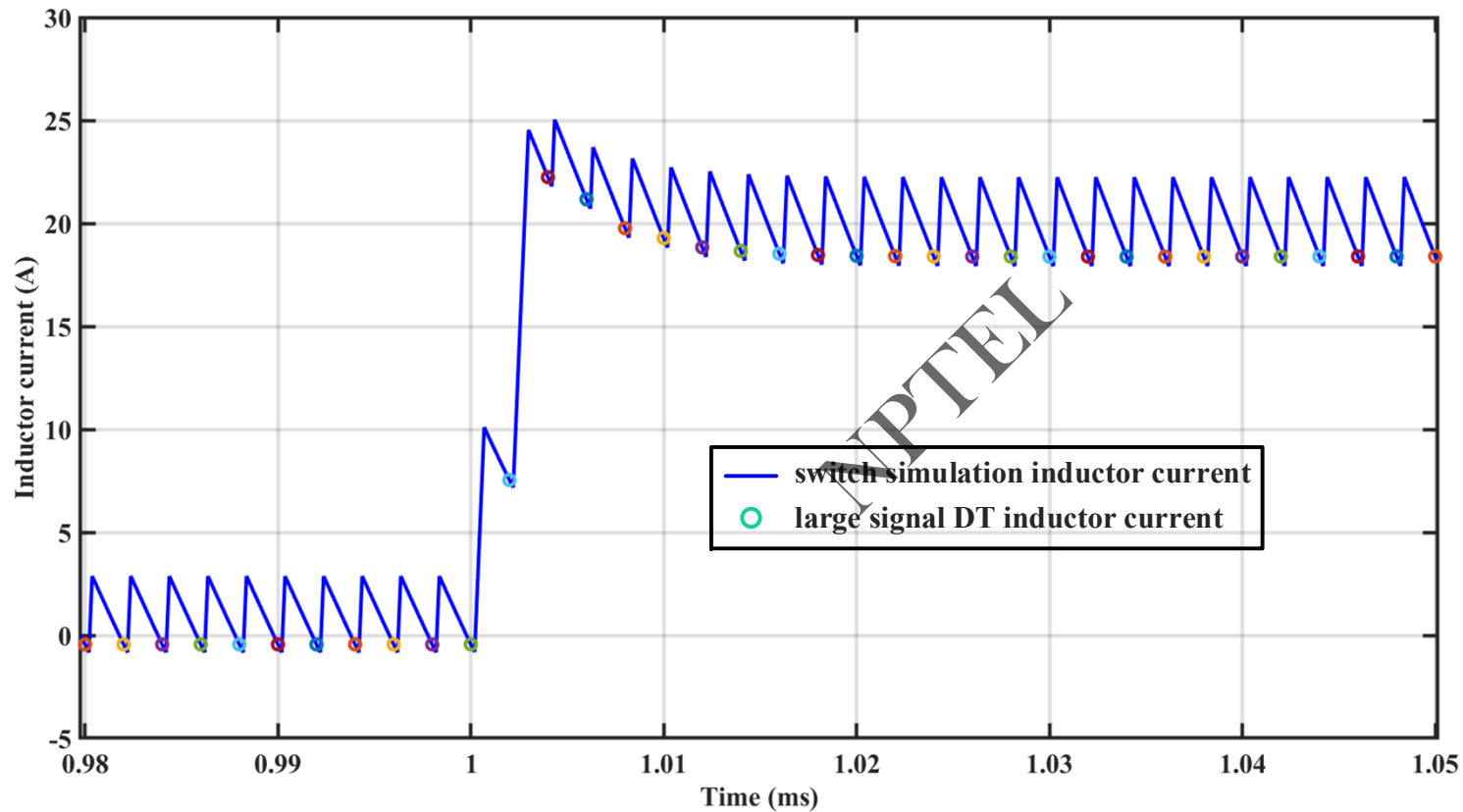Steps to Verify Large-Signal DT Model using MATLAB (contd...)




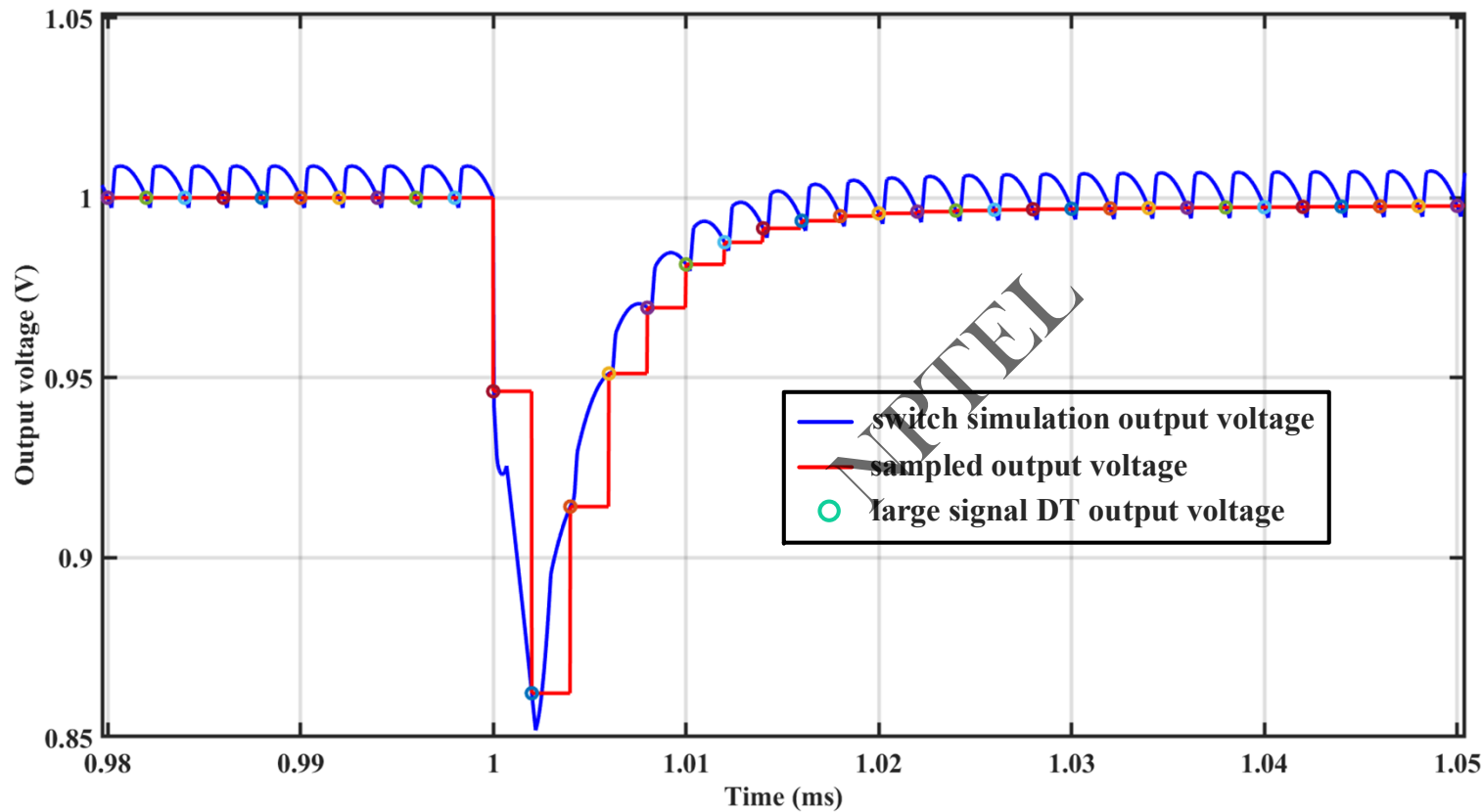Steps to Verify Large-Signal DT Model using MATLAB (contd...)



CONCLUSION

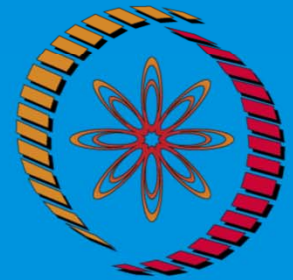- Recall of digital control architectures and MATLAB models
- Steps for simulation using MATLAB detailed switch models and discrete-time large-signal models
- MATLAB codes and step-by-step methods for model validation
- Validation case studies using a Buck Converter



**THANK
YOU !**