



NPTEL ONLINE CERTIFICATION COURSES

DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING

Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR

Module 02: Fixed and Variable Frequency Digital Control Architectures



Lecture 19: Overview of Digital Hysteresis Control Architectures




CONCEPTS COVERED

- Current hysteresis control with analog current loop
- Mixed-signal current hysteresis control and control waveforms
- Benefits of mixed-signal current hysteresis control

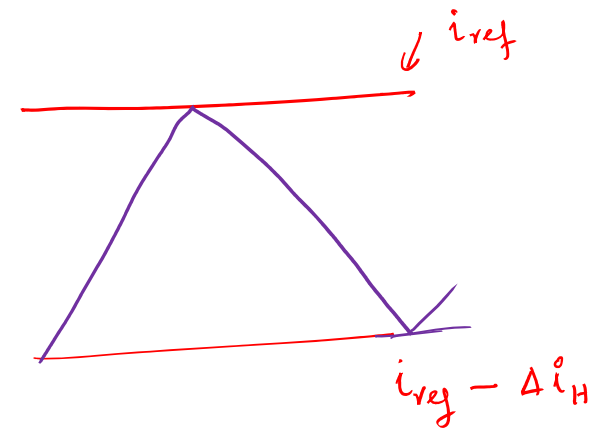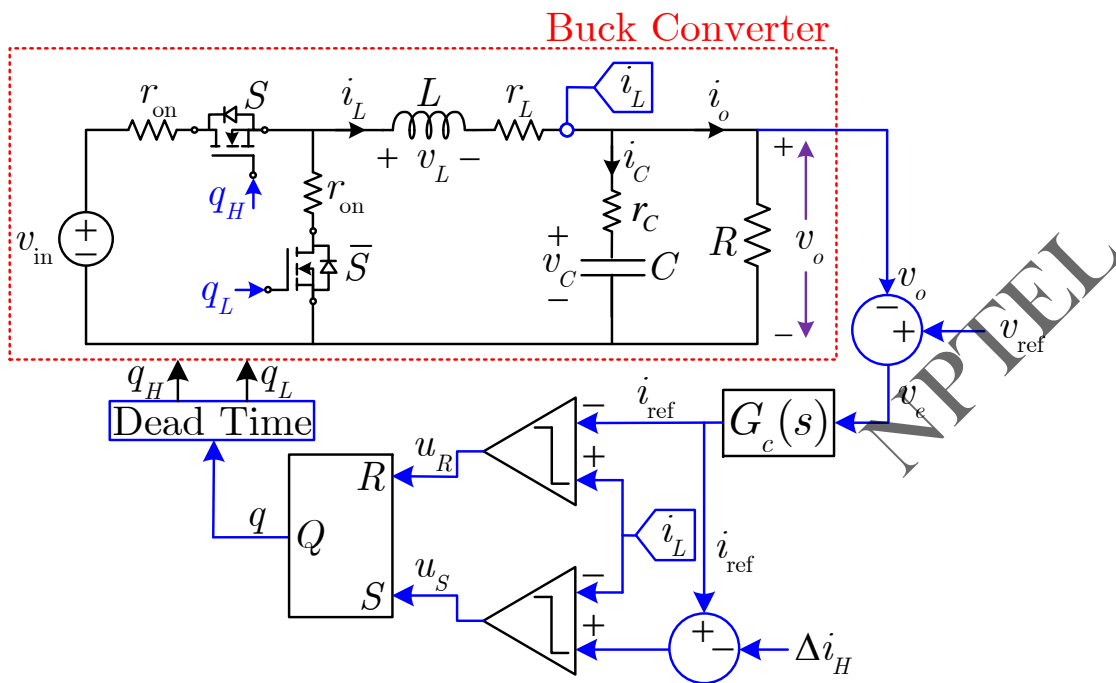Analog Hysteresis CMC in a Buck Converter




Closing Digital Loop

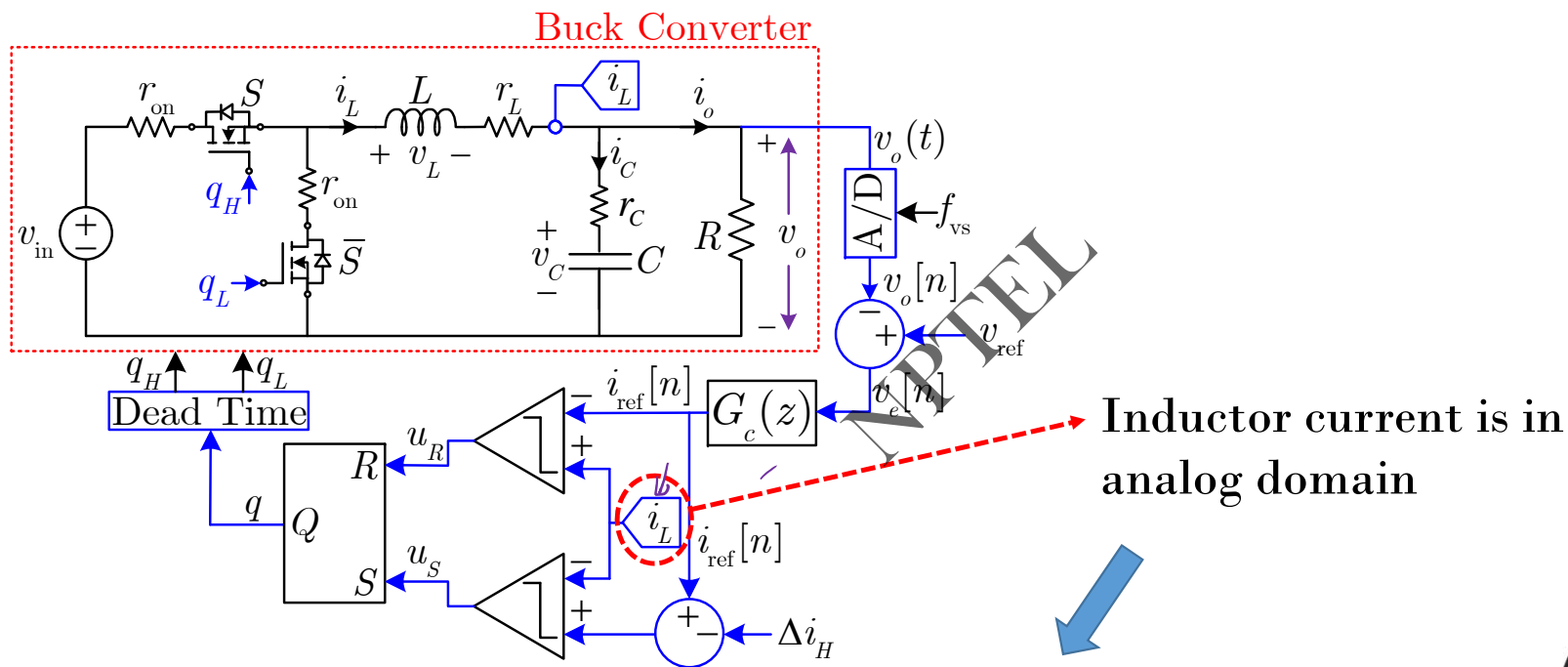


DAC converter is needed to generate analog current reference

Closing Digital Loop (contd...)


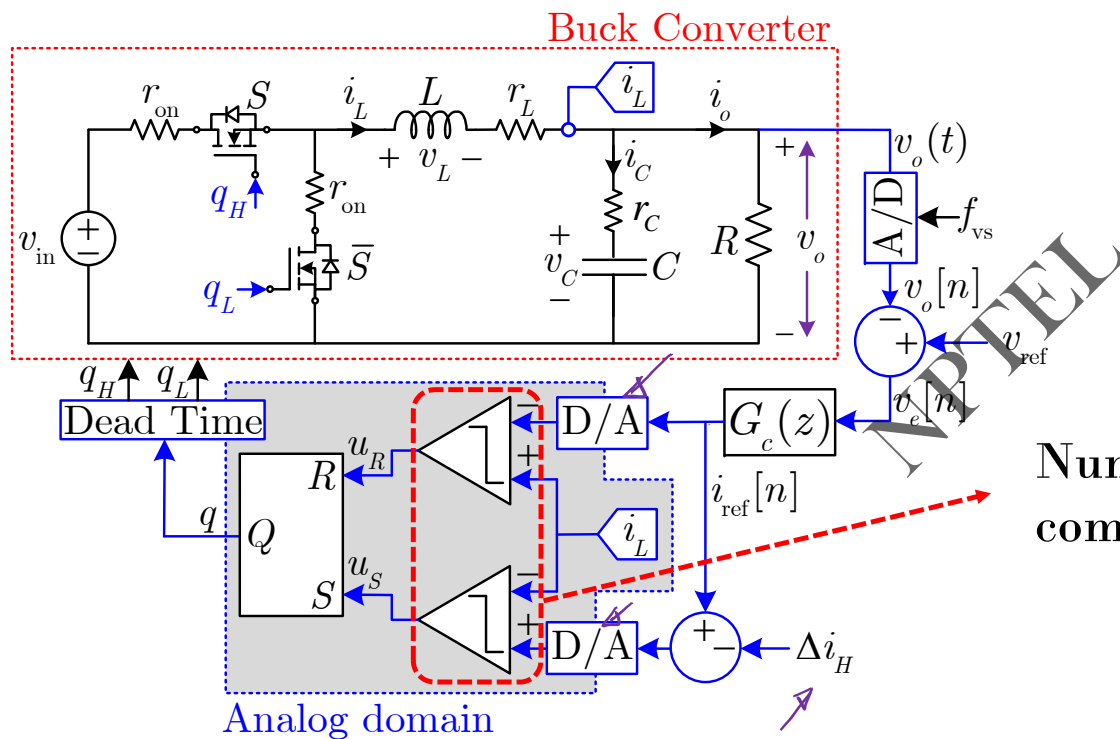


Number of DACs and analog comparator increases

Closing Digital Loop (contd...)

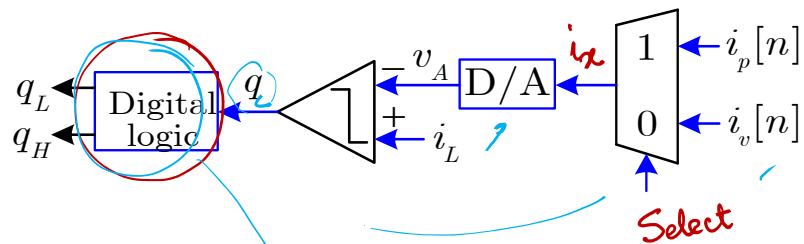


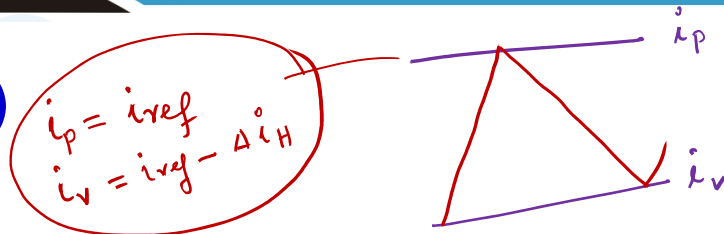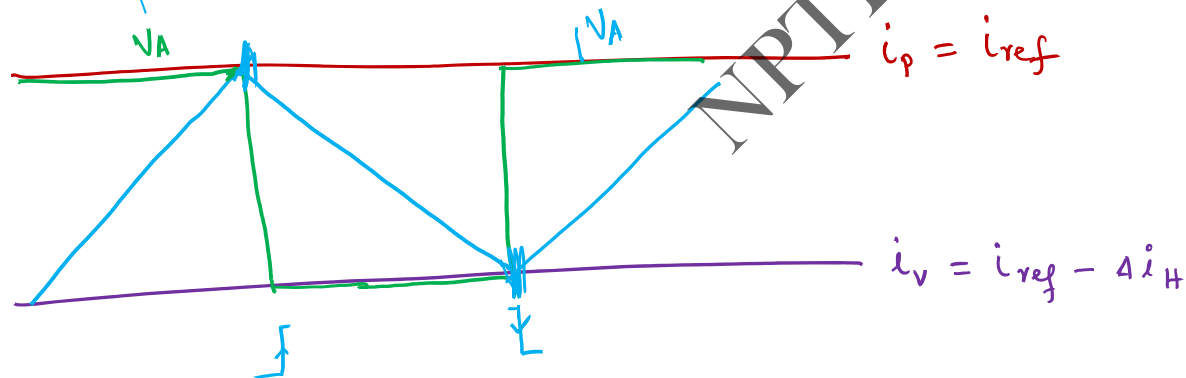Mixed signal hysteresis current controller block




[S. Kapat, "Parameter-Insensitive Mixed-Signal Hysteresis-Band ... ", *IEEE TPEL*, 2017]

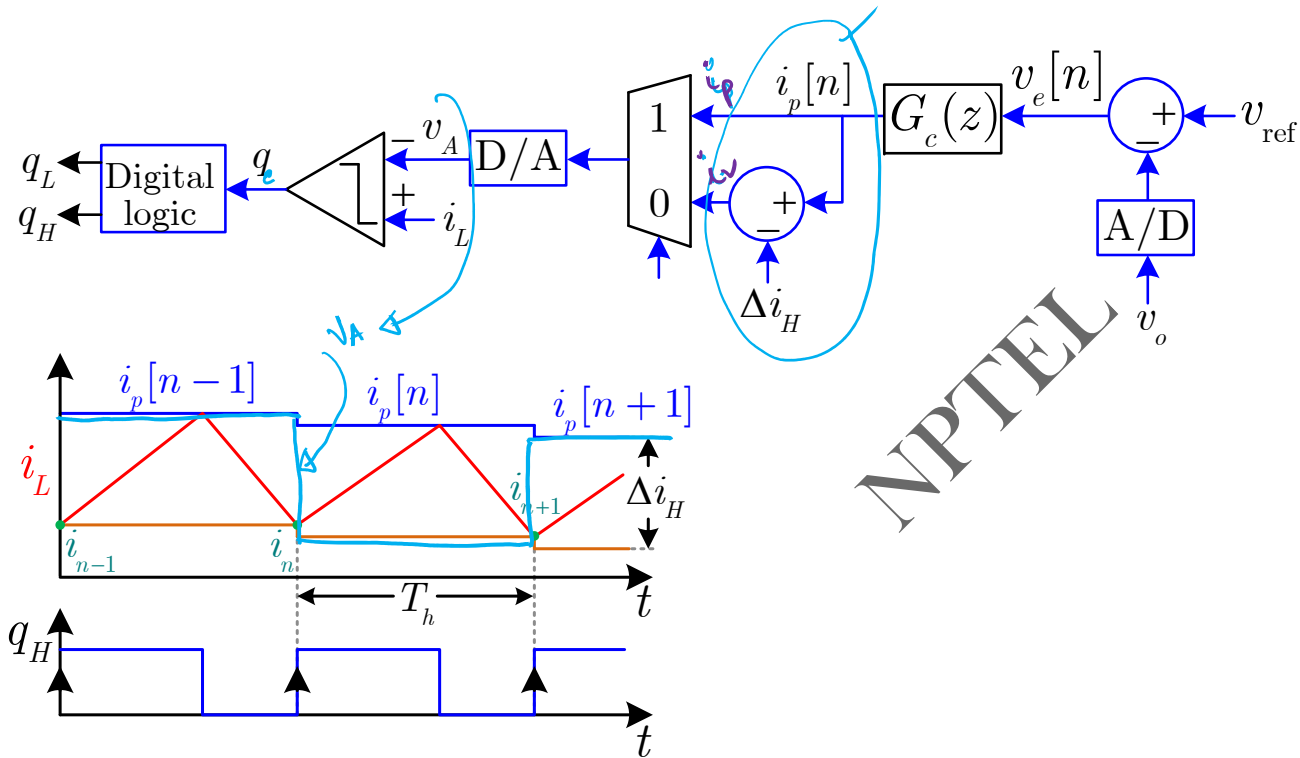Control Waveforms of Peak Current-mode MSHCC





[S. Kapat, "Parameter-Insensitive Mixed-Signal Hysteresis-Band ... ", *IEEE TPEL*, 2017]

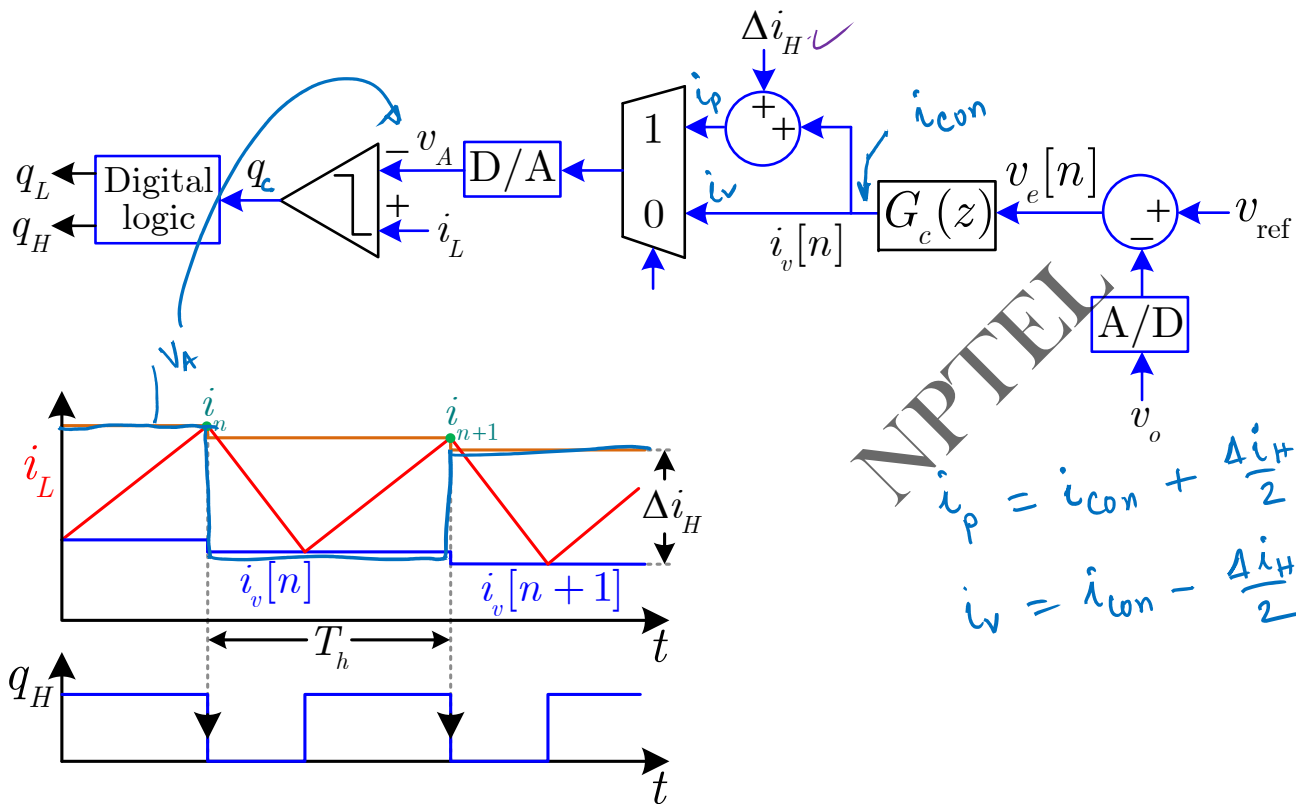Control Waveforms of Valley Current-mode MSHCC



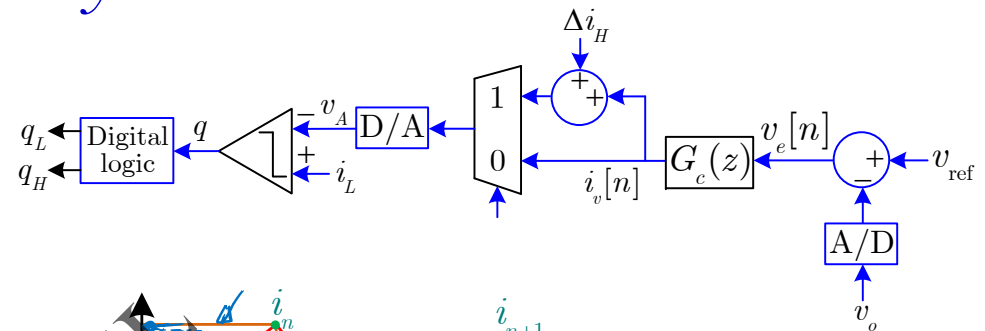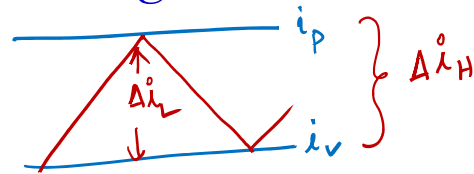Benefits of Mixed-Signal Current Hysteresis Control



— $\Delta i_L \approx \Delta i_H$

$$\Delta i_L = m_1 t_{on} = \Delta i_H$$

$$t_{on} = \frac{\Delta i_H}{m_1}$$

— Programmable f_{sw}


$$= m_1 dT$$

— Very fast transient

$$\Delta i_{H1} \rightarrow T_1$$


$$\Delta i_{H2} \rightarrow T_2$$
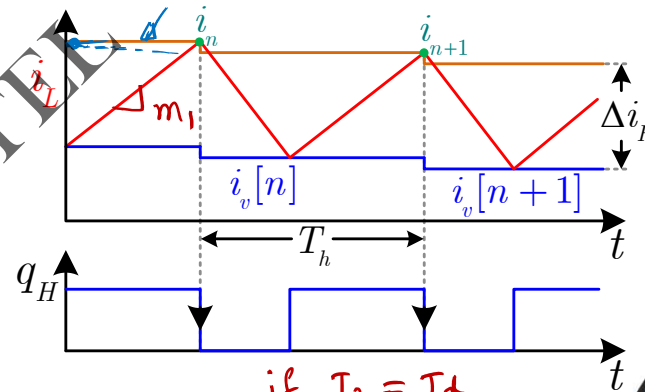
$$\frac{\Delta i_{H2}}{\Delta i_{H1}} = \frac{T_2}{T_1} \quad \Delta i_{H2} = \frac{\Delta i_{H1}}{T_1} \propto T_d$$



CONCLUSION

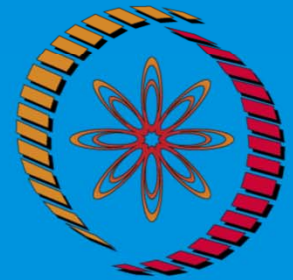- Current hysteresis control with analog current loop
- Mixed-signal current hysteresis control and control waveforms
- Benefits of mixed-signal current hysteresis control



**THANK
YOU !**