



**NPTEL ONLINE CERTIFICATION COURSES**

# **DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING**

**Dr. Santanu Kapat**

**Electrical Engineering Department, IIT KHARAGPUR**

**Module 04: Modeling Techniques and Mode Validation using MATLAB**


**Lecture 34: Derivation of Discrete-Time Large-Signal Models**



## CONCEPTS COVERED

- Discrete-time modeling in DC-DC converters
- Derivation of discrete-time large-signal models
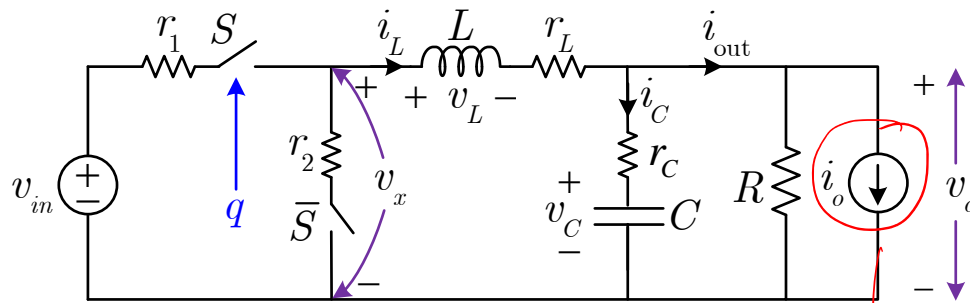
## State-Space Matrices of a Synchronous Buck Converter



Synchronous buck converter

$$B_1 = \begin{bmatrix} \frac{1}{L} & \frac{\alpha r_C}{L} \\ 0 & -\frac{\alpha}{C} \end{bmatrix} \quad B_2 = \begin{bmatrix} 0 & \frac{\alpha r_C}{L} \\ 0 & -\frac{\alpha}{C} \end{bmatrix}$$

$r_1 = r_2$

$$A_1 = A_2 = A = \begin{bmatrix} -\frac{(r_e + \alpha r_C)}{L} & -\frac{\alpha}{L} \\ \frac{\alpha}{C} & -\frac{\alpha}{RC} \end{bmatrix}$$

$$B_1 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \quad B_2 = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$


in absence of current sink

## Waveforms under Trailing-Edge Modulation with Interval-2 Sampling



Two subsequent sampling points
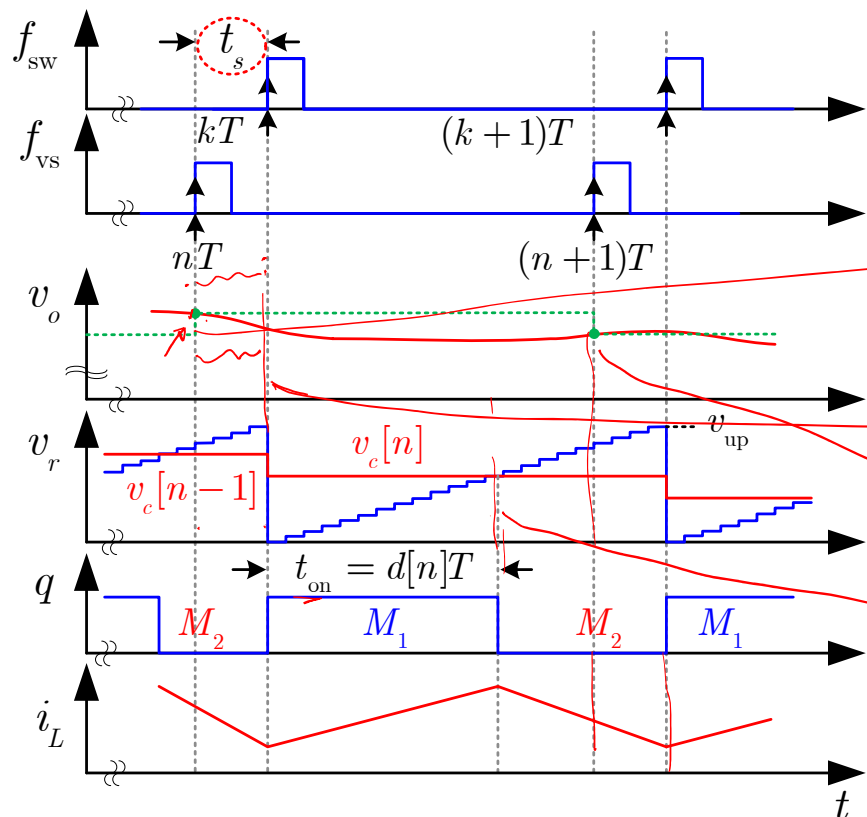
# Periodic Evolution of State Vector over within a Sampling Cycle



$$x(t) = \begin{bmatrix} i_L(t) \\ v_o(t) \end{bmatrix}$$

$$v_o(t) = C_o x(t)$$

Let  $x(t)|_{t=nT} = x_n$  initial state

$x(t)|_{t=nT+t_s} = x_1$



$x(t)|_{t=nT+t_s+t_{on}} = x_2$

$x(t)|_{t=(n+1)T} = x_{n+1}$  final state


intermediate states


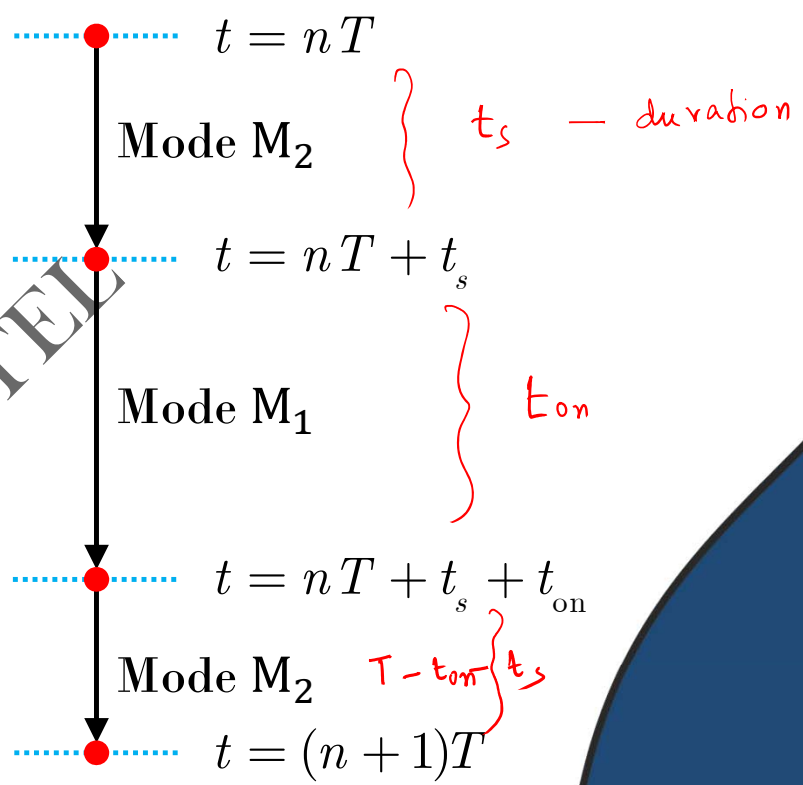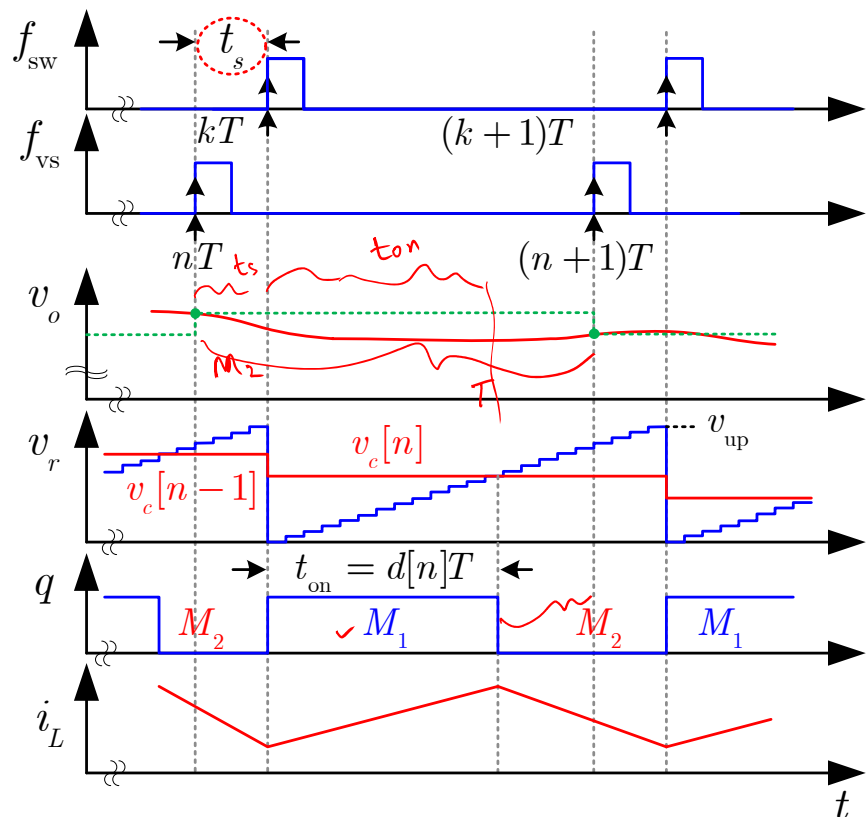
# Periodic Evolution of State Vector over within a Sampling Cycle (contd..)


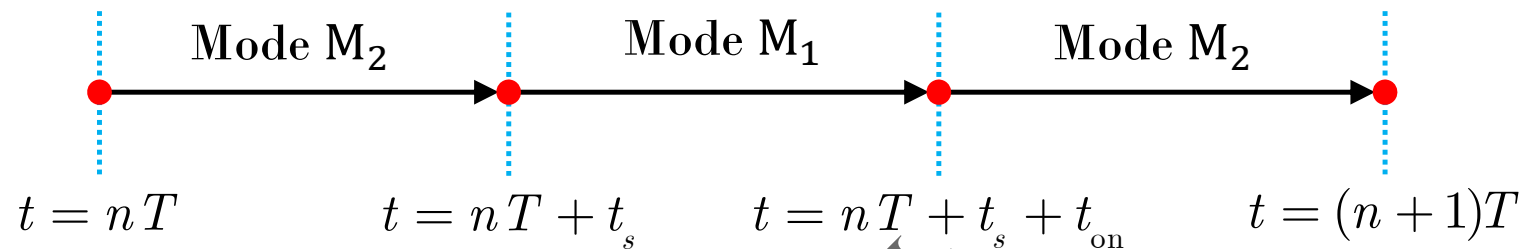
# Periodic Evolution of State Vector over within a Sampling Cycle (contd..)



S. No.	Mode	Duration	Initial state vector	Final state vector	State matrices
1.	M <sub>2</sub>	$nT \leq t < nT + t_s$	$x_n$	$\bar{x}_1$	$A_2, B_2$
2.	M <sub>1</sub>	$nT + t_s \leq t < nT + t_s + t_{on}$	$x_1$	$x_2$	$A_1, B_1$
3.	M <sub>2</sub>	$nT + t_s + t_{on} \leq t < (n+1)T$	$x_2$	$x_{n+1}$	$A_2, B_2$

[S. Kapat, "An Analytical Approach of Discrete-Time Modeling ..." *IEEE APEC*, 2021]

## Discrete-Time Large-Signal Model with Resistive Load

S. No.	Mode	Duration	Initial state vector	Final state vector	State matrices
1.	M <sub>2</sub>	$nT \leq t < nT + t_s$	$x_n$	$x_1$	$A_2 = A, B_2 = 0$
2.	M <sub>1</sub>	$nT + t_s \leq t < nT + t_s + t_{on}$	$x_1$	$x_2$	$A_1 = A, B_1$
3.	M <sub>2</sub>	$nT + t_s + t_{on} \leq t < (n+1)T$	$x_2$	$x_{n+1}$	$A_2 = A, B_2 = 0$

State-space solution

$$x(t) = e^{A_q(t-t_o)} x(t_o) + (e^{A_q(t-t_o)} - I) A_q^{-1} B_q u$$

$t = nT + t_s$   
 $t_o = nT$

$$t_o = nT \Rightarrow x(t_o) = x_n$$

$$t = nT + t_s \Rightarrow x(t) = x_1$$

$$\text{Mode M}_2 \Rightarrow x_1 = e^{At_s} x_n$$



## Discrete-Time Large-Signal Model with Resistive Load (contd..)

S. No.	Mode	Duration	Initial state vector	Final state vector	State matrices
1.	M <sub>2</sub>	$nT \leq t < nT + t_s$	$x_n$	$x_1$	$A_2 = A, B_2 = 0$
2.	M <sub>1</sub>	$nT + t_s \leq t < nT + t_s + t_{on}$	$x_1$	$x_2$	$A_1 = A, B_1$
3.	M <sub>2</sub>	$nT + t_s + t_{on} \leq t < (n+1)T$	$x_2$	$x_{n+1}$	$A_2 = A, B_2 = 0$

State-space solution

$$x(t) = e^{A_q(t-t_o)} x(t_o) + (e^{A_q(t-t_o)} - I) A_q^{-1} B_q u$$

$$A_1 = A_2 = A$$

$$t_o = nT + t_s \Rightarrow x(t_o) = x_1$$

$$t = nT + t_s + t_{on} \Rightarrow x(t) = x_2$$

$$\text{Mode } M_1 \Rightarrow x_2 = e^{A t_{on}} x_1 + (e^{A t_{on}} - I) A^{-1} B_1 v_{in}$$

## Discrete-Time Large-Signal Model with Resistive Load (contd..)

S. No.	Mode	Duration	Initial state vector	Final state vector	State matrices
1.	M <sub>2</sub>	$nT \leq t < nT + t_s$	$x_n$	$x_1$	$A_2 = A, B_2 = 0$
2.	M <sub>1</sub>	$nT + t_s \leq t < nT + t_s + t_{on}$	$x_1$	$x_2$	$A_1 = A, B_1$
3.	M <sub>2</sub>	$nT + t_s + t_{on} \leq t < (n+1)T$	$x_2$	$x_{n+1}$	$A_2 = A, B_2 = 0$

State-space solution

$$x(t) = e^{A_q(t-t_o)} x(t_o) + (e^{A_q(t-t_o)} - I) A_q^{-1} B_q u$$

$T - t_{on} - t_s$

$$t_o = nT + t_s + t_{on} \Rightarrow x(t_o) = x_2$$

$$t = (n+1)T \Rightarrow x(t) = x_{n+1}$$

$$\text{Mode M}_2 \Rightarrow x_{n+1} = e^{A(T-t_{on}-t_s)} x_2 + (0)$$

## Discrete-Time Large-Signal Model with Resistive Load (contd..)

S. No.	Mode	Duration	Initial state vector	Final state vector	State matrices
1.	M <sub>2</sub>	$nT \leq t < nT + t_s$	$x_n$	$x_1$	$A_2 = A, B_2 = 0$
2.	M <sub>1</sub>	$nT + t_s \leq t < nT + t_s + t_{on}$	$x_1$	$x_2$	$A_1 = A, B_1$
3.	M <sub>2</sub>	$nT + t_s + t_{on} \leq t < (n+1)T$	$x_2$	$x_{n+1}$	$A_2 = A, B_2 = 0$

$$x_n \rightarrow x_1 \rightarrow x_2 \rightarrow x_{n+1}$$

Mode M<sub>2</sub>:  $x_1 = e^{At_s} x_n$

Mode M<sub>1</sub>:  $x_2 = e^{At_{on}} x_1 + (e^{At_{on}} - I)A^{-1}B_1 v_{in}$

Mode M<sub>2</sub>:  $x_{n+1} = e^{A(T-t_{on}-t_s)} x_2$

[S. Kapat, "An Analytical Approach of Discrete-Time Modeling ..." *IEEE APEC*, 2021]

# Discrete-Time Large-Signal Model with Resistive Load (contd..)

Eliminate  $x_1$  and  $x_2$  to obtain  $x_{n+1}$  in terms of  $x_n$

Mode M<sub>2</sub>:  $x_1 = e^{At_s} x_n$

Mode M<sub>1</sub>:  $x_2 = e^{At_{on}} x_1 + (e^{At_{on}} - I)A^{-1}B_1 v_{in}$   
*in terms of  $x_n$*

Mode M<sub>2</sub>:  $x_{n+1} = e^{A(T-t_{on}-t_s)} x_2$

## Large-Signal Discrete-Time Model

$$x_{n+1} = e^{AT} x_n + e^{A(T-t_{on}-t_s)} (e^{At_{on}} - I) A^{-1} B_1 v_{in}$$

*Handwritten notes:*  
 $e^{A_1 t_1} \cdot e^{A_2 t_2} = e^{(A_1 t_1 + A_2 t_2)}$   
 $A_1 A_2 \neq A_2 A_1$   
 if

*Handwritten derivation:*  
 $e^{At_s} \cdot e^{At_{on}} \cdot e^{A(T-t_{on}-t_s)}$   
 $= e^{A(t_s + t_{on} + T - t_{on} - t_s)}$   
 $= e^{AT}$

## Complete Discrete-Time Large-Signal Model with Resistive Load

### Large-Signal Discrete-Time Model

$$x_{n+1} = e^{AT} x_n + e^{A(T-t_{\text{on}}-t_s)} (e^{At_{\text{on}}} - I) A^{-1} B_1 v_{\text{in}}$$


$$x_{n+1} = \begin{bmatrix} i_L[n+1] \\ v_c[n+1] \end{bmatrix}$$

$$x_{n+1} = \overset{2 \times 1}{e^{AT}} \overset{2 \times 2}{x_n} + \overset{2 \times 2}{e^{A(T-t_{\text{on}}-t_s)}} (\overset{2 \times 2}{e^{At_{\text{on}}} - I}) \overset{2 \times 2}{A^{-1}} \overset{2 \times 1}{B_1} \overset{1 \times 1}{v_{\text{in}}} \triangleq f(x_n, t_{\text{on}}) = \begin{bmatrix} f_1 \\ f_2 \end{bmatrix}$$

[S. Kapat, "An Analytical Approach of Discrete-Time Modeling ..." *IEEE APEC*, 2021]
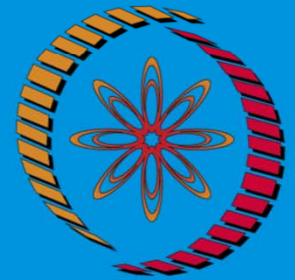
## CONCLUSION

- Discrete-time modeling in DC-DC converters
- Derivation of discrete-time large-signal models



**THANK  
YOU !**