



NPTEL ONLINE CERTIFICATION COURSES

DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING

Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR

Module 04: Modeling Techniques and Mode Validation using MATLAB


Lecture 39: Discrete-Time Transfer Functions and Closed Loop Block Diagrams




CONCEPTS COVERED

- Step-by-step derivations of various discrete-time transfer functions
- Discrete-time control-to-current and control-to-output TFs
- Loop transfer function under digital voltage mode control
- Loop transfer function under digital current mode control

State-Space Modeling of DC-DC Converters

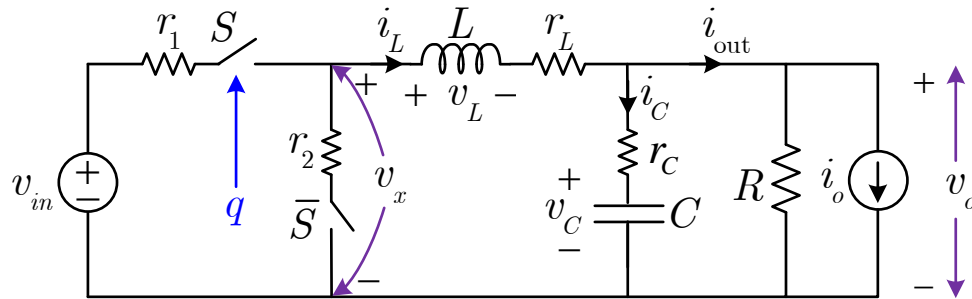

Synchronous buck converter

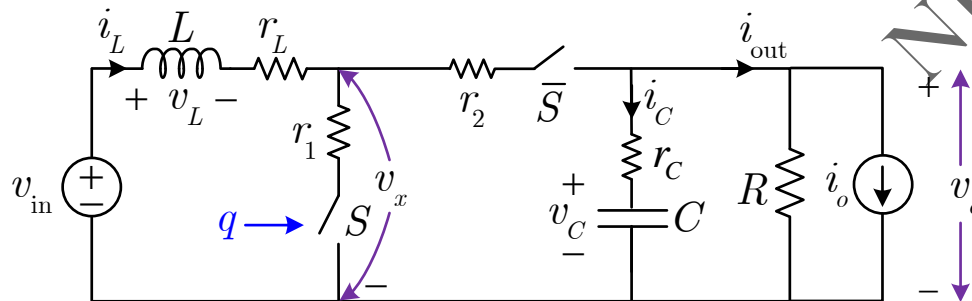

Synchronous boost converter

State variables:

$x_1 = i_L$ inductor current

$x_2 = v_C$ capacitor voltage

$$x = \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

Input variables:

$u_1 = v_{in}$ input voltage

$u_2 = i_o$ sink current

$$u = \begin{bmatrix} v_{in} \\ i_o \end{bmatrix}$$

State-Space Modeling of DC-DC Converters (contd...)

- State-space model

$$\dot{x} = A_q x + B_q u$$


Buck converter matrices

$$A_q = \begin{bmatrix} -\frac{(r_e + \alpha r_c)}{L} & -\frac{\alpha}{L} \\ \frac{\alpha}{C} & -\frac{1}{RC} \end{bmatrix} \quad B_q = \begin{bmatrix} \frac{q}{L} & \frac{\alpha r_c}{L} \\ 0 & -\frac{\alpha}{C} \end{bmatrix}$$

where $r_e = r_1 + r_L$ and $\alpha = \frac{R}{R + r_c}$

[For details, refer to [Lecture~33](#) of this course]

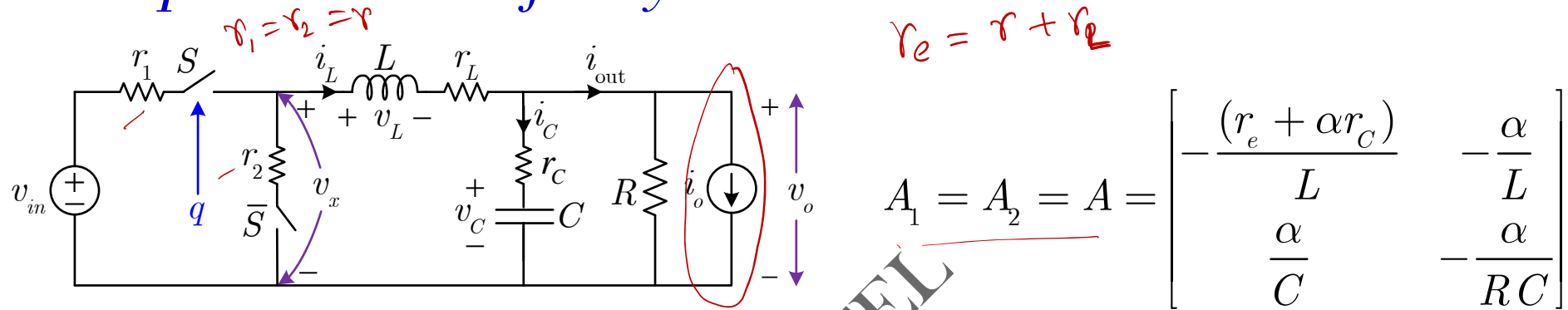State-Space Matrices of a Synchronous Buck Converter



Synchronous buck converter

$$B_1 = \begin{bmatrix} \frac{1}{L} & \frac{\alpha r_C}{L} \\ 0 & -\frac{\alpha}{C} \end{bmatrix} \quad B_2 = \begin{bmatrix} 0 & \frac{\alpha r_C}{L} \\ 0 & -\frac{\alpha}{C} \end{bmatrix}$$

$$B_1 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \quad B_2 = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

in absence of current sink

Discrete-Time Large Signal and Small Signal Model

Large-Signal Discrete-Time Model

$$x_{n+1} = e^{AT} x_n + e^{A(T-t_{\text{on}}-t_s)} (e^{At_{\text{on}}} - I) A^{-1} B_1 v_{\text{in}}$$

$$C_{\text{eq}} = [\alpha r_c \quad \alpha]$$

$$\alpha = \frac{R}{R+r_c}$$

$$v_o[n] = C_{\text{eq}} x_n$$

Small-Signal Discrete-Time Model

$$\tilde{x}_{n+1} = A_{\text{eq}} \tilde{x}_n + B_{\text{eq}} \tilde{d}$$

$$\tilde{v}_o[n] = C_{\text{eq}} \tilde{x}_n$$

$$B_1 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}$$

where $A_{\text{eq}} = e^{AT}$ and $B_{\text{eq}} = e^{A(T-t_d)} B_1 V_{\text{in}} T$

[For details, refer to [Lecture~38](#) of this course]

Small-Signal Transfer Functions

$$\tilde{x}_{n+1} = A_{\text{eq}} \tilde{x}_n + B_{\text{eq}} \tilde{d} \quad \text{and} \quad \tilde{v}_o[n] = C_{\text{eq}} \tilde{x}_n$$

Apply Z-transformation

$$\Rightarrow \tilde{x}(z) \times zI = A_{\text{eq}} \tilde{x}(z) + B_{\text{eq}} \tilde{d}(z) \quad \text{and} \quad \tilde{v}_o(z) = C_{\text{eq}} \tilde{x}(z)$$

$$\Rightarrow \tilde{x}(z) = (zI - A_{\text{eq}})^{-1} B_{\text{eq}} \tilde{d}(z)$$

$$\Rightarrow \frac{\overset{2 \times 1}{\tilde{x}(z)}}{\underset{1 \times 1}{\tilde{d}(z)}} = \boxed{\overset{2 \times 1}{(zI - A_{\text{eq}})^{-1} B_{\text{eq}}}}$$

Small-Signal Transfer Functions

$$\tilde{x}_{n+1} = A_{\text{eq}} \tilde{x}_n + B_{\text{eq}} \tilde{d}$$

$$\frac{\tilde{x}(z)}{\tilde{d}(z)} = \left(zI - A_{\text{eq}} \right)^{-1} B_{\text{eq}}$$

$$\tilde{i}_L(z) = [1 \ 0] \tilde{x}(z)$$

$$\Rightarrow G_{\text{id}}(z) = \frac{\tilde{i}_L(z)}{\tilde{d}(z)} = [1 \ 0] \left(zI - A_{\text{eq}} \right)^{-1} B_{\text{eq}}$$

Control-to-current
transfer function

$$\tilde{x}(z) = \begin{bmatrix} \tilde{i}_L(z) \\ \tilde{v}_c(z) \end{bmatrix}$$
$$\tilde{i}_L(z) = \begin{bmatrix} 1 & 0 \end{bmatrix} \tilde{x}(z)$$

NPTEL

Small-Signal Transfer Functions

$$\tilde{x}_{n+1} = A_{\text{eq}} \tilde{x}_n + B_{\text{eq}} \tilde{d}$$

$$\tilde{v}_o[n] = C_{\text{eq}} \tilde{x}_n$$

$$\frac{\tilde{x}(z)}{\tilde{d}(z)} = (zI - A_{\text{eq}})^{-1} B_{\text{eq}}$$

$$\tilde{v}_o(z) = C_{\text{eq}} \tilde{x}(z)$$

$$\tilde{x}(z) = (zI - A_{\text{eq}})^{-1} B_{\text{eq}} \tilde{d}(z)$$

$$\frac{\tilde{i}_L(z)}{\tilde{d}(z)} = G_{ic}(z)$$

$$\frac{\tilde{v}_o(z)}{\tilde{d}(z)} = G_{vd}(z)$$

$$\Rightarrow G_{vd}(z) = \frac{\tilde{v}_o(z)}{\tilde{d}(z)} = C_{\text{eq}} (zI - A_{\text{eq}})^{-1} B_{\text{eq}}$$

Control-to-output
transfer function



Digital Voltage Mode Control

$$\tilde{x}_{n+1} = A_{eq} \tilde{x}_n + B_{eq} \tilde{d}$$

$$\tilde{v}_o[n] = C_{eq} \tilde{x}_n$$

$$\tilde{d} = \frac{\tilde{v}_m}{m_c T} = F_m \tilde{v}_m$$
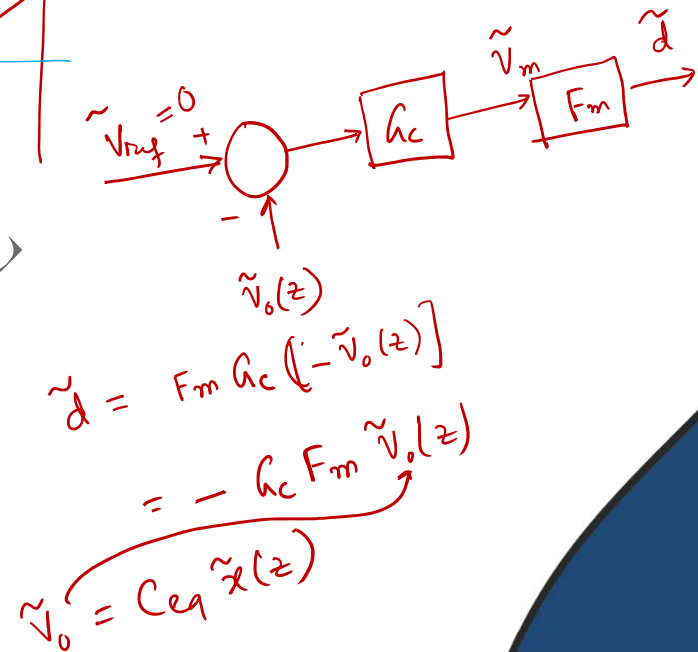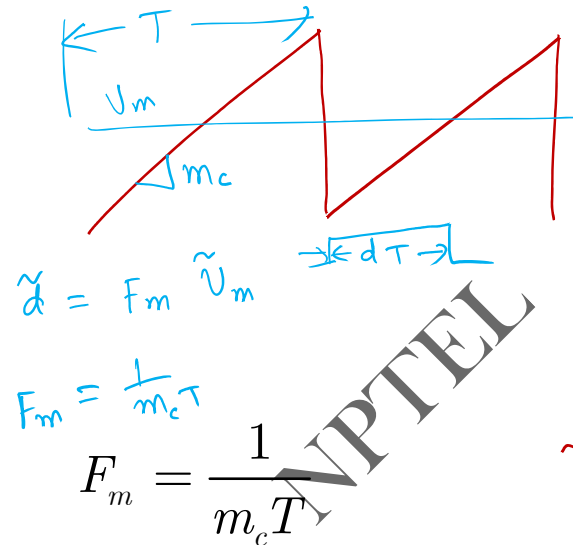
$$\tilde{d} = F_m \tilde{v}_m = -G_c F_m \tilde{v}_o = -G_c F_m C_{eq} \tilde{x}_n$$



Digital Voltage Mode Control

$$\tilde{x}_{n+1} = A_{eq} \tilde{x}_n + B_{eq} \tilde{d} \quad \text{and} \quad \tilde{v}_o[n] = C_{eq} \tilde{x}_n$$

$$\tilde{d} = F_m \tilde{v}_m = -G_c F_m \tilde{v}_o = -G_c F_m C_{eq} \tilde{x}_n$$

Apply Z-transformation

$$zI \times \tilde{x}_n(z) = A_{eq} \tilde{x}_n(z) - G_c F_m B_{eq} C_{eq} \tilde{x}_n(z)$$

$$\left| zI_{2 \times 2} - A_{eq} + G_c F_m B_{eq} C_{eq} \right| = 0$$

characteristic equation

$$\begin{aligned} \tilde{x}_{n+1} &= A_{eq} \tilde{x}_n + B_{eq} \tilde{d} \\ zI \times \tilde{x}(z) &= A_{eq} \tilde{x}(z) + B_{eq} \tilde{d}(z) \\ \tilde{d}(z) &= -G_c F_m C_{eq} \tilde{x}(z) \\ zI \times \tilde{x}(z) &= [A_{eq} - G_c F_m C_{eq}] \tilde{x}(z) \end{aligned}$$

$$(zI - A_{eq} + G_c F_m C_{eq}) \tilde{x}(z) = 0$$


Digital VMC – Loop Transfer Function

$$K_{\text{loop}}(z) = F_m G_c G_{\text{vd}}$$

where $F_m = \frac{1}{m_c T}$

$$G_c = K_p + \frac{K_i}{1 - z^{-1}} \quad (\text{PI Controller})$$
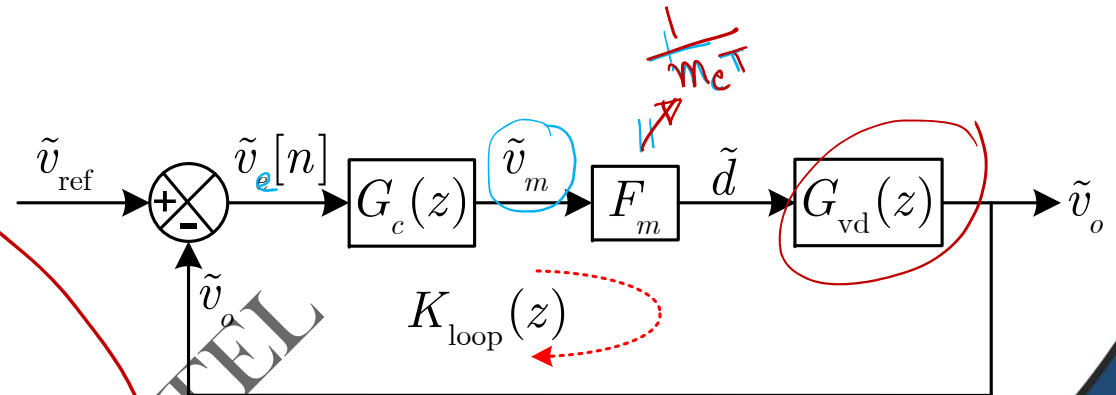
$$G_{\text{vd}}(z) = C_{\text{eq}} (zI - A_{\text{eq}})^{-1} B_{\text{eq}}$$



Digital PID controller

$$G_c(z) = K_p + K_i \frac{1}{1 - z^{-1}} + K_d (1 - z^{-1})$$

Mixed Signal Peak Current Mode Control

$$\tilde{x}_{n+1} = A_{eq} \tilde{x}_n + B_{eq} \tilde{d}$$

$$\tilde{v}_o[n] = C_{eq} \tilde{x}_n$$

$$\tilde{d} = \frac{(\tilde{i}_{ref} - \tilde{i}_L)}{m_1 T} = F_m \times (\tilde{i}_{ref} - \tilde{i}_L)$$


$$\tilde{i}_{ref}[n] = K_p (v_{ref} - v_o[n]) + u_i[n]$$

$$u_i[n] = K_i (v_{ref} - v_o[n]) + u_i[n-1]$$

NPTEL


$$F_m = \frac{1}{m_1 T}$$
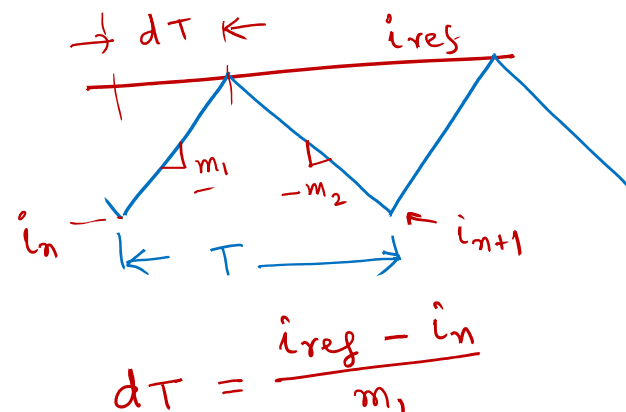
$$\frac{\tilde{i}_{ref}(z)}{\tilde{v}_e(z)} = G_c(z) = K_p + \frac{K_i}{1-z^{-1}}$$



Mixed Signal Peak Current Mode Control
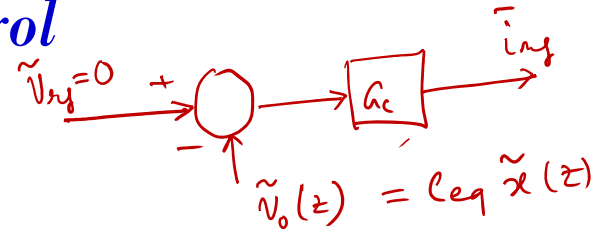
$$\tilde{x}_{n+1} = A_{\text{eq}} \tilde{x}_n + B_{\text{eq}} \tilde{d} \quad \text{and} \quad \tilde{v}_o[n] = C_{\text{eq}} \tilde{x}_n$$



Perturb and apply Z-transformation

$$\tilde{i}_{\text{ref}}(z) = -G_c(z) \tilde{v}_o(z)$$

$$\tilde{i}_{\text{ref}}(z) = -G_c(z) C_{\text{eq}} \tilde{x}(z)$$

$$G_c(z) = K_p + \frac{K_i}{1 - z^{-1}}$$

NPTEL

Mixed Signal Peak Current Mode Control

$$\tilde{x}_{n+1} = A_{eq} \tilde{x}_n + B_{eq} \tilde{d}$$

$$= A_{eq} \tilde{x}_n + B_{eq} F_m (\tilde{i}_{ref} - \tilde{i}_L)$$

$$\tilde{i}_{ref}(z) = -G_c(z) C_{eq} \tilde{x}(z)$$

$$\tilde{i}_L = [1 \ 0] \tilde{x}$$

$$\tilde{d} = F_m (\tilde{i}_{ref} - \tilde{i}_L)$$

$$\tilde{x}_{n+1} = A_{eq} \tilde{x}_n + B_{eq} \tilde{d}$$

$$\tilde{d} = F_m (\tilde{i}_{ref} - \tilde{i}_L)$$

$$\tilde{i}_L = [1 \ 0] \tilde{x}_n$$

$$\tilde{i}_{ref}(z) = -G_c C_{eq} \tilde{x}(z)$$

$$zI \tilde{x}(z) = A_{eq} \tilde{x}(z) + B_{eq} F_m [\tilde{i}_{ref}(z) - \tilde{i}_L(z)]$$

Mixed Signal Peak Current Mode Control

Apply Z-transformation

$$zI \times \tilde{x}_n(z) = A_{eq} \tilde{x}_n(z) - F_m G_c B_{eq} C_{eq} \tilde{x}_n(z) - B_{eq} F_m [1 \ 0] \tilde{x}_n(z)$$

$$\Rightarrow \left| zI_{2 \times 2} - A_{eq} + F_m B_{eq} [1 \ 0] + F_m G_c B_{eq} C_{eq} \right| = 0$$

Mixed Signal Peak CMC Loop Transfer Function

$$\tilde{d} = F_m (\hat{i}_m - \tilde{i}_L)$$


$$K_{\text{loop}}(z) = \frac{F_m G_c G_{\text{vd}}}{1 + F_m G_{\text{id}}}$$

where $F_m = \frac{1}{m_1 T}$

$$G_c = K_p + \frac{K_i}{1 - z^{-1}} \quad (\text{PI Controller})$$


$$G_{\text{vd}}(z) = C_{\text{eq}} (zI - A_{\text{eq}})^{-1} B_{\text{eq}}$$
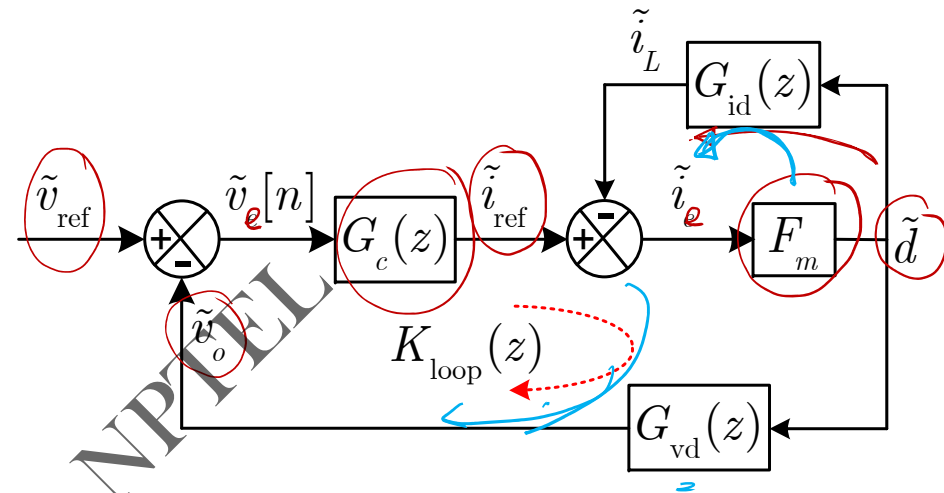
$$G_{\text{id}}(z) = [1 \ 0] (zI - A_{\text{eq}})^{-1} B_{\text{eq}}$$



CONCLUSION

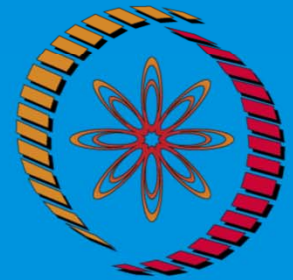- Step-by-step derivations of various discrete-time transfer functions
- Discrete-time control-to-current and control-to-output TFs
- Loop transfer function under digital voltage mode control
- Loop transfer function under digital current mode control



**THANK
YOU !**