



NPTEL ONLINE CERTIFICATION COURSES

DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING

Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR

Module 01: Introduction to Digital Control in SMPCs


Lecture 06: Recap of Feedback and Feedforward Control Methods in SMPCs



CONCEPTS COVERED

- Overview of (analog) feedback and feedforward control
- Primary objectives using feedback and feedforward control
- Recap of analog voltage mode control – example of single-loop control
- Recap of analog current mode control – example of two-loop control
- Recap of input voltage and load current feedforward actions

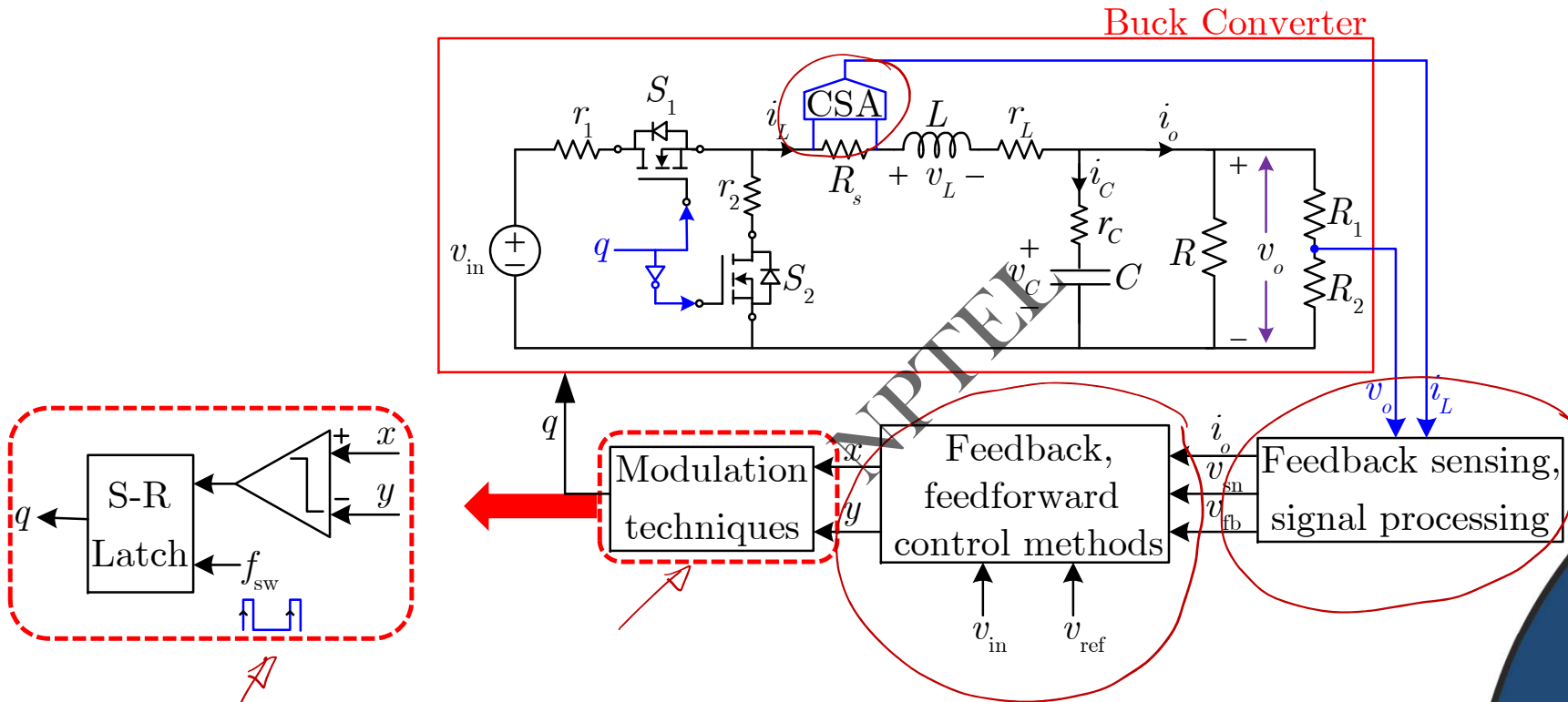
Overview of Feedback/Feedforward Control Methods



S. Kapat & P. Krein, "A Tutorial and Review Discussions ...", *IEEE Open J. Power Electronics*

Role of Feedback/Feedforward Control

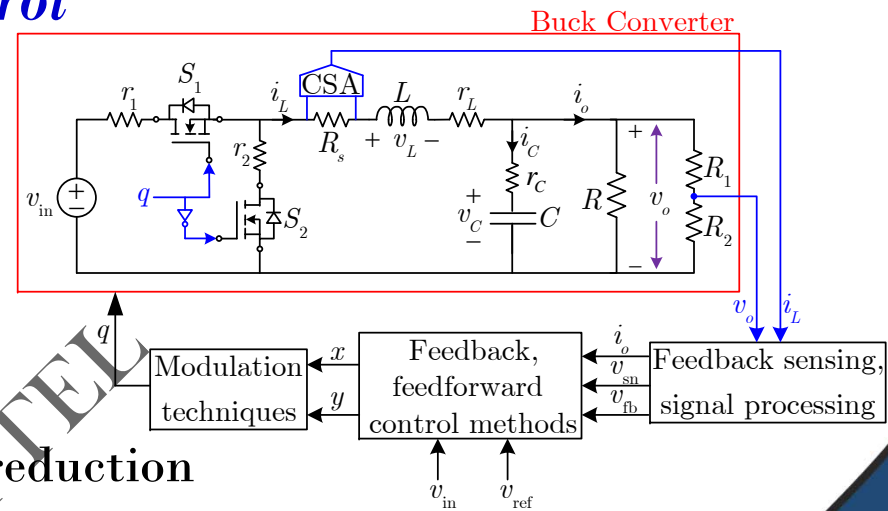- Output voltage regulation
- Fast load transient requirements
- Protection using current limit
- Input supply disturbance rejection, EMI reduction
- Nearly flat efficiency curve over a wide load current range
- Consideration: fast scale and large-signal stability
- Constraint: variations in on/off-time as well as frequency




Feedback/Feedforward Control

- Voltage mode control with and without input voltage feedforward
- Current mode control with and without DC droop control (or AVP)
- State feedback control- linear or nonlinear
- Fixed and/or variable frequency control
- Multimode control for wide load range

Interdependency of modulation and control!!


Single Loop Feedback Control in SMPC

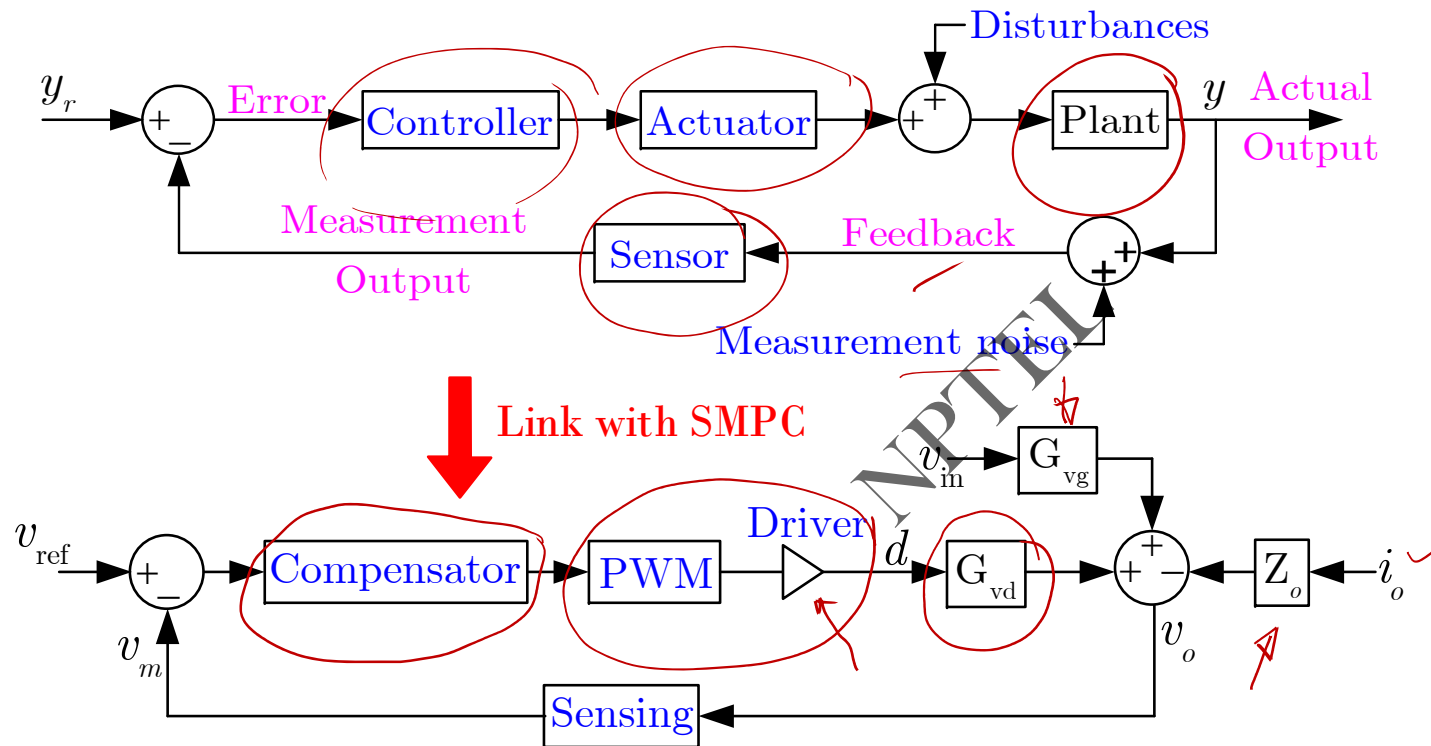

[For details, refer to Lecture~15, NPTEL “Control and Tuning Methods ...” course ([link](#))


Basic Two Loop Output Feedback Control

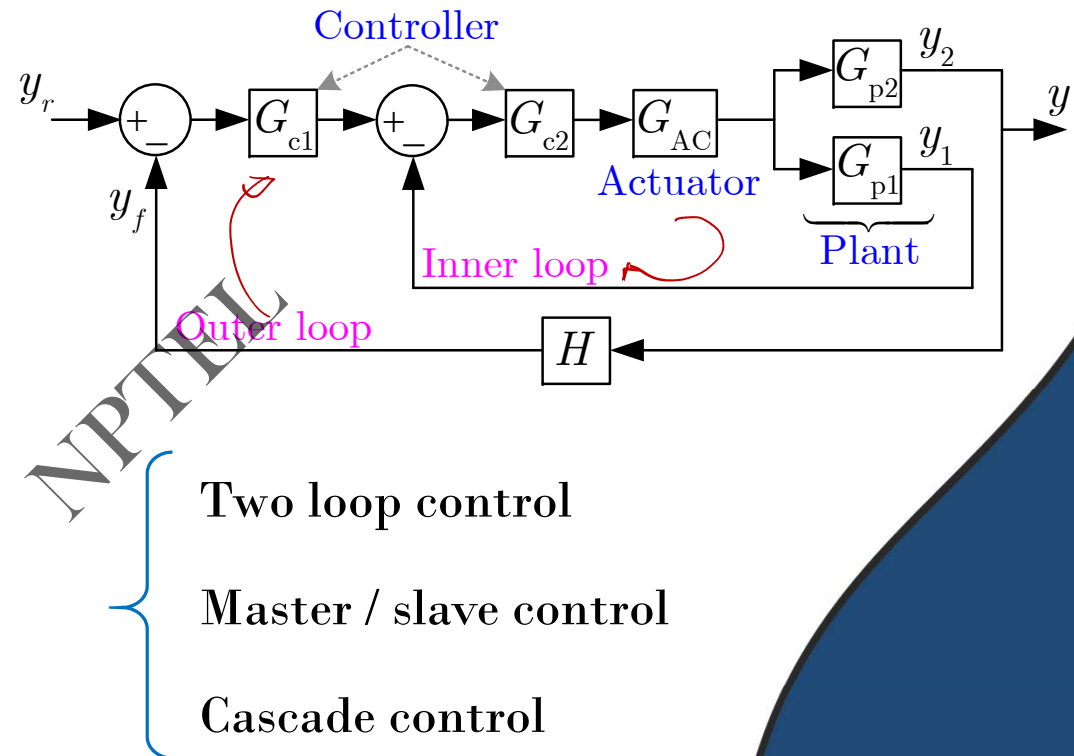- Outer loop → generally (output) voltage loop
- Inner loop:
 - Inductor current
 - Capacitor current
 - Derivative of output voltage
 - Ripple output voltage




[For details, refer to Lecture~15, NPTEL “Control and Tuning Methods ...” course ([link](#))

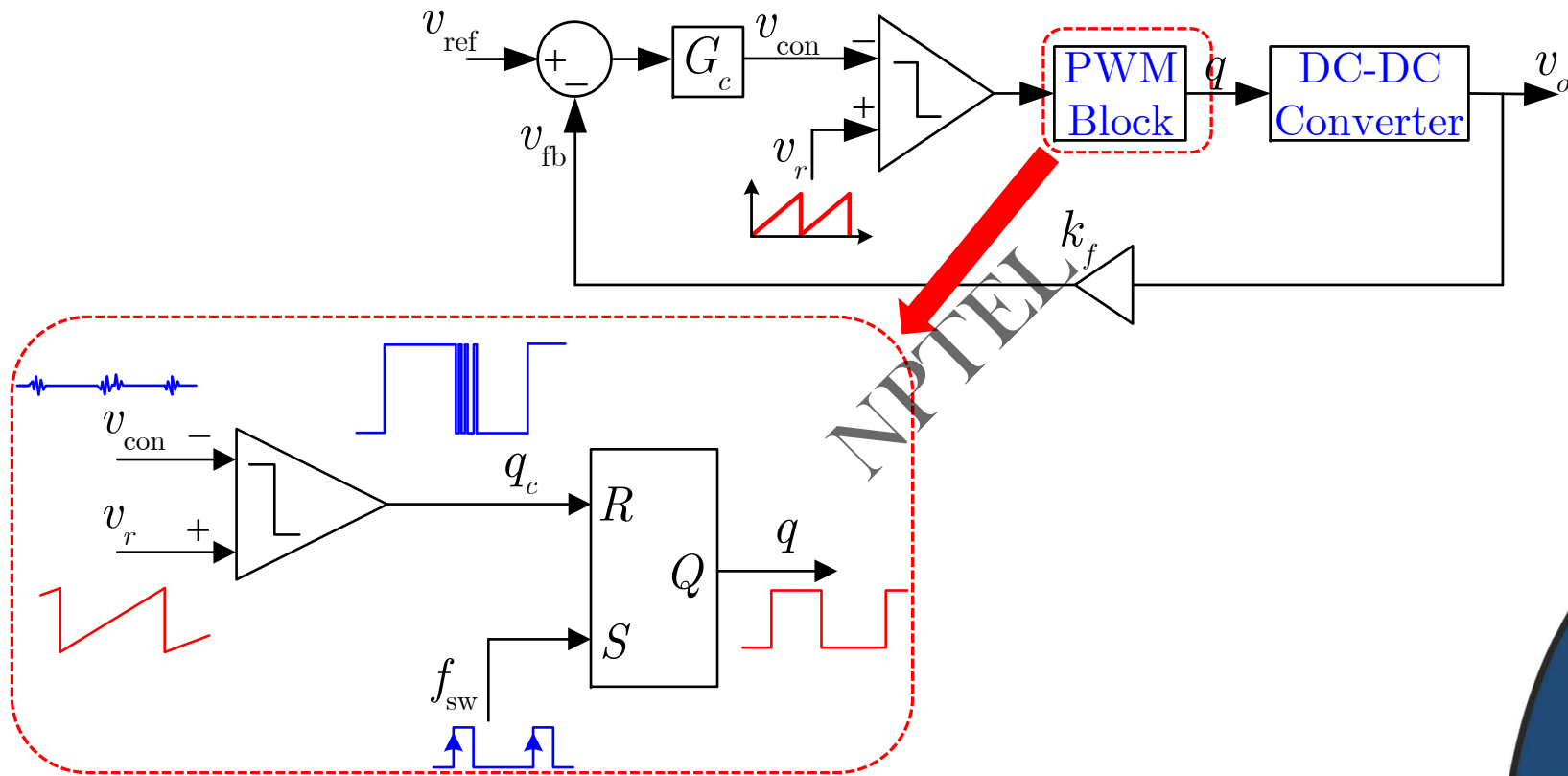Single Feedback Loop : Voltage Mode Control




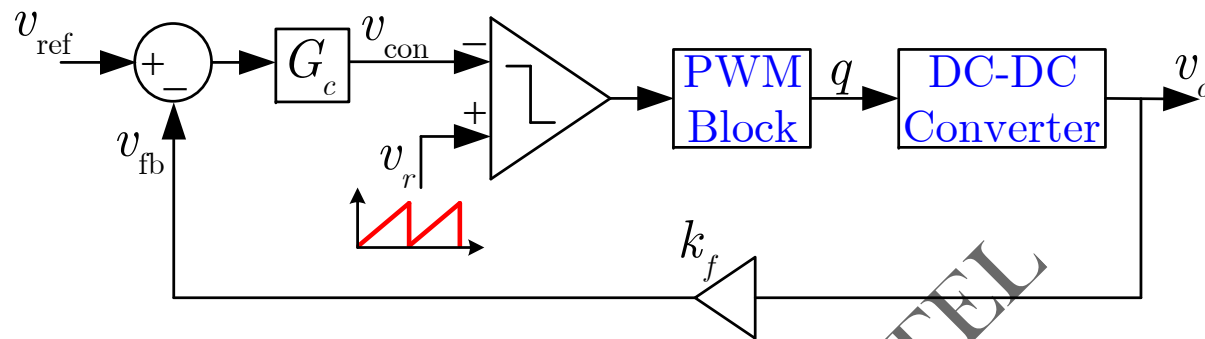Limitations of Single Loop Voltage Mode Control



- No control over current !!!
- Compensation sensitive to operating conditions
- Fault protection and start-up logics separately needed
- Difficult to optimize transient and start-up performance

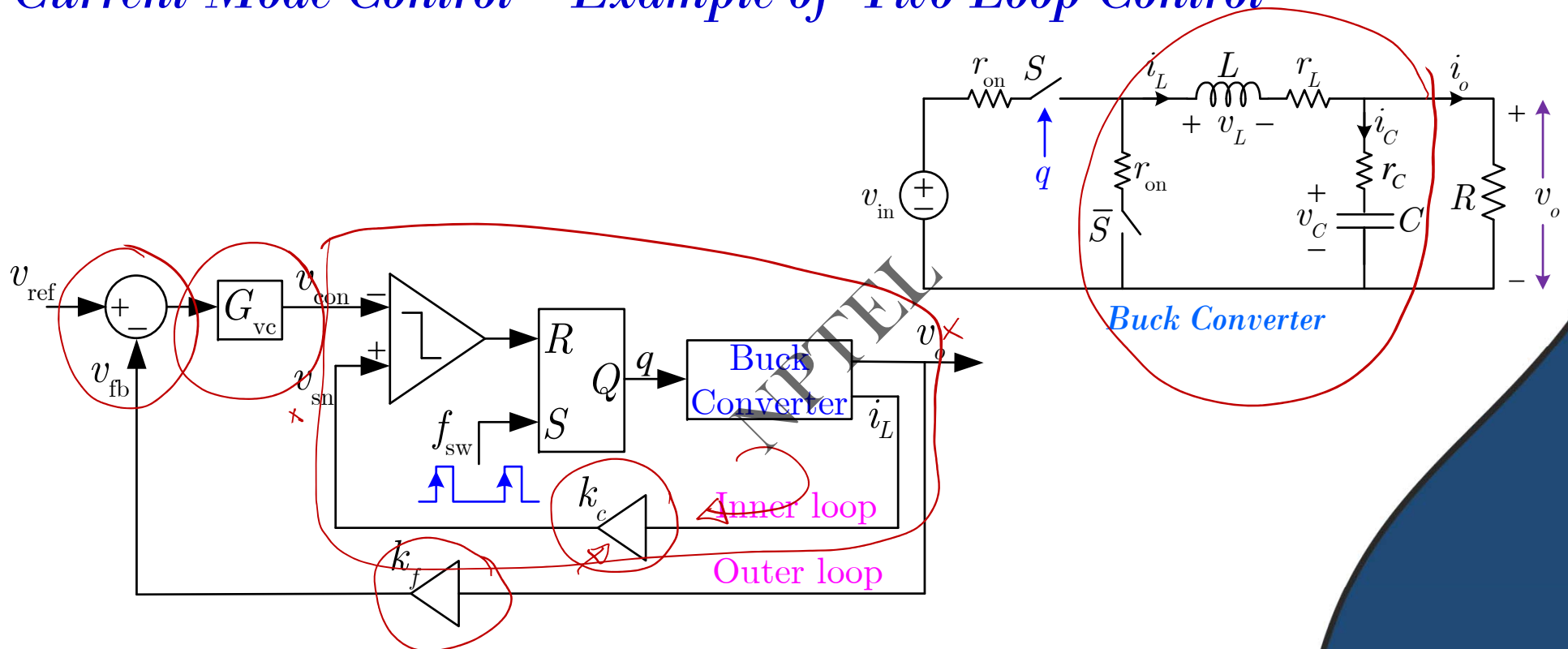Current Mode Control – Example of Two Loop Control



[For details, refer to Lecture~15, NPTEL “Control and Tuning Methods ...” course ([link](#))

Advantages of Two Loop Current Mode Control

- Possibility of reduced-order system dynamics using time-scale separation
- Simplified controller design with improved robustness
- Higher bandwidth can be achieved without compromising phase margin
- But, sensor requirement increases in current based implementation
- Existence of sub-harmonic instability over wide duty ratio range


Input Voltage Feedforward in Direct Duty Control in a Buck Converter

$$v_o = dv_{in} = \underbrace{\left(\frac{1}{V_U} \right)}_{F_m} \times v_{con} \times v_{in}$$

(modulator gain)


- Objective is to make Δv_o even without changing v_{con}
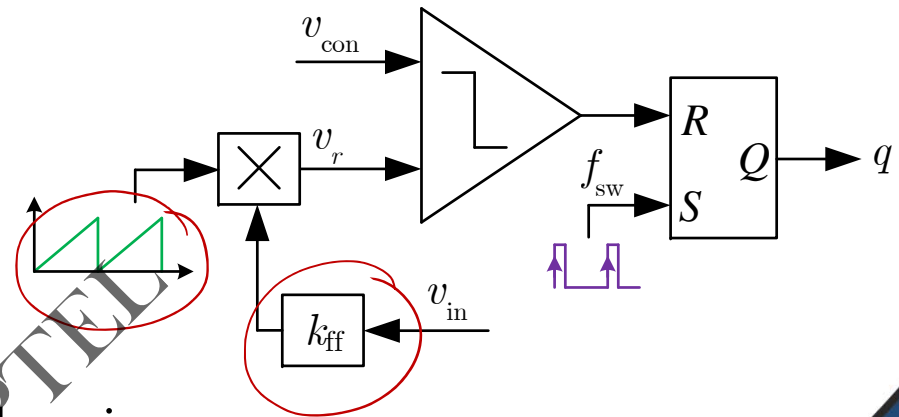
$$\text{If } V_U = k_{ff} v_{in} \quad v_o = \frac{1}{k_{ff} v_{in}} \times v_{in} \times v_{con} = \frac{v_{con}}{k_{ff}} \rightarrow \text{Insensitive to input voltage variation}$$




[For details, refer to Lecture~14, NPTEL “Control and Tuning Methods ...” course ([link](#))

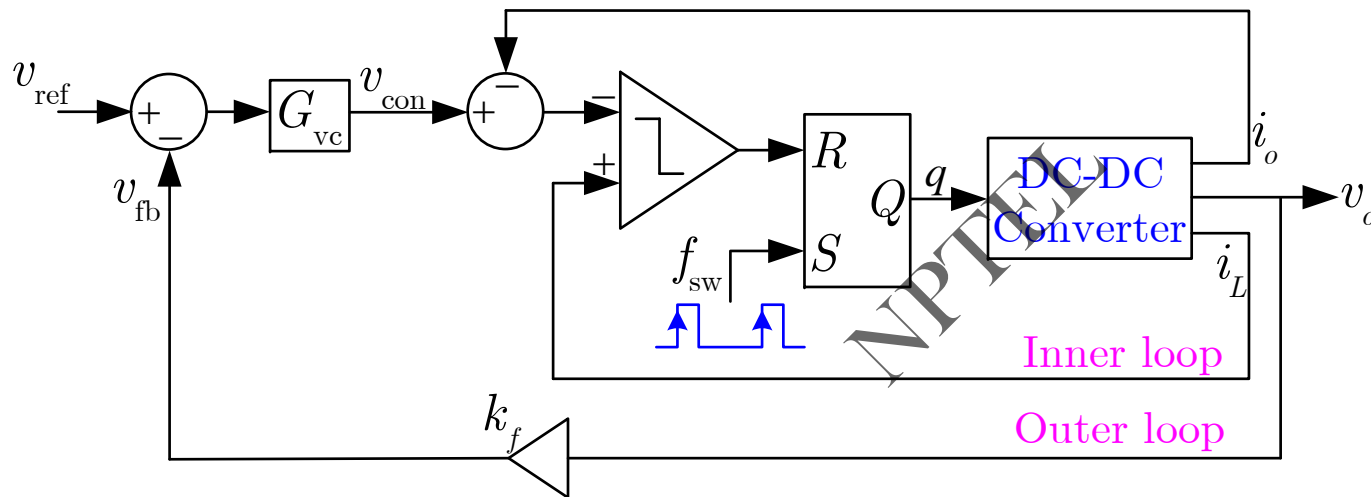Load Current Feedforward in Current Mode Control



[For details, refer to Lecture~17, NPTEL “Control and Tuning Methods ...” course ([link](#))

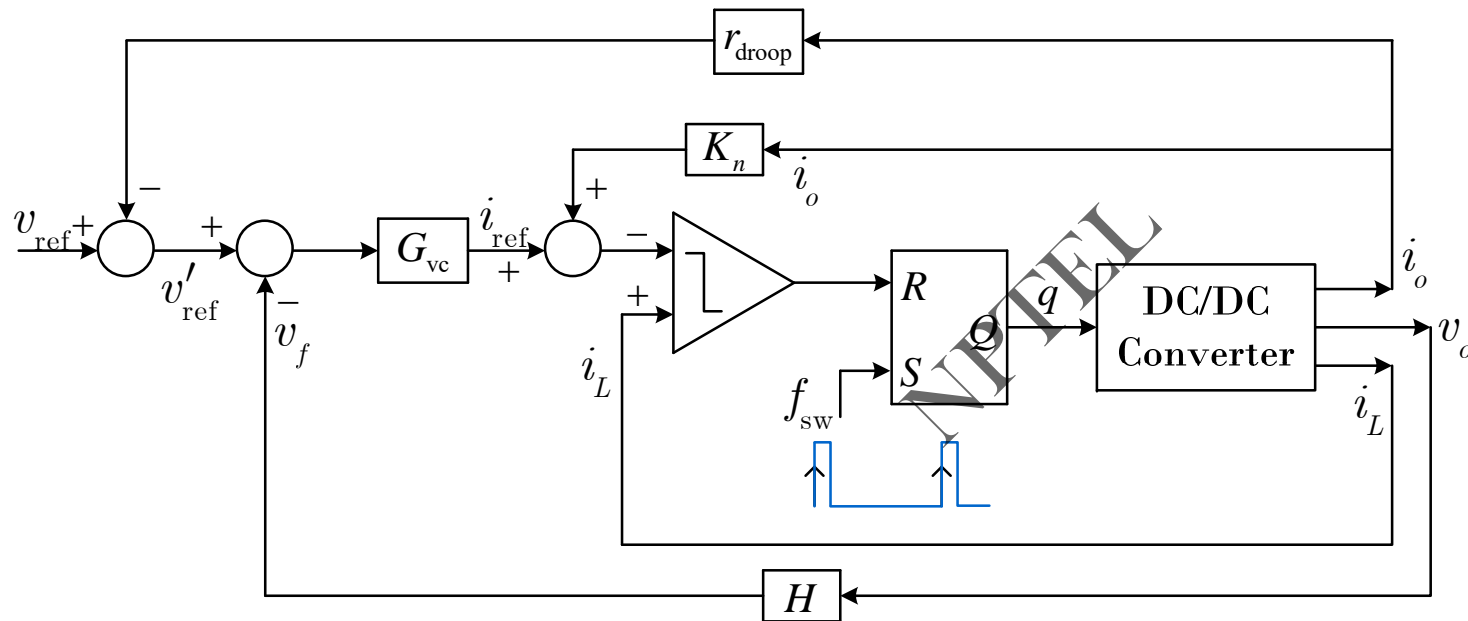Load Current Feedforward with Droop – Adaptive Voltage Positioning



[For details, refer to Lecture~17, NPTEL “Control and Tuning Methods ...” course ([link](#))


Questions

- How to digitize single-loop and multi-loop analog feedback control?
- What will design flexibilities using various modulation techniques?
- How many ADC and/or DAC needed?
- How to incorporate feedback forward actions in digital control?

Objectives of this course – coming soon!!

CONCLUSION

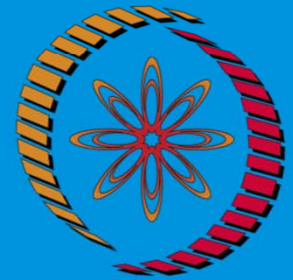- Primary objectives using feedback and feedforward control - discussed
- Recap of analog voltage mode control – example of single-loop control
- Recap of analog current mode control – example of two-loop control
- Recap of input voltage and load current feedforward actions



**THANK
YOU !**