

NPTEL ONLINE CERTIFICATION COURSES

DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING

Dr. Santanu Kapat Electrical Engineering Department, IIT KHARAGPUR

Module 01: Introduction to Digital Control in SMPCs

Lecture 05: Introducing Basic Digitization in Power Electronic Converters






CONCEPTS COVERED


- Basics of feedback and feedforward control
- Few basic requirements with PMBus
- Basic level of digitization using housekeeping
- Possibility of further digitization

Control of DC-DC Converters

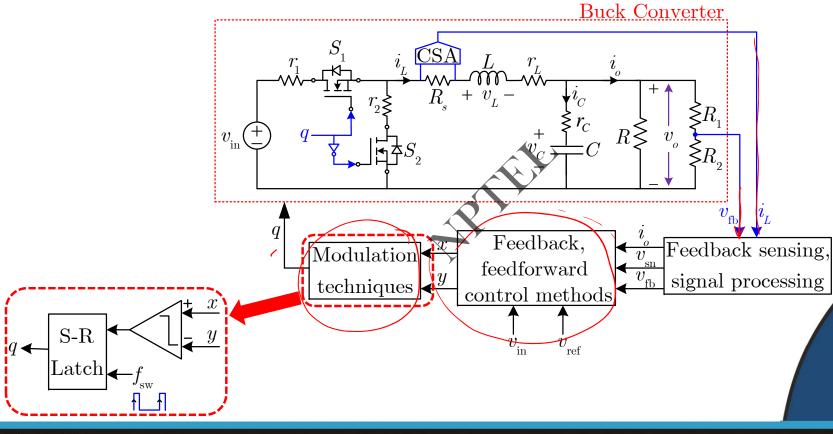



Buck Converter Voltage Mode Control

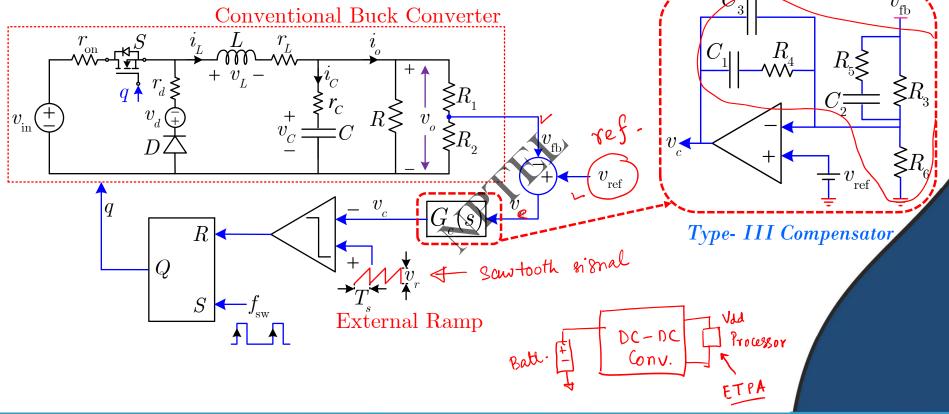




Basic Digitization Process: Buck Converter VMC

- Requirements
 - 1. v_{ref} programming
 - 2. Adaptive Constant-ON time
 - 3. $PMBus^{TM}$






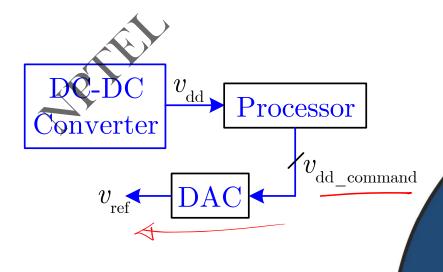- 1. v_{ref} programming
 - o Dynamic adjustment of v_{ref} (maybe needed for DVS)
- How to do that?
- Who provides v_{ref} command?





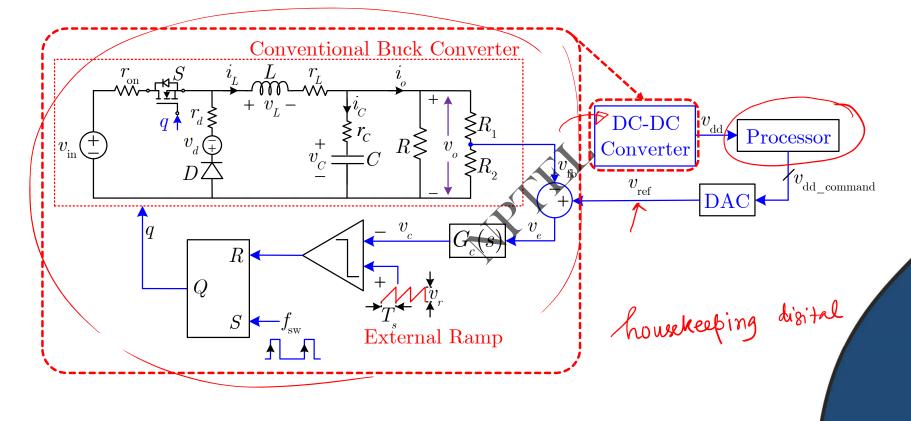




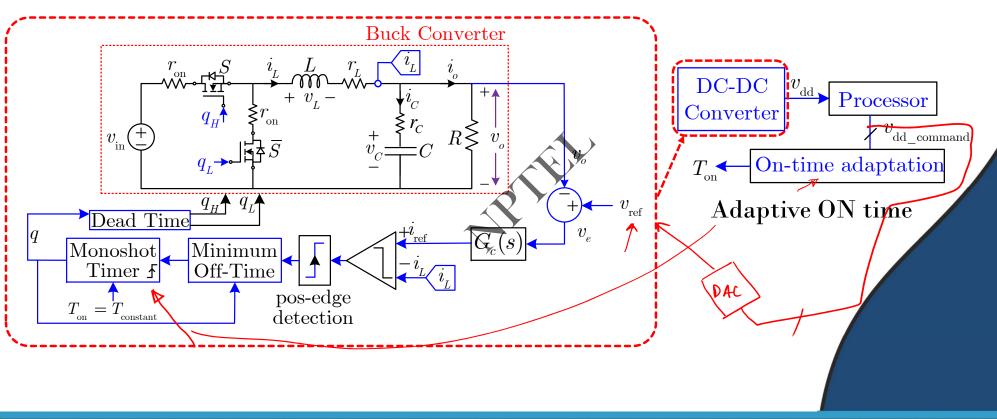- 2. Adaptive Constant-ON time
 - Improvement of light-load efficiency

$$\Delta i_{\!\scriptscriptstyle L} = rac{T_{\!\scriptscriptstyle
m on}}{L} imes \left(V_{\!\scriptscriptstyle
m in} - V_{\!\scriptscriptstyle o}
ight) \qquad \qquad f_{\!\scriptscriptstyle SW} = rac{1}{T_{\!\scriptscriptstyle
m on}} imes V_{\!\scriptscriptstyle
m in} \ ,$$


- lacksquare Inductor ripple is dependent on $V_{
 m in}$
- ${\color{gray} \bullet}$ $T_{\rm on}$ can be changed adaptively to maintain the ripple within the given range








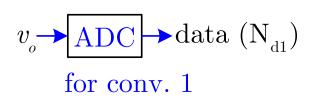
- 3. PMBusTM
- What data is stored?
 - Output voltage information
 - Other information



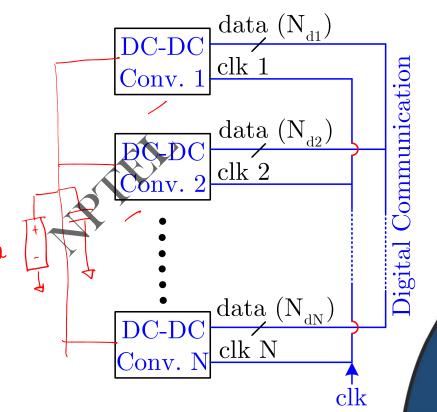




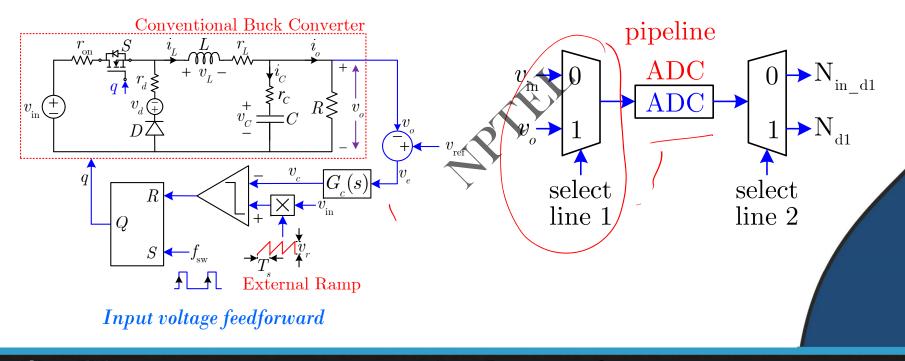 $\blacksquare \quad Input \ voltage \ feedforward \ \& \ PMBus^{^{TM}}$





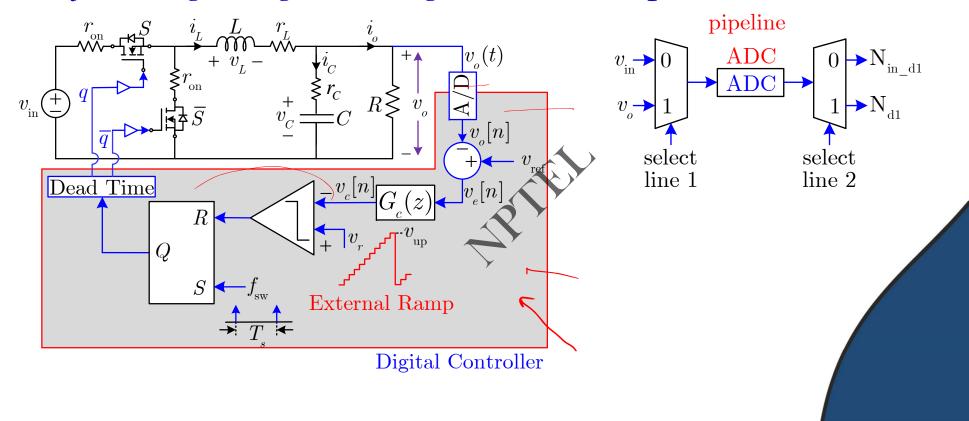Why not Digitizing the Voltage Feedback Loop in VMC





CONCLUSION

- Basics of feedback and feedforward control
- Few basic requirements with PMBus
- Basic level of digitization using housekeeping
- Possibility of further digitization

