



**NPTEL ONLINE CERTIFICATION COURSES**

# **DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING**

**Dr. Santanu Kapat**

**Electrical Engineering Department, IIT KHARAGPUR**

**Module 01: Introduction to Digital Control in SMPCs**

**Lecture 04: Overview of Digital Control Implementation Platforms**




## CONCEPTS COVERED

- Example of CMOS based digital circuit implementation
- Difference between ASIC and LUT based implementation
- Embedded control platforms – ASIC, FPGA, uC
- Digital control platforms in this course
- Why HDL based implementation and FPGA prototyping?

## TWO-input AND Gate – An Example

$$y = AB$$

 




$$y = AB = \overline{\overline{AB}} = \overline{\overline{A} + \overline{B}} = \overline{\overline{A} + \overline{B}}$$

$$y = AB = \overline{\overline{AB}} = \overline{\overline{A} + \overline{B}}$$


$$x \triangleq \overline{\overline{A} + \overline{B}}$$
   
## CMOS Implementation of a TWO-input AND Gate

$$y = AB = \overline{\overline{AB}} = \overline{\overline{A} + \overline{B}} = \overline{\overline{x}}$$


 
## CMOS Implementation of a TWO-input AND Gate




Problems

Fixed hardware

Number of transistor = 6

## Look-up-table (LUT) of a TWO-input Digital Logic

A	B	y
0	0	$y_0$
0	1	$y_1$
1	0	$y_2$
1	1	$y_3$

 

Question :


Flexible hardware

Each  $y_K$  can take either '0' or 1

Total number of possible two-input functions  $2^4 = \underline{16}$


In general =  $2^{2^N}$     N= no of input
 
## LUT based Implementation of a TWO-input Digital Logic



$A$	$B$	$y$
0	0	$y_0$
0	1	$y_1$
1	0	$y_2$
1	1	$y_3$

## CMOS Implementation of a SRAM Cell



 


Total transistor for each SRAM cell = 6

Total transistor for FOUR SRAM cells = 24


   
## CMOS Implementation of a TWO-input Digital MUX



Total transistor = 6 (including inverter)

## *LUT and ASIC Implementation of a TWO-input AND Gate*

*For 2 Input ASIC AND gate*

Total no of transistor = 6 ✓

*For 2 Input LUT based AND gate*


- 4 SRAM cells  $\longrightarrow$  24 transistors
- 2 2-input (input side) MUX  $\longrightarrow$   $(12-2)=10$  transistors
- 1 2-input (input side) MUX  $\longrightarrow$  6 transistors

Total no of transistor = 40 ✓


## *TWO-input AND Gate – Comparing LUT and ASIC Implementation*

Method	Description	Benefits	Limitations
ASIC	6 -Transistors ✓	<u>Hardware</u> optimized, power efficient	Fixed design, high <u>NRE</u> cost, long <u>development time</u>
LUT ↑	40 transistors ✓	<u>Configurable</u> <u>hardware</u> , low NRE cost, short development time ↑	<u>Expensive</u> <u>hardware</u> , power hungry, large <u>component cost</u>

# FPGA – Field Programmable Gate Array

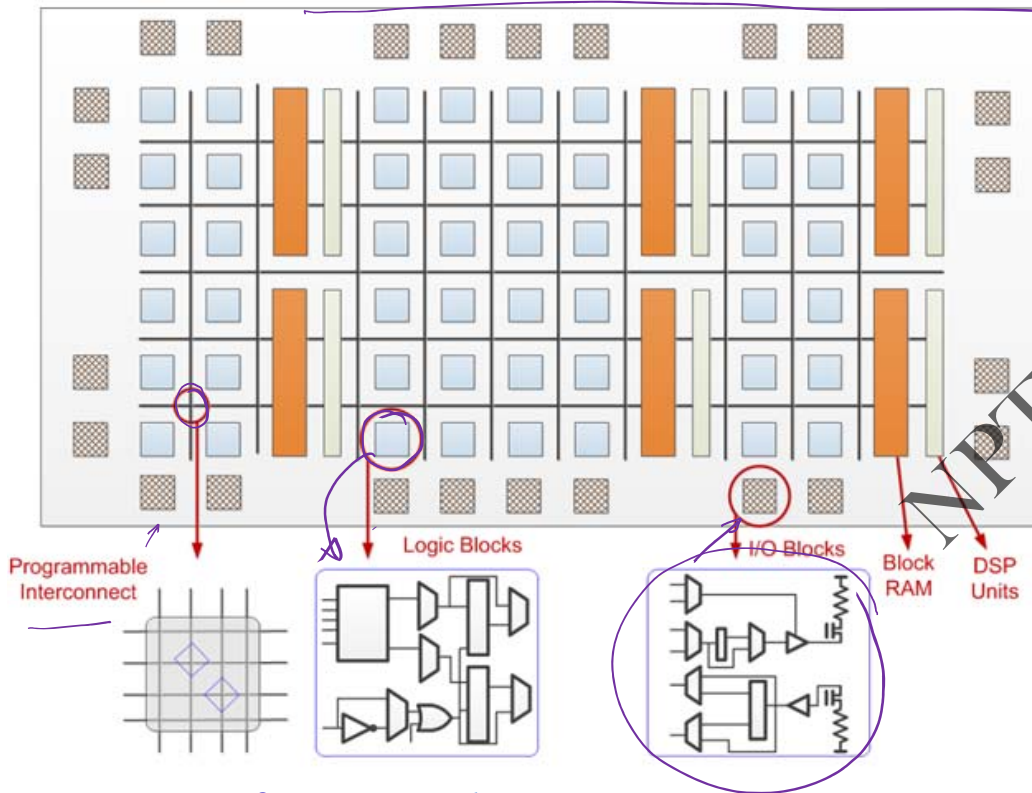

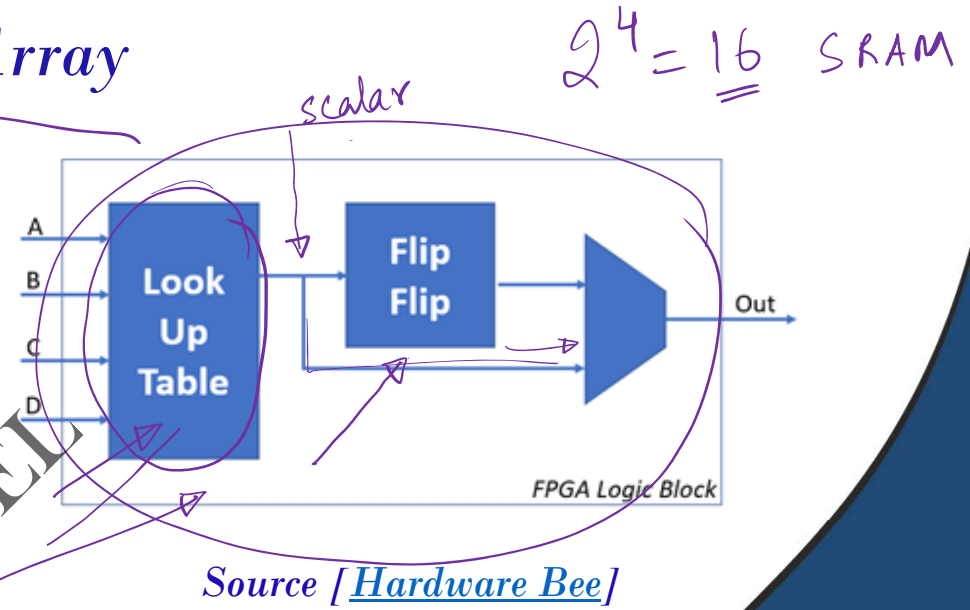Source [[Medium.com](https://medium.com/)]




Source [[Hardware Bee](https://www.hardwarebee.com/)]

CLB

Verilog HDL


## *FPGA Kit for This Course*

 

NPTEL



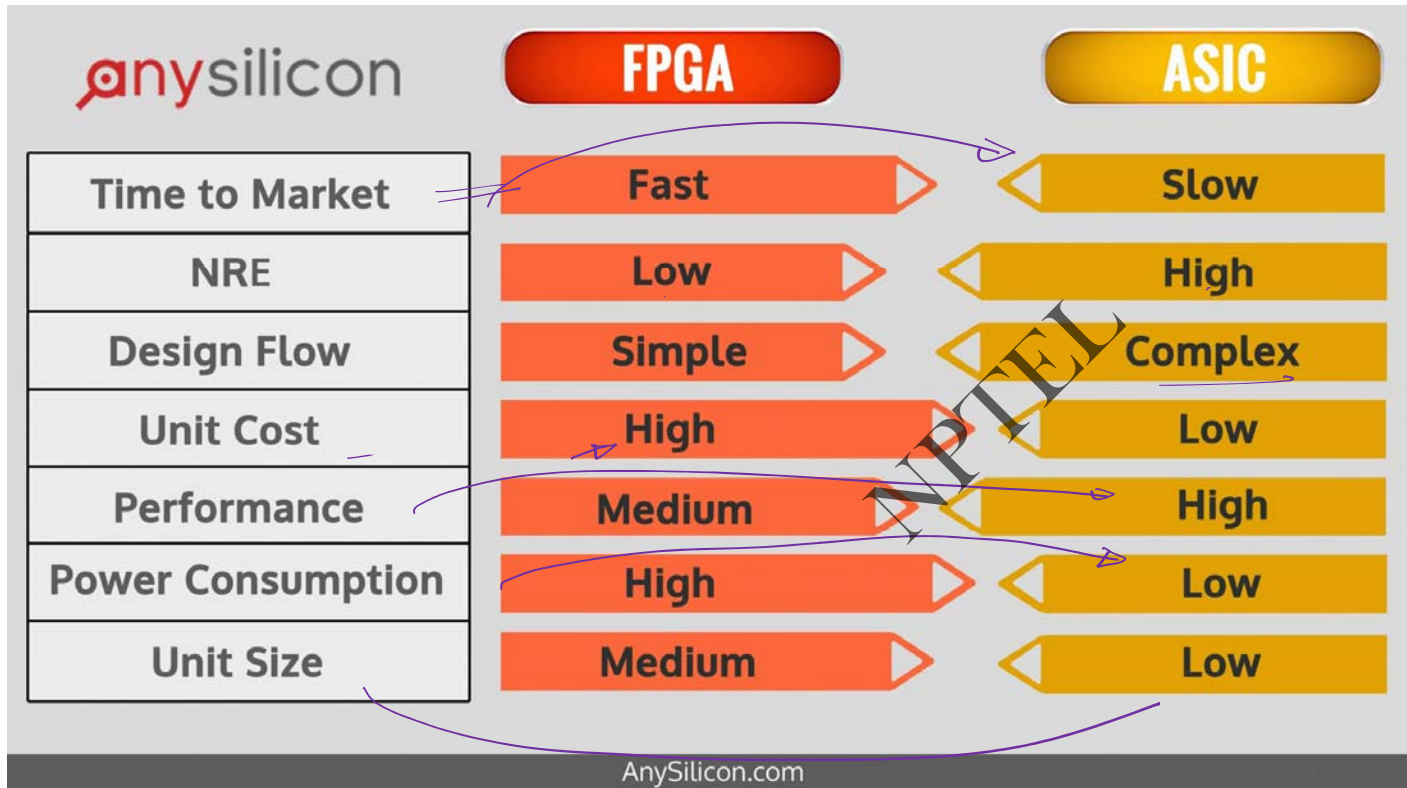


*Xilinx FPGA [[Numato Lab](http://www.numato.com)]*

## FPGA vs ASIC Implementation



Source – [anysilicon.com](http://anysilicon.com)


## FPGA vs CPLD

	CPLD	FPGA
 Flexibility	Low	High
 Price	Low	High
 Security	High	Low
 Speed	High	High
 Capacity	Low	High
 Application	Simple	Complex

Source – [Outsourcetit.today](http://Outsourcetit.today)


 
# FPGA vs Microcontroller vs. ASIC Solutions



Source – [Octopart.com](http://Octopart.com)

Micro	FPGA
Write software.	Design hardware.
Typically executes <u>one instruction at a time</u> .	All parts of your circuit can operate independently.
Fixed maximum clock speed.	Maximum clock speed is dependent on your design.
A handful of I/O pins that can be accessed in small groups (typically eight) at a time.	Many I/O pins that can all be accessed simultaneously.
Usually store programs in nonvolatile (persistent) memory.	RAM based and needs to be programed after power on (the Mojo does this automatically).
Often very power efficient with advanced sleep modes.	Power usage depends on your design but typically requires more than a microcontroller.
Fixed peripherals that limit the devices you can connect.	Can interface with virtually any digital device.

Source – [fpgakey.com](http://fpgakey.com)





## *FPGA and Microcontrollers in This Course*

- Verilog HDL based implementation and  
Xilinx Spartan 6 FPGA prototyping
- Introduction to STM32 microcontroller and  
selected hardware demonstrations
- Introduction to C2000 microcontroller and  
selected hardware demonstrations

## Why Verilog HDL based Implementation?


Hardware descriptive language

Digital pulse width modulator

 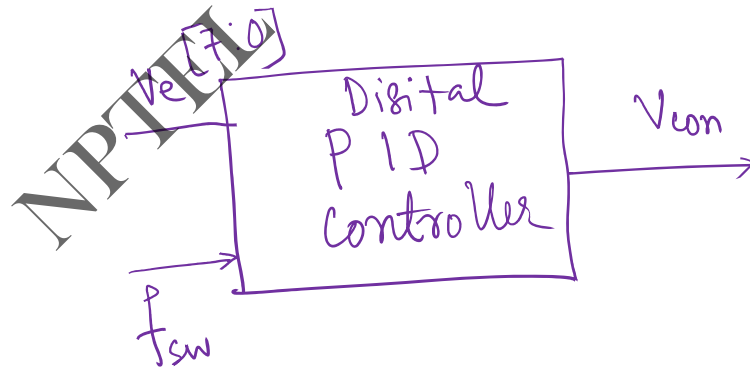

## CONCLUSION

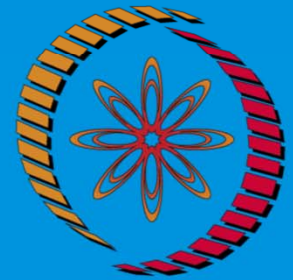- Example of CMOS based digital circuit implementation
- Difference between ASIC and LUT based implementation
- Embedded control platforms – ASIC, FPGA, uC
- Digital control platforms in this course
- Why HDL based implementation and FPGA prototyping?



**THANK  
YOU !**