

#### NPTEL ONLINE CERTIFICATION COURSES

# DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING

Dr. Santanu Kapat Electrical Engineering Department, IIT KHARAGPUR

Module 01: Introduction to Digital Control in SMPCs

Lecture 08: Levels of Digitization in Single-loop Feedback Control in SMPCs







## **CONCEPTS COVERED**

- Recap of analog voltage mode control
- Digitizing single feedback loop
- Sampling and quantization
- Sampling delay and timing diagrams
- Summary of single-loop digital control

#### Analog Voltage Mode Control

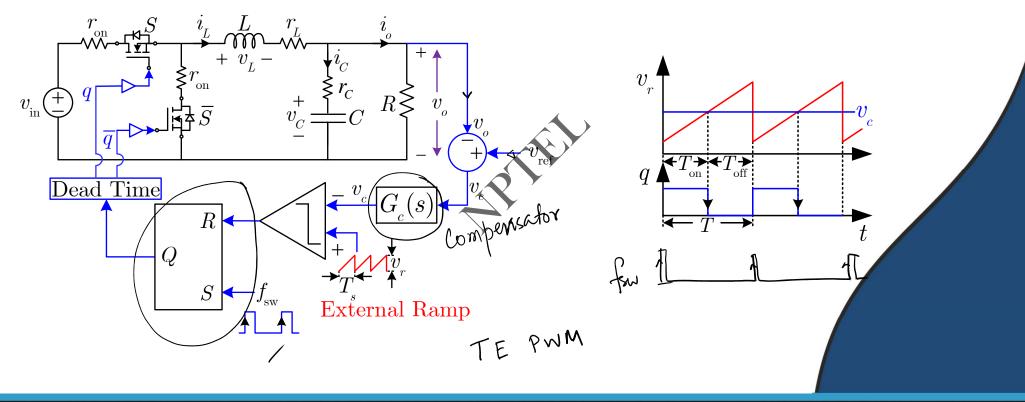




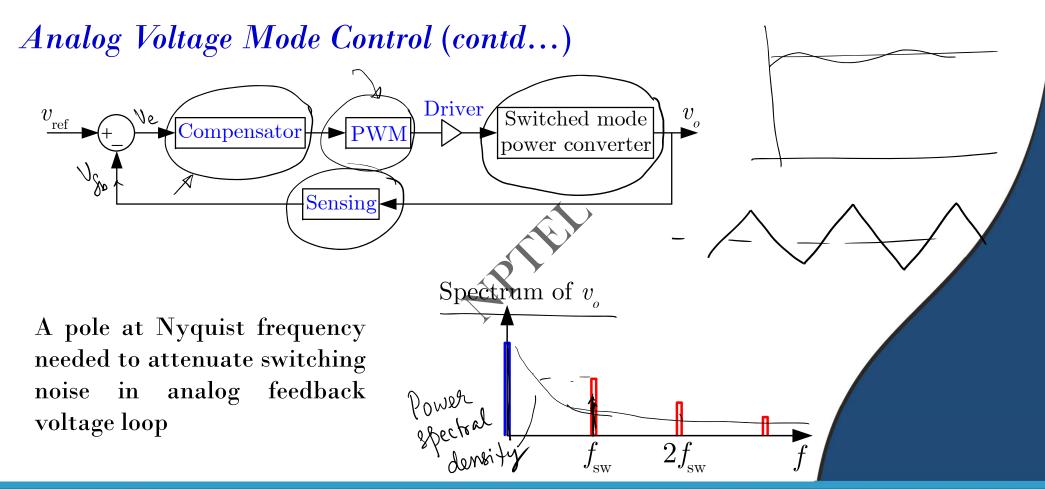





## Closing Digital Loop

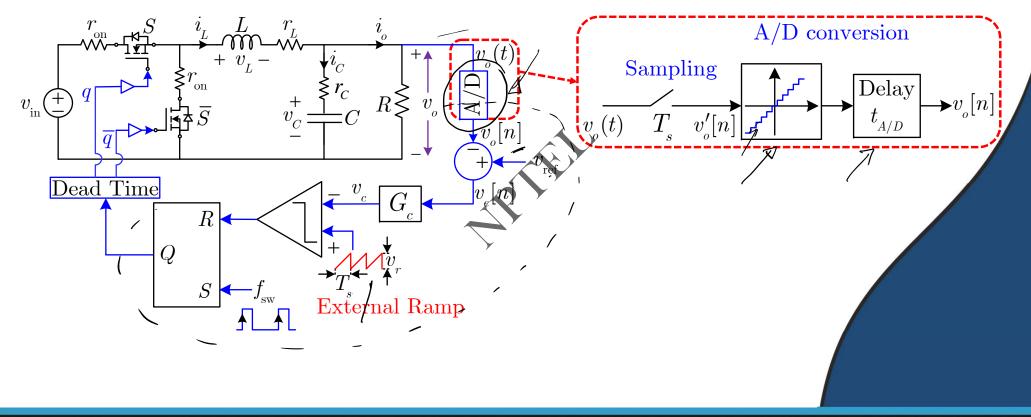




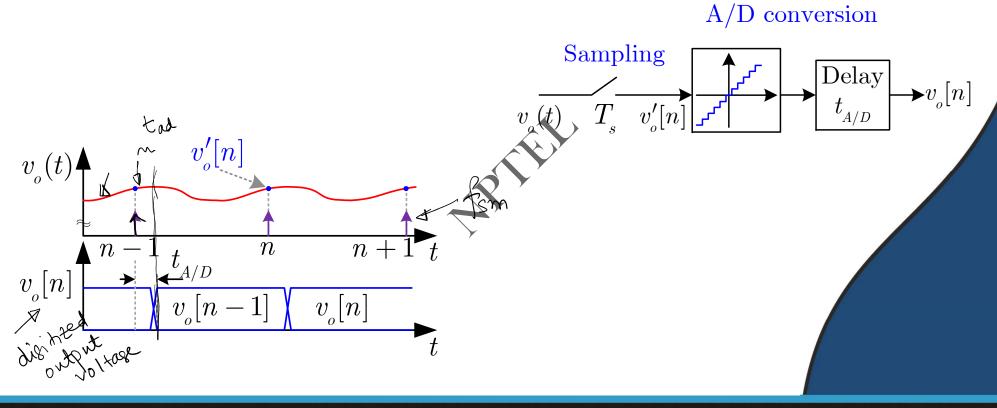



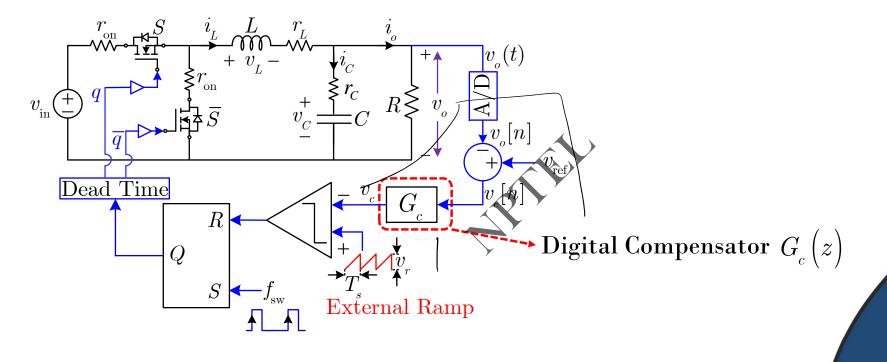




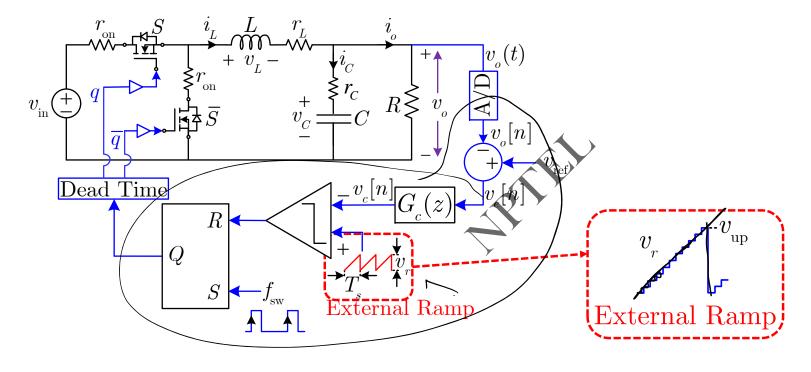






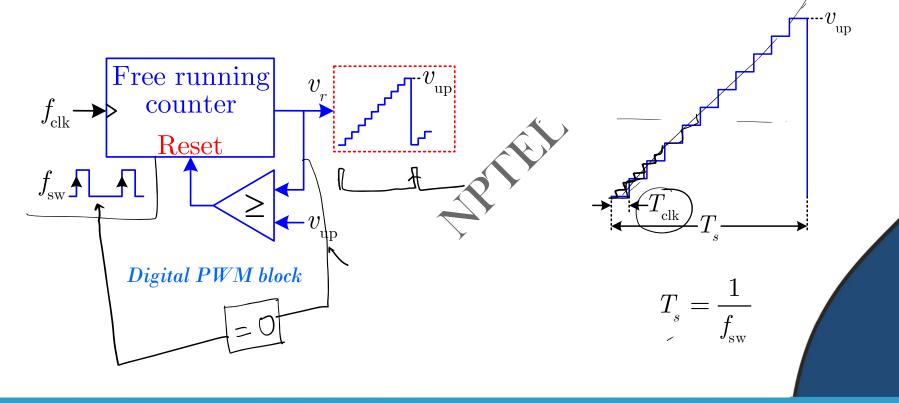



## Digital Voltage Mode Control

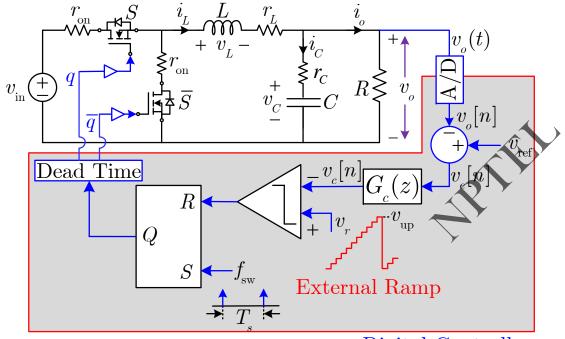



Digital Controller

 $DPWM\ voltage\text{-}mode\ control:\ Buck\ Converter$ 



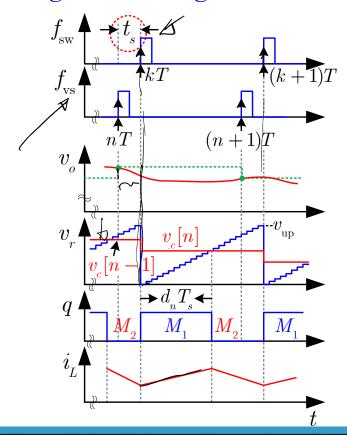
#### Digital Voltage Mode Control (contd...)



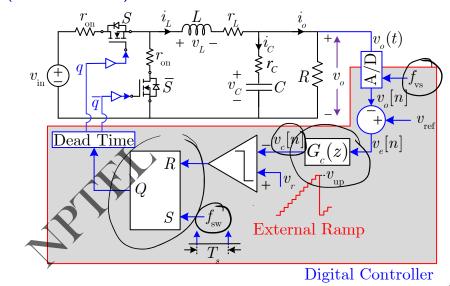

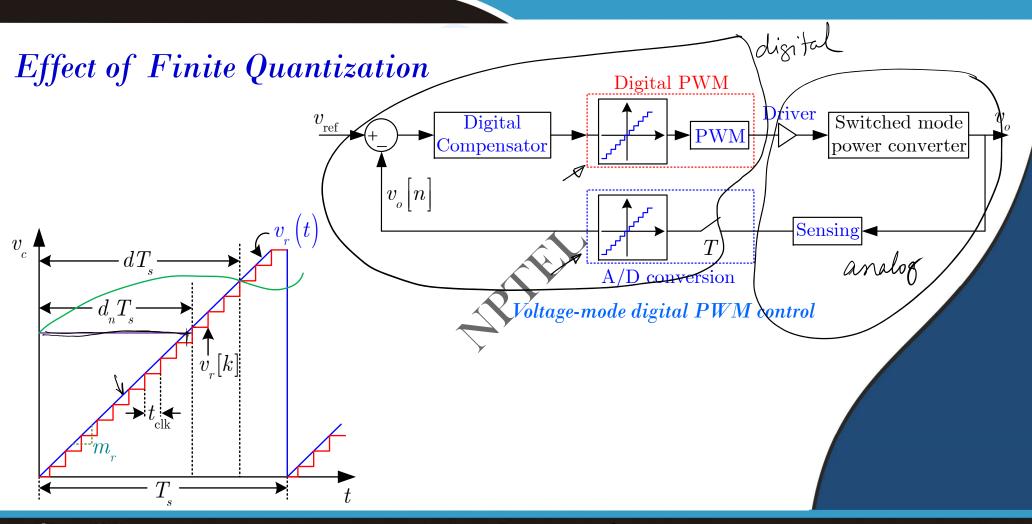
Delay – maybe even larger than switching period!!







Effect of Finite Quantization (contd...)

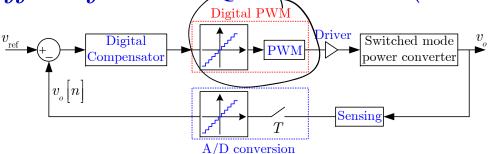


Voltage-mode digital PWM control

If DPWM resolution poor than ADC




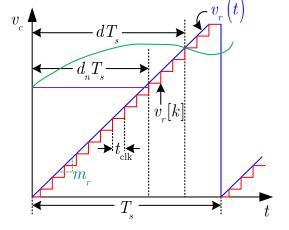- Exact duty ratio may not be obtained
- □ This would eventually take error voltage outside the zero-error-bin






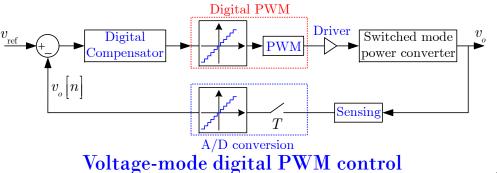
# Effect of Finite Quantization (contd...)





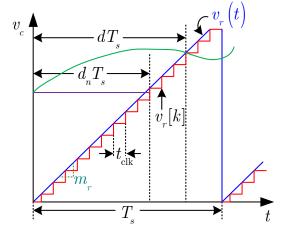



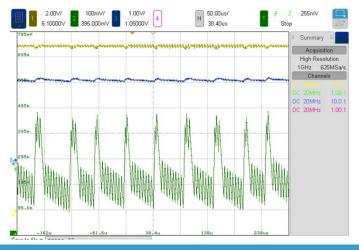

Results in limit cycle oscillation (LCO):

DPWM synchronous buck converter





#### **CONCLUSION**

- Recap of analog voltage mode control
- Digitizing single feedback loop
- Sampling and quantization
- Sampling delay and timing diagrams
- Summary of single-loop digital control

