



**NPTEL ONLINE CERTIFICATION COURSES**

# **DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING**

**Dr. Santanu Kapat**

**Electrical Engineering Department, IIT KHARAGPUR**

**Module 04: Modeling Techniques and Mode Validation using MATLAB**


**Lecture 36: Validation of Discrete-Time Large-Signal Models using MATLAB – Part II**





## CONCEPTS COVERED

- Recall of digital control architectures and MATLAB models
- Steps for simulation using MATLAB detailed switch models and discrete-time large-signal models
- MATLAB codes and step-by-step methods for model validation
- Validation case studies using a Boost Converter

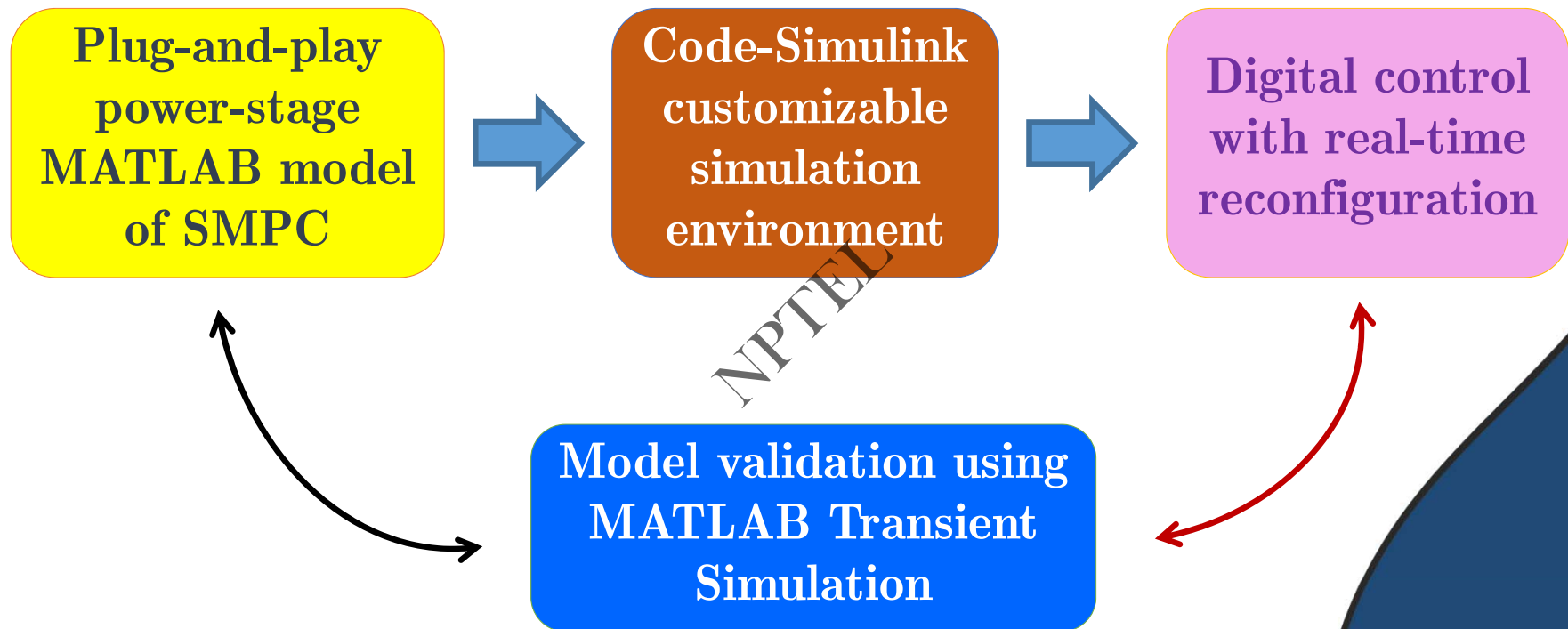
## *Overall Plan for MATLAB based Validation*


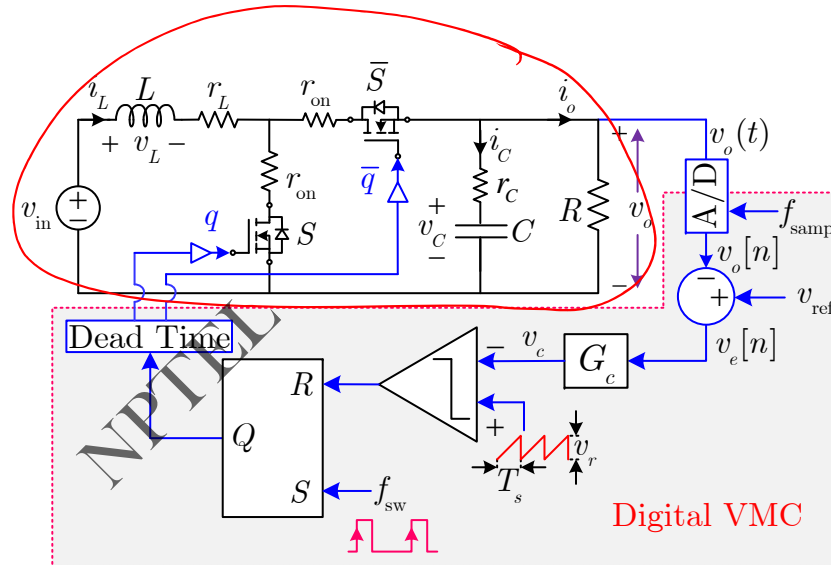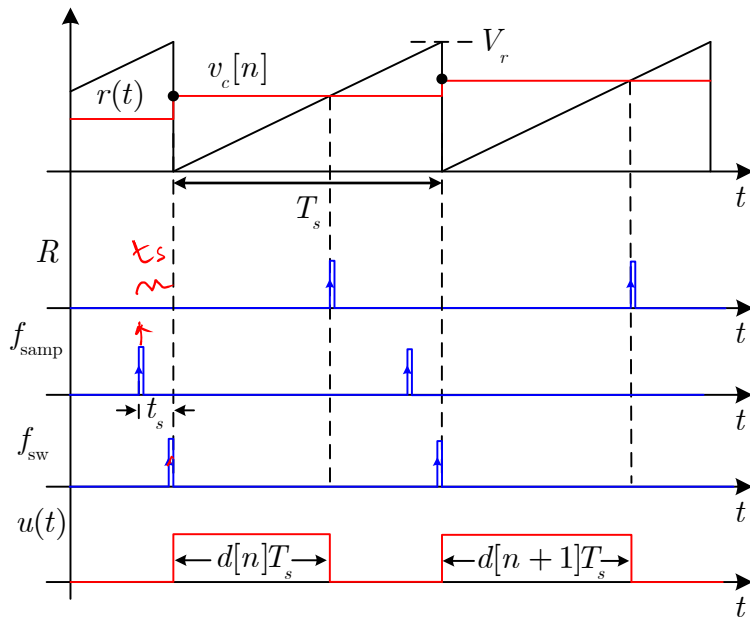
# Digital Voltage Mode Control (DVMMC) of Boost Converter


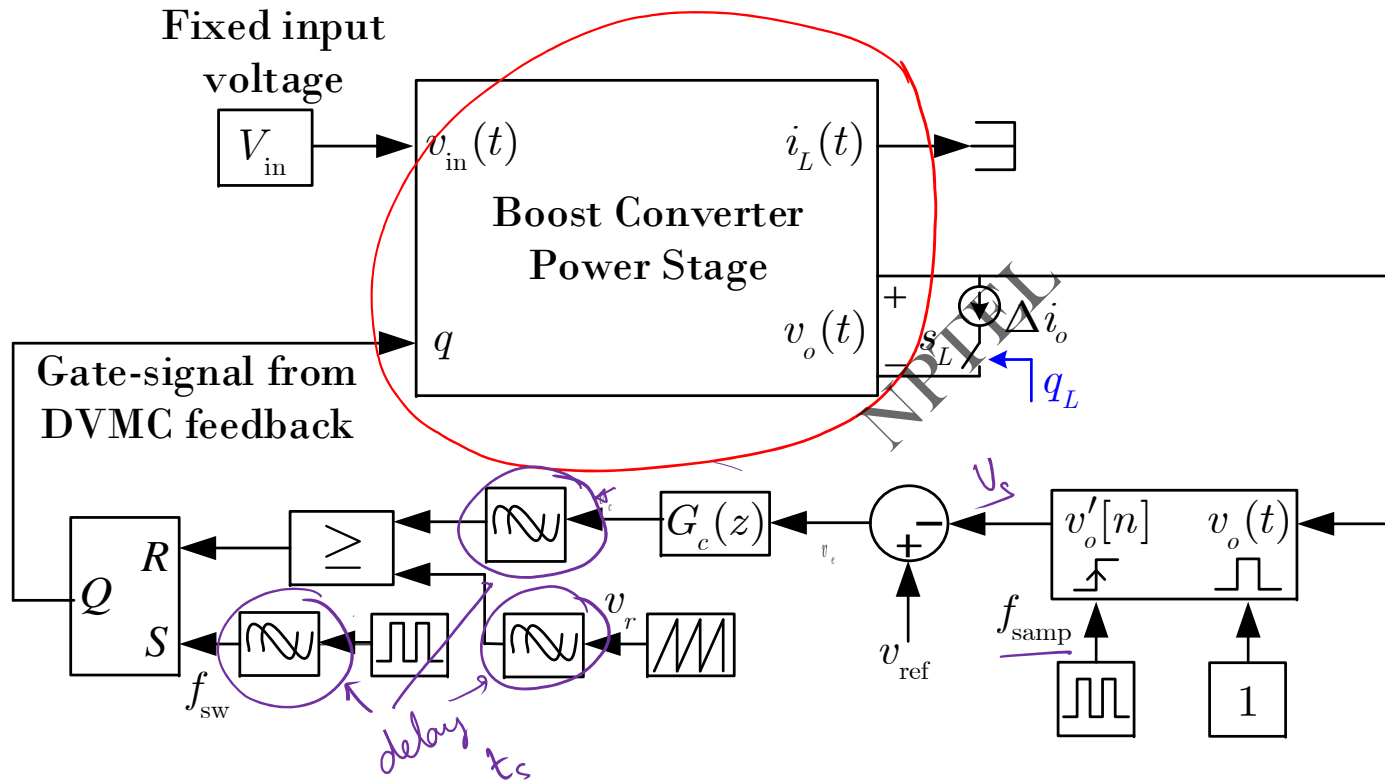
### *Device Under Test (DUT) for Validation of DT Large-Signal Model*



## *Validation of DT Large-Signal Model under Closed Loop*

### a) Using actual switch simulation

1. Provide initial conditions for  $v_C(t)$  and  $i_L(t)$
2. Do not turn on  $S_L$  for 1 ms and let the converter reach steady-state
3. Apply a load step
4. Capture time domain data and store as  $v_o$  and  $i_L$

## *Validation of DT Large-Signal Model under Closed Loop (contd...)*


### b) Using DT large-signal model

1. Provide initial conditions for  $v_C(t)$  and  $i_L(t)$  same as the switch simulation
2. Let the DT large-signal model run for 1 ms
3. Capture  $v_o(t)$  and  $i_L(t)$  for every sampling cycle until 1 ms

## Validation of DT Large-Signal Model under Closed Loop (contd...)

b) Using DT large-signal model

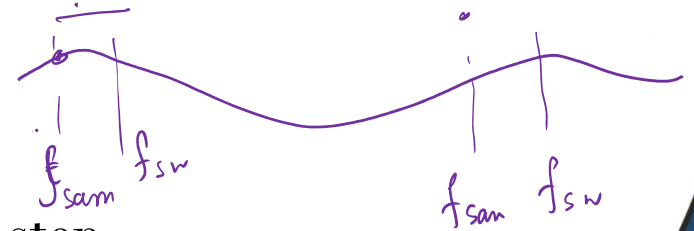4. Change the load resistance at 1 ms to emulate a load step
5. Capture  $v_o(t)$  and  $i_L(t)$  for every sampling cycle until the end time  
same as simulation run time
6. Compare the captured data of  $v_o$  &  $i_L$  for DT large-signal validation





# Steps to Verify Large-Signal DT Model using MATLAB

## boost\_conv\_DVMC\_simulation.m


```
clear; close all; clc;
%% Setting parameters
boost_parameter;
DCM_En=0;
N_tran=500; T_tran=2*N_tran*T;
t_start=0; t_sim=T_tran;
%% Controller parameters
Kp=8; Ki=0.7; Kd=(1*C)/T;
t_s=0.1*T;
V_m=10; R1=10; R2=2; R=R1;
I_L_int=0; V_c_int=4.99;
V_s_int=V_c_int; V_integral=0;
.....
```

## boost\_parameter.m

```
L=2e-6; % inductance
C=100e-6; % output capacitance
T=2e-6; % switching time period
r_L=10e-3; % inductor DCR
v_d=0*0.7; % diode voltage drop
r_l=5e-3; % LS MOS on resistance
r_d=5e-3; % HS MOS on resistance
r_C=5e-3; % capacitor ESR
Vin=3.3; % input voltage
Vref=5; % ref. output voltage
```

$$V_{ref} = 5 \text{ V}$$
$$V_{in} = 3.3 \text{ V}$$
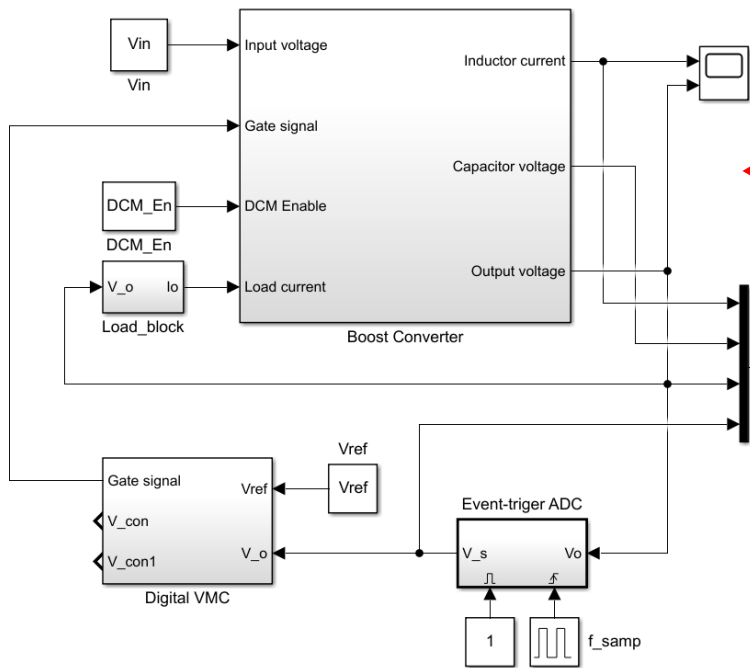
## Steps to Verify Large-Signal DT Model using MATLAB (contd...)




**boost\_conv\_DVMC\_simulation.m**

```
.....
sim('boost_converter_DVMC.slx');

t=boost_result.time; t_scale=t*1e3;
x=boost_result.data; i_L=x(:,1);
V_cap=x(:,2);
V_o=x(:,3); V_s=x(:,4);
%% Plot subroutine
plot_boost_simulation;
```
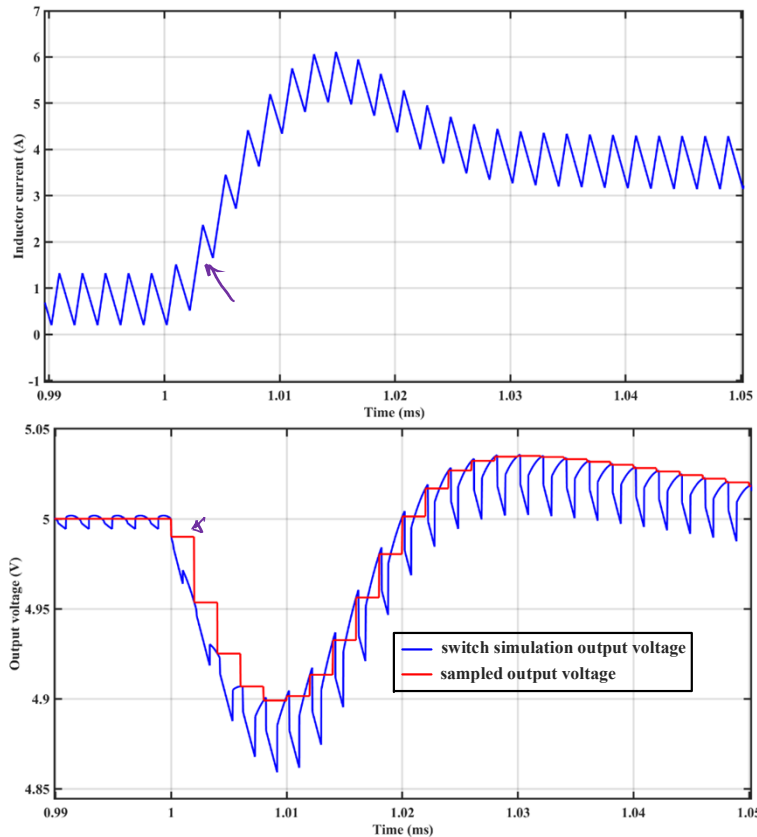
## Steps to Verify Large-Signal DT Model using MATLAB (contd...)



### boost\_conv\_DVMC\_simulation.m

```
.....  
sim('boost_converter_DVMC.slx');  
  
t=boost_result.time; t_scale=t*1e3;  
x=boost_result.data; i_L=x(:,1);  
V_cap=x(:,2);  
V_o=x(:,3); V_s=x(:,4);  
%% Plot subroutine  
plot_boost_simulation;
```

## Steps to Verify Large-Signal DT Model using MATLAB (contd...)

### boost\_DT\_LSM\_TE.m

```
clc
boost_parameter;

Kp=8; Ki=0.7; Kd=(1*C)/T;
t_s=0.1*T; V_m=10; R1=10;
R2=2; R=R1; N_tran=500;

boost_DT_model_matrices;

.....
```

*Comment*

*$R_1 = R_2$*

### boost\_DT\_model\_matrices.m

```
alpha=R/(R+r_C); r_e=(r_l+r_L);
T_s=t_s; I_den=[1 0; 0 1];

%% Define system, input and output matrices
A_on=[-r_e/L 0; 0 -alpha/(R*C)];
A_off=[-(r_e+(alpha*r_C))/L -alpha/L;
       alpha/C -alpha/(R*C)];
B=[1/L; 0];
C_on=[0 alpha];
C_off=[r_C*alpha alpha];
```

*A<sub>on</sub>*

*A<sub>off</sub>*

*B*

*C<sub>on</sub>*

*C<sub>off</sub>*

$$C_{off} = \begin{bmatrix} \alpha r_c & \alpha \end{bmatrix}$$

$$C_{on} = \begin{bmatrix} 0 & \alpha \end{bmatrix}$$

## Steps to Verify Large-Signal DT Model using MATLAB (contd...)

### boost\_DT\_LSM\_TE.m

```
.....  
i_L_n=I_L_int; v_cap_n=V_c_int;  
x_n=[i_L_n; v_cap_n];  
V_o_s=C_off*x_n; Vsam=v_cap_n;  
V_intg_int=0; Ve_int=0;  
t1=0; t1_scale=t1*1e3;  
  
figure(1)  
plot(t1_scale,x_n(1),'o','Linewidth', 2); hold on; grid on;  
  
figure(2)  
plot(t1_scale,Vsam,'o','Linewidth', 2); hold on; grid on;  
.....
```

NPTEL

## Steps to Verify Large-Signal DT Model using MATLAB (contd...)

### boost\_DT\_dynamics.m

$N_{tran}$   
0 to  $N_{tran}-1$

```
for n=0:N_tran-1
    figure(2)
    plot(tl_scale,Vsam,'o','Linewidth', 2); hold on; grid on;
    Ve=(Vref-Vsam);
    V_intg=V_intg_int+(Ki*Ve); V_intg_int=V_intg;
    V_der=Kd*(Ve-Ve_int); Ve_int=Ve;
    Vcon=(Kp*Ve)+V_intg+V_der; D_temp=Vcon/V_m;

    if D_temp<0
        D=0;
    elseif D_temp>1
        D=1;
    end

    .....
end
```

$$u_I[n] = u_I[n-1] + K_i V_e[n]$$

$$u_D[n] = K_d (V_e[n] - V_e[n-1])$$

$$u_P[n] = K_p V_e[n]$$

$$u[n] = u_P[n] + u_I[n] + u_D[n]$$

### boost\_DT\_LSM\_TE.m

```
.....
%% DT Large-Signal Model
boost_DT_dynamics;
R=R2; N_tran=500;
boost_DT_model_matrices;
V_o_s=C_off*x_n; Vsam=
V_o_s;
boost_DT_dynamics;
```


## Steps to Verify Large-Signal DT Model using MATLAB (contd...)

### boost\_DT\_dynamics.m

```
.....
else
    D=D_temp;
end
A_LS=(expm(A_off*(T-(D*T)-T_s)))*(expm(A_on*D*T))*(expm(A_off*T_s));
B1=(expm(A_off*(T-(D*T)-T_s)))*(expm(A_on*D*T))*((expm(A_off*T_s))-I_den)*(inv(A_off))*B;
B2=(expm(A_off*(T-(D*T)-T_s))*((expm(A_on*D*T))-I_den)*(inv(A_on))*B;
B3=((expm(A_off*(T-(D*T)-T_s))-I_den)*(inv(A_off))*B; B_LS=B1+B2+B3;
x_n1=A_LS*x_n+B_LS*Vin;
t1=t1+T; t1_scale=t1*1e3; x_n=x_n1; V_o_s=C_m*x_n; Vsam= V_o_s;
figure(1)
plot(t1_scale,x_n(1),'o','Linewidth', 2); hold on; grid on;
end
```


$$x_{n+1} = \underline{A_{eq}} x_n + \underline{B_{eq}} V_{in}$$
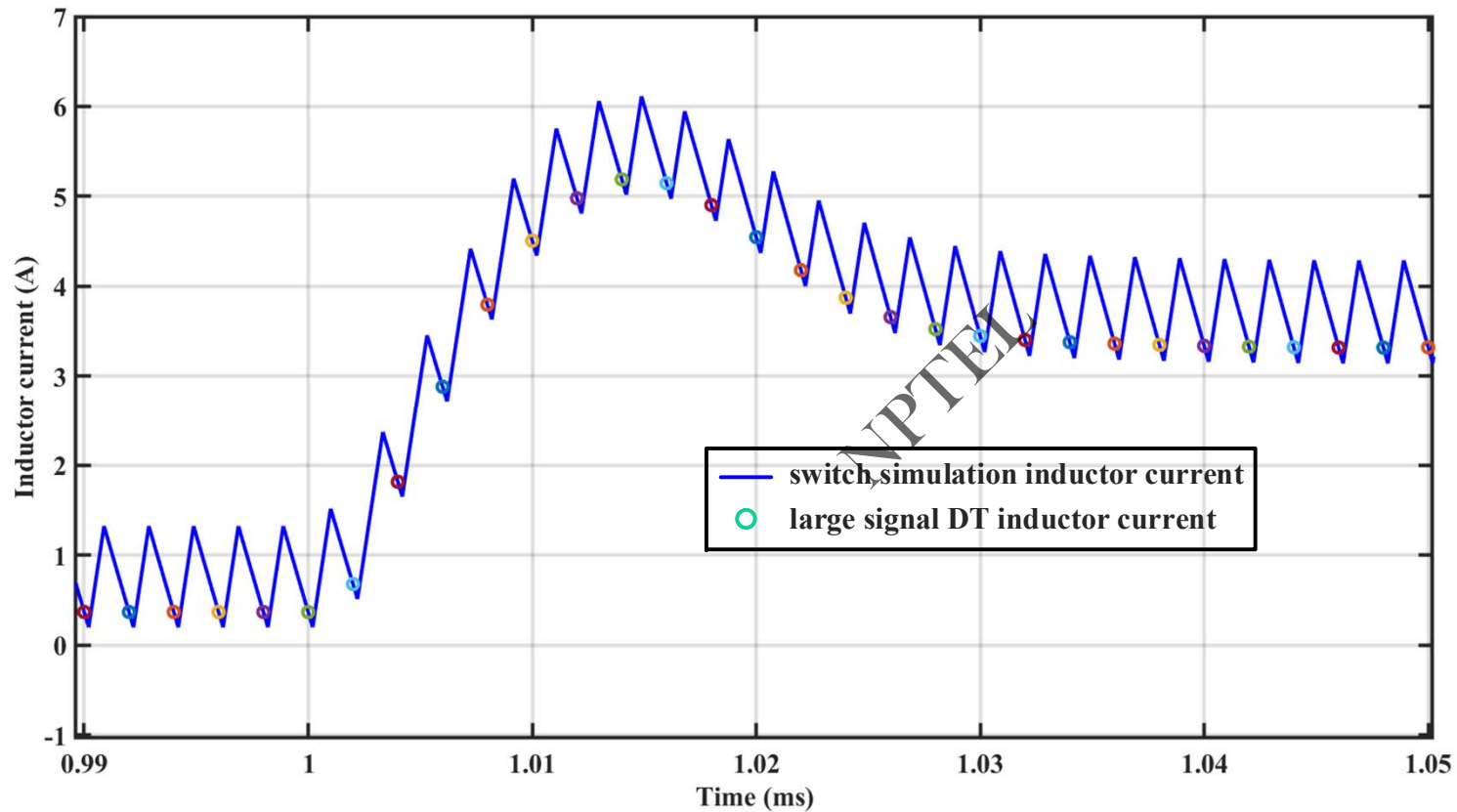
## Steps to Verify Large-Signal DT Model using MATLAB (contd...)





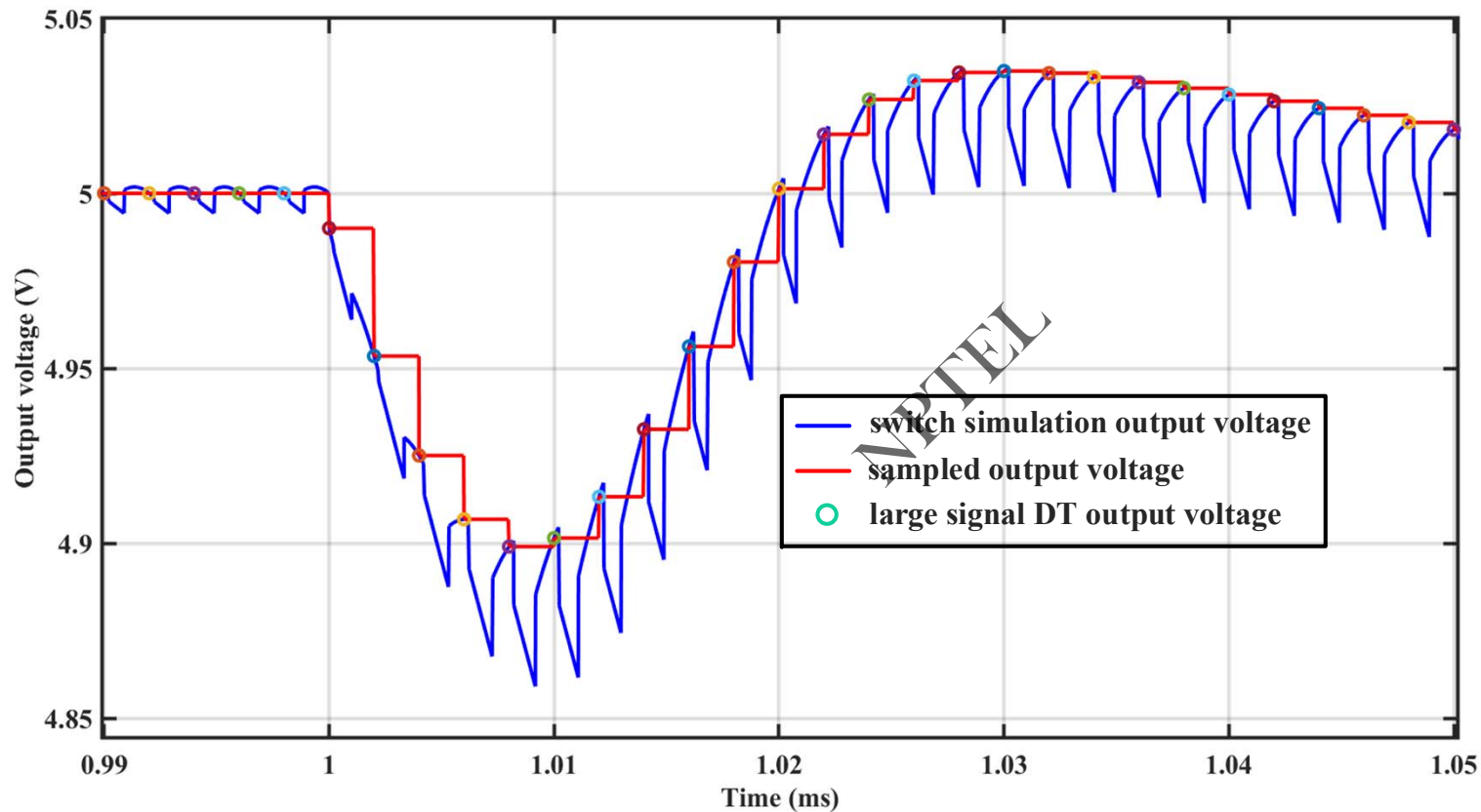
## Steps to Verify Large-Signal DT Model using MATLAB (contd...)


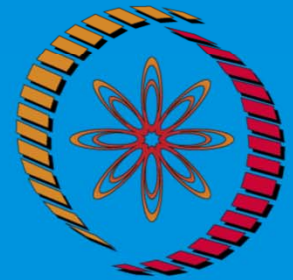
# CONCLUSION

- Recall of digital control architectures and MATLAB models
- Steps for simulation using MATLAB detailed switch models and discrete-time large-signal models
- MATLAB codes and step-by-step methods for model validation
- Validation case studies using a Boost Converter



**THANK  
YOU !**