



**NPTEL ONLINE CERTIFICATION COURSES**

# **DIGITAL CONTROL IN SMPCs AND FPGA-BASED PROTOTYPING**

**Dr. Santanu Kapat**

**Electrical Engineering Department, IIT KHARAGPUR**

**Module 04: Modeling Techniques and Mode Validation using MATLAB**

**Lecture 40: Model Accuracy with MATLAB Case Studies – Comparative Study**



## CONCEPTS COVERED


- CT control-to-output TF for synchronous buck converter with sampling delay
- DT control-to-output TF for synchronous buck converter
- DT and CT small-signal models – MATLAB implementation
- Small-signal model accuracy comparison – MATLAB case study

### *Buck Converter CT Control-to-Output TF for Sampled Data System*

$$G_{\text{vd}}(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)} = \frac{V_{\text{IN}}}{\frac{R + r_e}{R}} \frac{(1 + r_C C s)}{\left(1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}\right)}$$

~~Total loop delay  $\tau_d = t_s + DT$~~
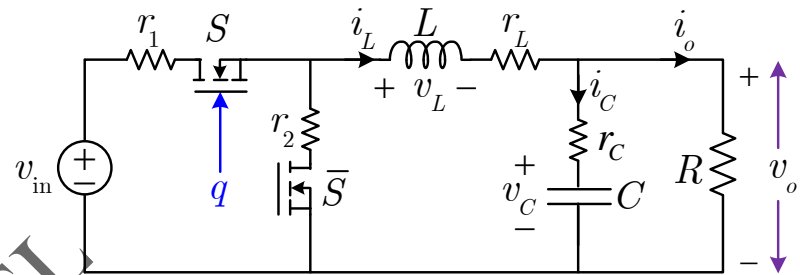
$$G_{\text{vd\_delay}}(s) = e^{-s\tau_d} \times G_{\text{vd}}(s) \Rightarrow G_{\text{vd\_delay}}(s) = \frac{V_{\text{IN}}}{\frac{R + r_e}{R}} \frac{(1 + r_c C s) e^{-s\tau_d}}{\left(1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}\right)}$$



$$w_0 \approx \frac{1}{\sqrt{L}} e$$

[ For details, refer to [Lecture~31, NPTEL “Digital Control in Switched...” course](#) ]




## Buck Converter DT Control-to-Output TF

$$\tilde{x}_{n+1} = A_{\text{eq}} \tilde{x}_n + B_{\text{eq}} \tilde{d} \quad \text{and} \quad \tilde{v}_o[n] = C_{\text{eq}} \tilde{x}_n$$

where  $A_{\text{eq}} = e^{A T}$  and  $B_{\text{eq}} = e^{A(T-t_d)} B_1 V_{\text{in}} T$

total loop delay  $\tau_d = t_s + DT$  and  $C_{\text{eq}} = \begin{bmatrix} \alpha r_c & \alpha \end{bmatrix}$

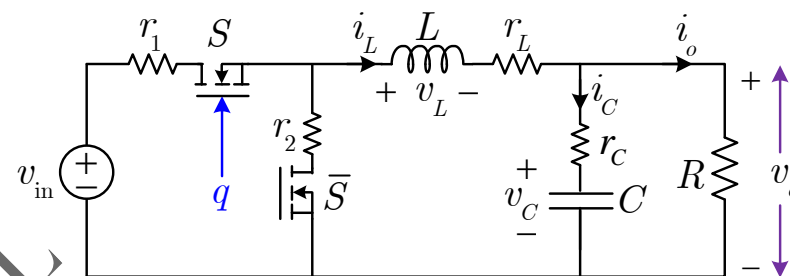
Applying Z-transformation  $G_{\text{vd}}(z) = \frac{\tilde{v}_o(z)}{\tilde{d}(z)} = C_{\text{eq}} (zI - A_{\text{eq}})^{-1} B_{\text{eq}}$




[ For details, refer to [Lecture~38, NPTEL “Digital Control in Switched...” course](#) ]
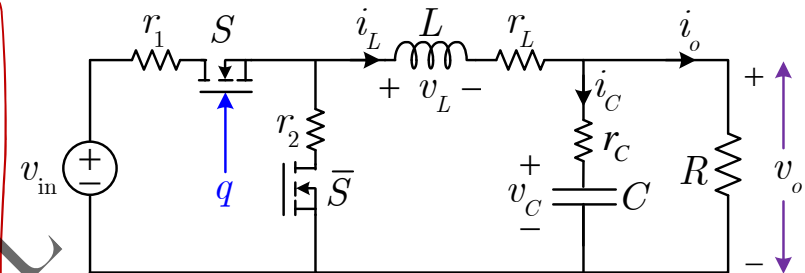
## Synchronous Buck Converter Parameter

$L=0.5\text{e-}6$ ;      % output inductance  
 $C=200\text{e-}6$ ;      % output capacitance  
 $T=2\text{e-}6$ ;      % switching time period  
 $r_L=5\text{e-}3$ ;      % inductor DCR  
 $r_1=5\text{e-}3$ ;      % High-side MOSFET on resistance  
 $r_2=5\text{e-}3$ ;      % Low-side MOSFET on resistance  
 $r_d=r_2$ ;      % diode on resistance  
 $v_d=0.55$ ;      % diode voltage drop  
 $r_C=3\text{e-}3$ ;      % capacitor ESR  
 $V_{in}=12$ ;      % nominal input voltage  
 $V_{ref}=1$ ;      % reference output voltage  
 $I_{o\_max}=20$ ;      % maximum load current


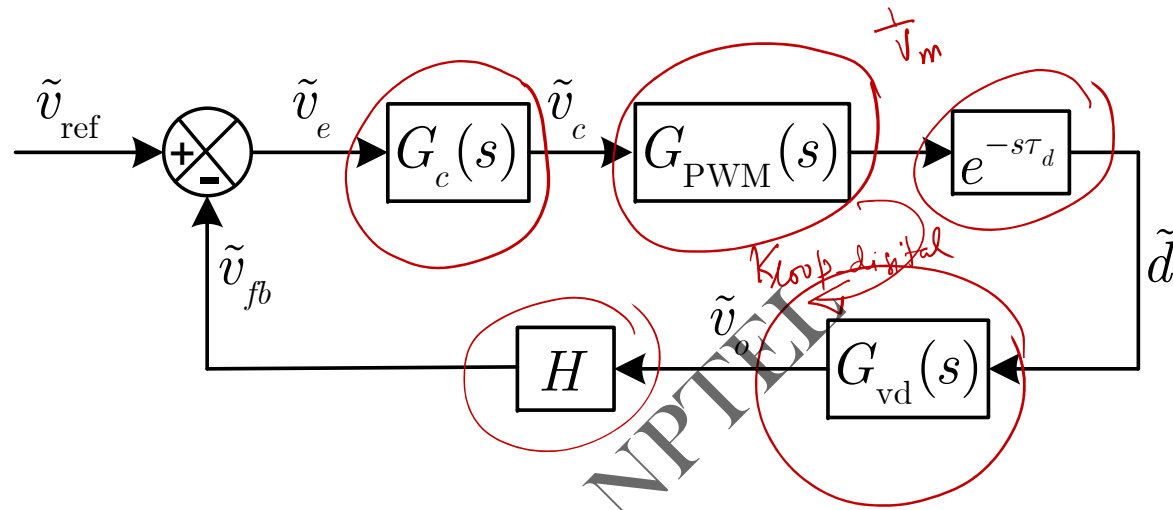
## Approximate CT Small-Signal Model under Digital Control



$$K_{\text{loop, digital}}(s) = K_{\text{loop, analog}}(s) \times e^{-s\tau_d} \quad \tau_d = t_{\text{adc}} + t_{\text{DPWM}}$$

[R. Erickson and D. Maksimovic, “Fundamentals of power electronics”, 3<sup>rd</sup> Ed., Springer, 2020]

## Buck Converter CT Control-to-Output TF

%% Define parameters

buck\_parameter;

V\_m=10; R=1;

D=Vref/Vin; r\_eq=r\_L+r\_l;

Fm=1/V\_m; t\_s=0.1\*T; t\_d=t\_s+(D\*T);

%% Define poles

alpha=(R+r\_eq)/R;

V\_e=Vin/alpha;

z\_c=sqrt(L/C);

w\_o\_ideal=1/sqrt(L\*C);

w\_o=w\_o\_ideal\*(sqrt((R+r\_eq)/(R+r\_C)));

Q=alpha/(((r\_C+r\_eq)/z\_c)+(z\_c/R));

.....

$Z_d = t_s + DT$   
ADC delay  
DPWM delay

NPTTEL

## Buck Converter CT Control-to-Output TF (cont....)

```

.....
%% Define zeros
w_z=1/(r_C*C);
%% Control-to-output TF Gvd
num_c=V_e*[1/w_z 1];
den_c=[1/(w_o^2) 1/(Q*w_o) 1];
Gvd=tf(num_c,den_c);
Gvd_delay=tf(num_c,den_c,'InputDelay',t_d);
Gvc=Fm*Gvd;
Gvc_delay=Fm*Gvd_delay;
figure(1)
bode(Gvc,'--b'); hold on;
bode(Gvc_delay,'g'); hold on;
    
```

$$T_d = t_s + DT$$

NPTEL

$$G_{vc}(s) = F_m G_{vd}(s)$$

$$G_{vc\_delay}(s) = F_m G_{vd\_delay}(s)$$

$$G_{vd\_delay} = G_{vd} \times e^{-sT_d}$$

$$\tilde{V}_o(s)$$

$$\tilde{d}(s)$$



## Buck Converter DT Control-to-Output TF

```
%% Load system parameters
```

```
buck_parameter;
```

```
V_m=10; R=1; ✓
```

```
alpha=R/(R+r_C); r_e=(r_l+r_L);
```

```
F_m=1/V_m; D=Vref/Vin; t_s=0.1*T;
```

```
%% Steady-state quantities
```

```
Io=Vref/R; I_L_av=Io;
```

```
Xss=[I_L_av; Vref];
```

```
%% Define system, input and output matrices
```

```
A_on=[-(r_e+(alpha*r_C))/L -alpha/L; alpha/C  
alpha/(R*C)];
```

```
A_off=A_on;
```

```
B=[1/L; 0];
```

```
C_m=[r_C*alpha alpha];
```

```
.....
```

$$C_m = \begin{bmatrix} \alpha r_c & \alpha \end{bmatrix}$$

## Buck Converter DT Control-to-Output TF (cont....)

```

.....
%% Obtain Aeq and Beq matrices
Aeq=(expm(A_on*T));
Beq=(expm(A_on*(T-(D*T)-t_s)))*B*Vin*T;
Ceq=C_m;
Deq=0;
%% DT Small-Signal Model
[num_vd,den_vd]=ss2tf(Aeq,Beq,Ceq,Deq);
G_vdd=tf(num_vd,den_vd,T);
G_vcd=F_m*G_vdd;
figure(1)
bode(G_vcd,'r'); hold on;
    
```

Lecture 38, 37

$$\tilde{x}_{n+1} = A_{eq} \tilde{x}_n + B_{eq} \tilde{d}$$

$$\tilde{v}_o[n] = C_{eq} \tilde{x}_n + D_{eq} \tilde{d}$$


NPTTEL

$$G_{vcd}(z)$$

$$G_{vc}(z) = F_m G_{vd}(z)$$


## Model Accuracy | Control-to-Output TF – Comparative Study

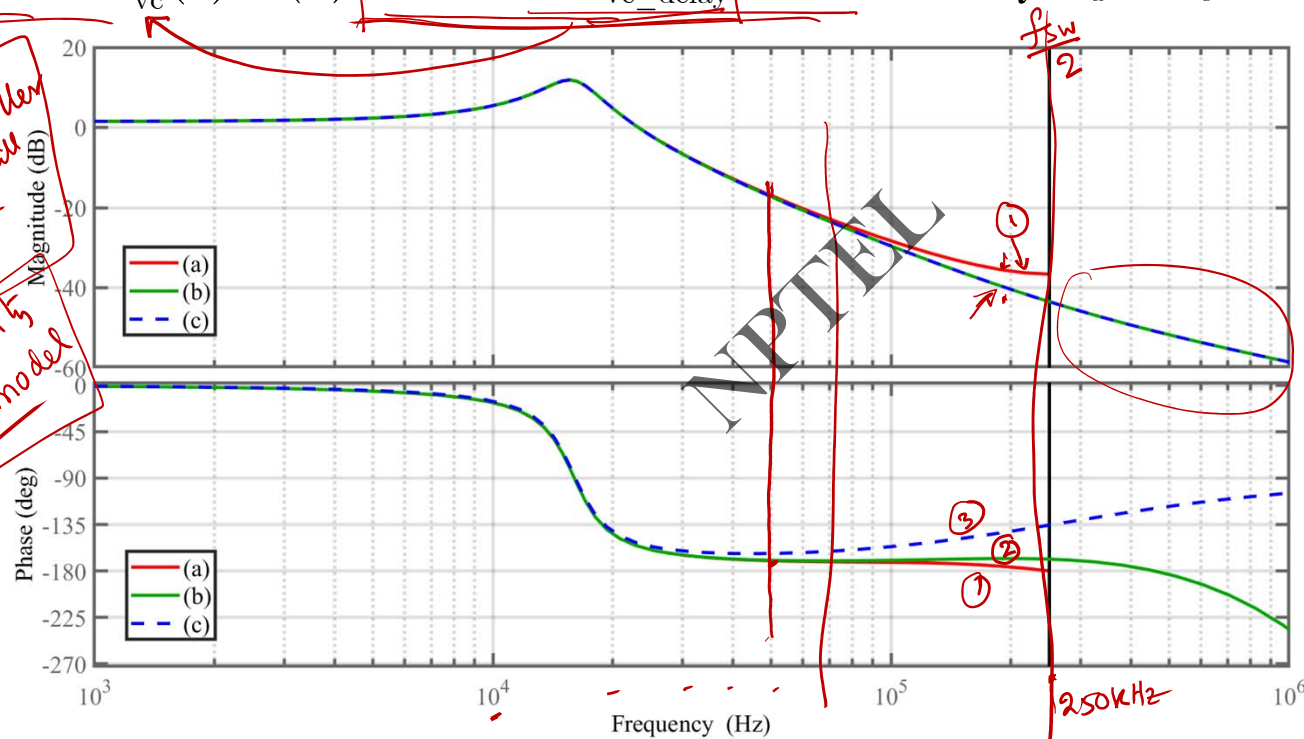(a) DT SSM  $G_{vc}(z)$ , (b) CT SSM  $G_{vc\_delay}(s)$  with delay  $\tau_d = t_s + DT$ , (c) CT SSM  $G_{vc}(s)$


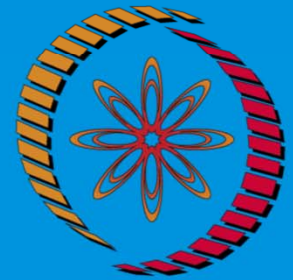
## CONCLUSION

- CT control-to-output TF for synchronous buck converter with sampling delay
- DT control-to-output TF for synchronous buck converter
- DT and CT small-signal models – MATLAB implementation
- Small-signal model accuracy comparison – MATLAB case study



**THANK  
YOU !**