



NPTEL ONLINE CERTIFICATION COURSES

# CONTROL AND TUNING METHODS IN SMPCs

Dr. Santanu Kapat


Electrical Engineering Department, IIT KHARAGPUR

**Module 01: Switched Mode Power Converters and Simulation**


**Lecture 01: DC Power Conversion Systems – Introduction**
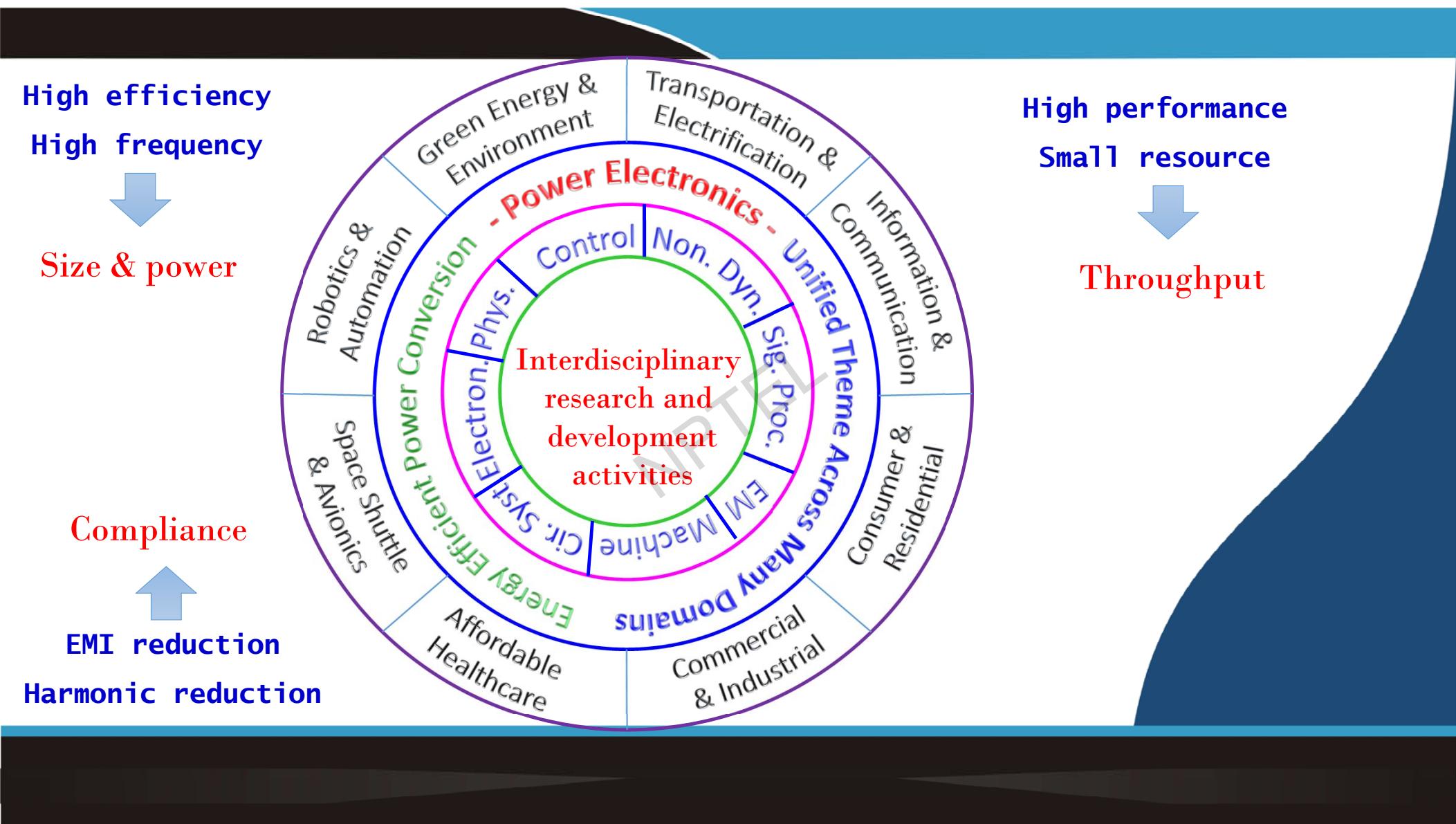
# Concepts Covered

- Recent trends in power electronics
- Few emerging applications and challenges
- Understanding need for DC power conversion
- Primary objectives of voltage and current regulators
- Course overview and reference resources


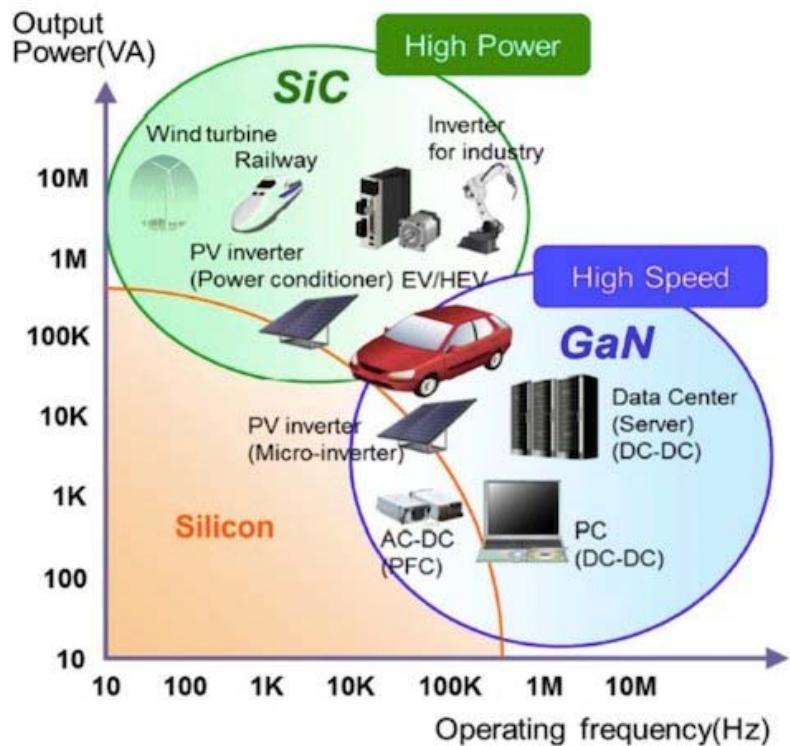
## *Wide Band Gap (WBG) Devices in Power Electronics*




- Wide band gap
- High junction temperature
- Lower on resistance
- Lower gate charge requirement
- Negligible reverse recovery

Source: [The Graham Lab, Georgia Tech](#)

# GaN Based Power Electronics – Market Forecast
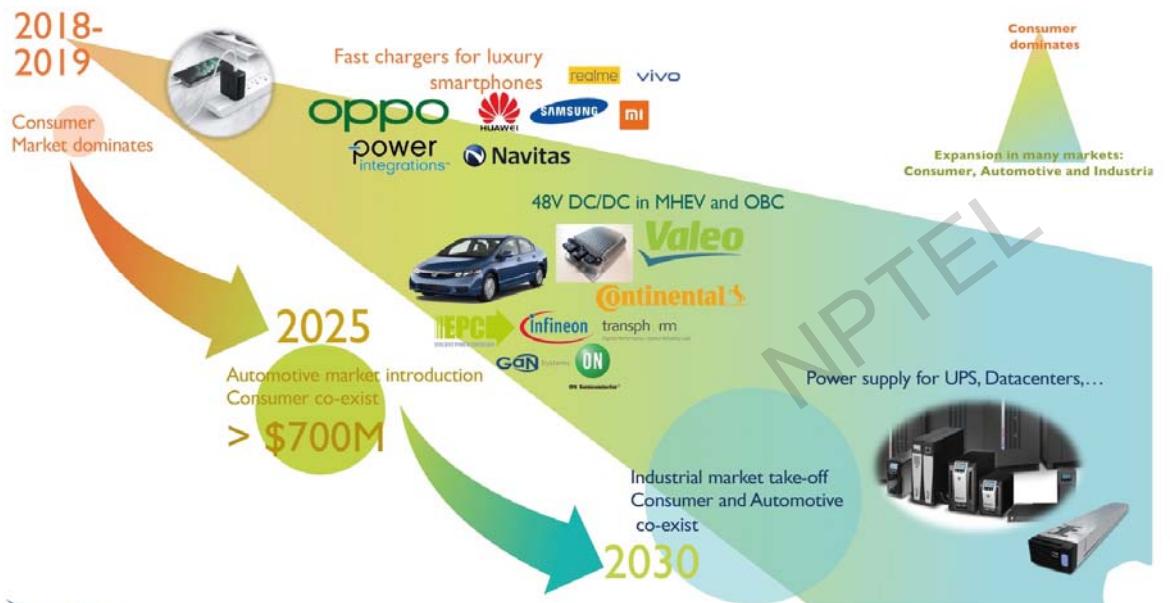
## Power GaN - Entering: a new era

(Source: Power GaN: Epitaxy, Devices, Applications & Technology Trends report, Yole Développement? 2019)



Source: Yole Development

© 2020 | www.yole.fr – www.i-micronews.com

# *SiC Based Power Electronics and Applications*

## **Power SiC: long-term evolution**

(Source: Power SiC 2019: Materials, Devices, and Applications, Yole Développement)




Source: Yole Development
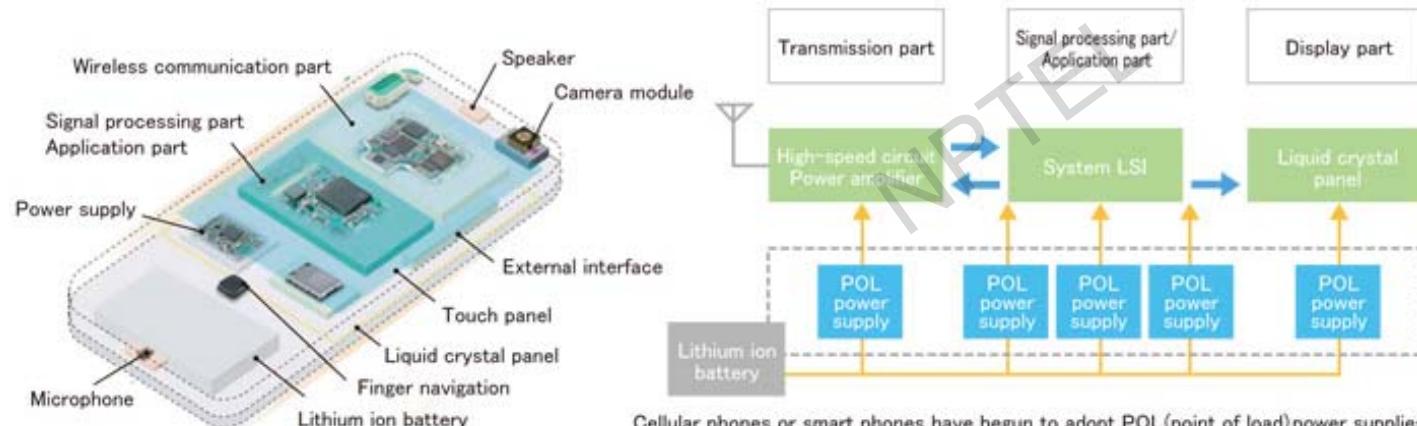
# DC Power Conversion in a Smartphone



Samsung smartphone **Multiple step-down and step-up voltage regulators**




Cellular phones or smart phones have begun to adopt POL(point of load) power supplies, in which small power supplies are distributed in close proximity to each load, as the number of channels of power supplies increase.

**POL  
(Point of load)**

Source: [TDK product center](#)

# Power Supply Network in a Smartphone

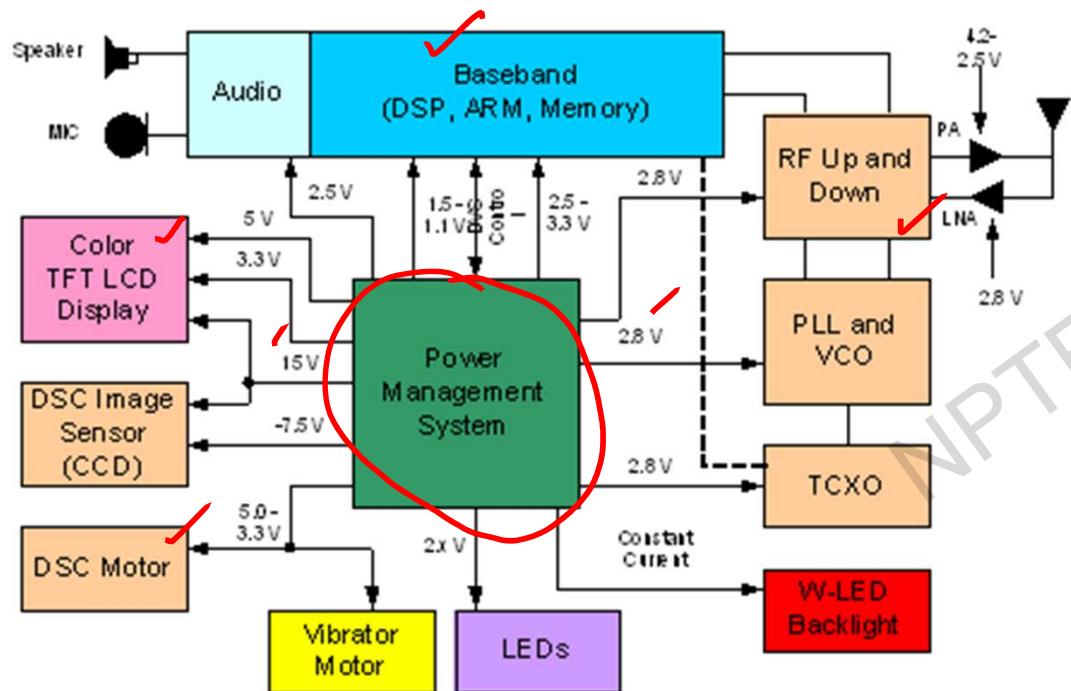

❑ Multiple outputs with multiple

voltage/current requirements


❑ Only one source – Li-ion battery

❑ Require multiple DC

voltage regulators

Source: [EDN Network](#)

## *Power Supply Network in Data Center*

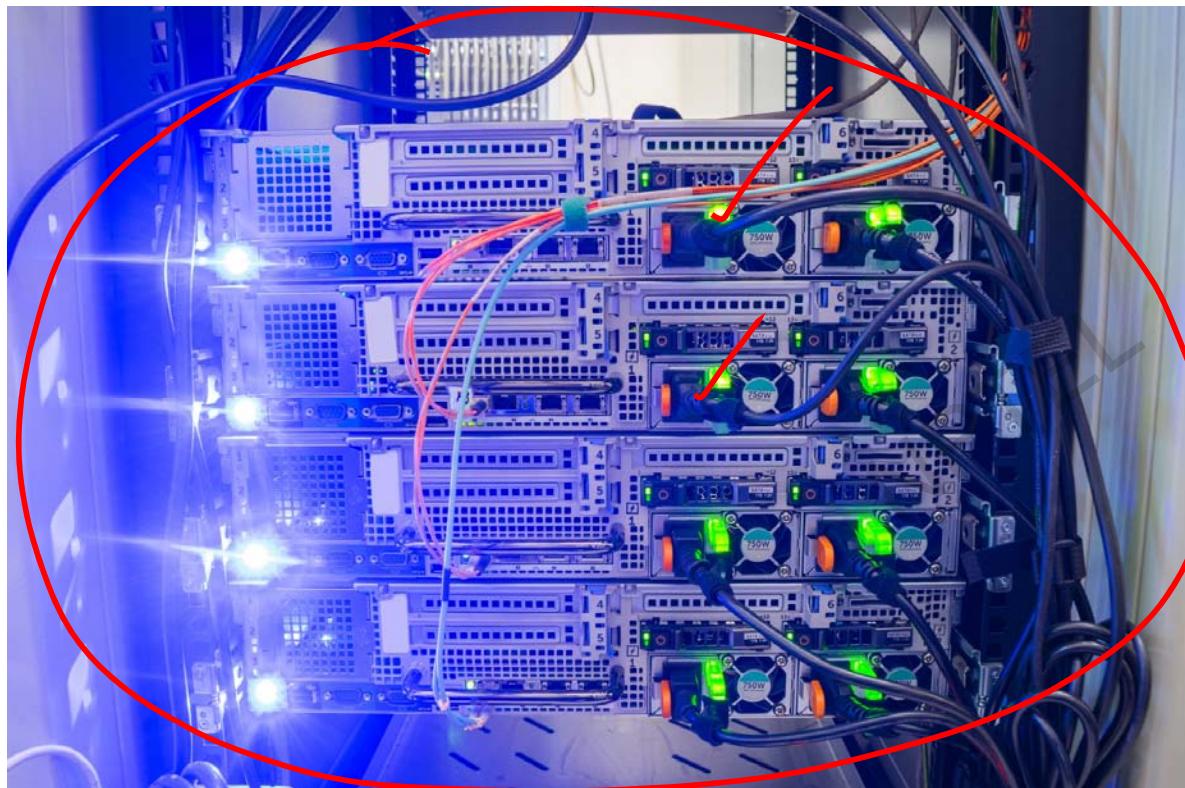


Source: [DataCenter Knowledge](#)


- Low voltage high current
- Modular plug-and-play power supply with hot swapping
- Ultra-fast transient performance
- High efficiency

# *48V DC Power Conversion in Data Center*

## Intermediate Bus Architecture

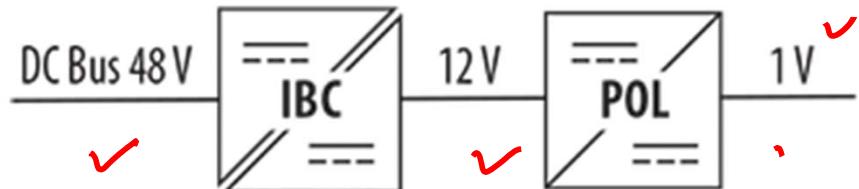

## DC Bus Architecture

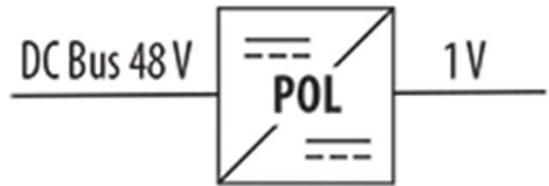


- ❑ POL (point of load) converter may need to drive 100s of A, even more
- ❑ Challenges – POL architectures and control methods to meet high efficiency and fast transient

Source: [Efficient Power Conversion \(EPC\)](#)


# *Power Supply Network in Electric Vehicles*

All-Electric Vehicle

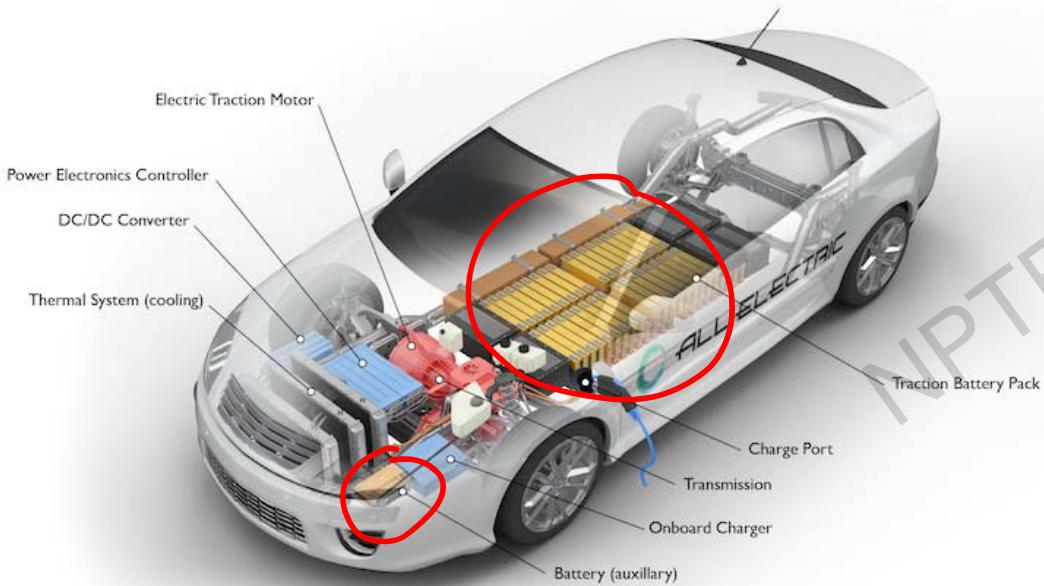


afdc.energy.gov

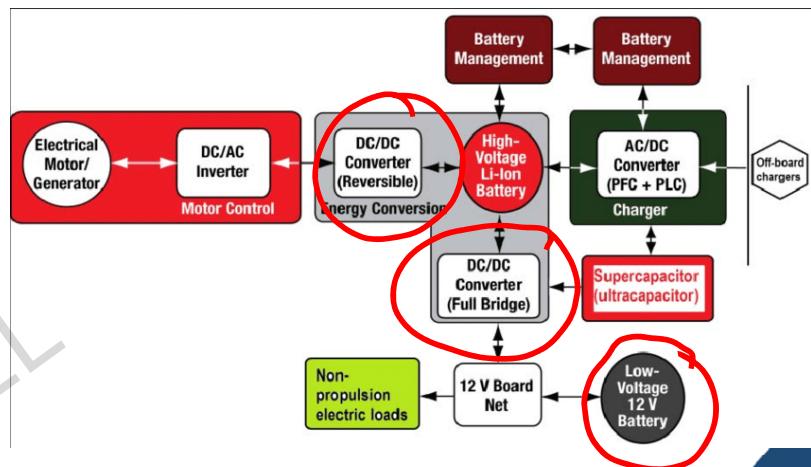Source: [AFDC, Department of Energy, USA](#)



Source: [Texas Instruments](#)

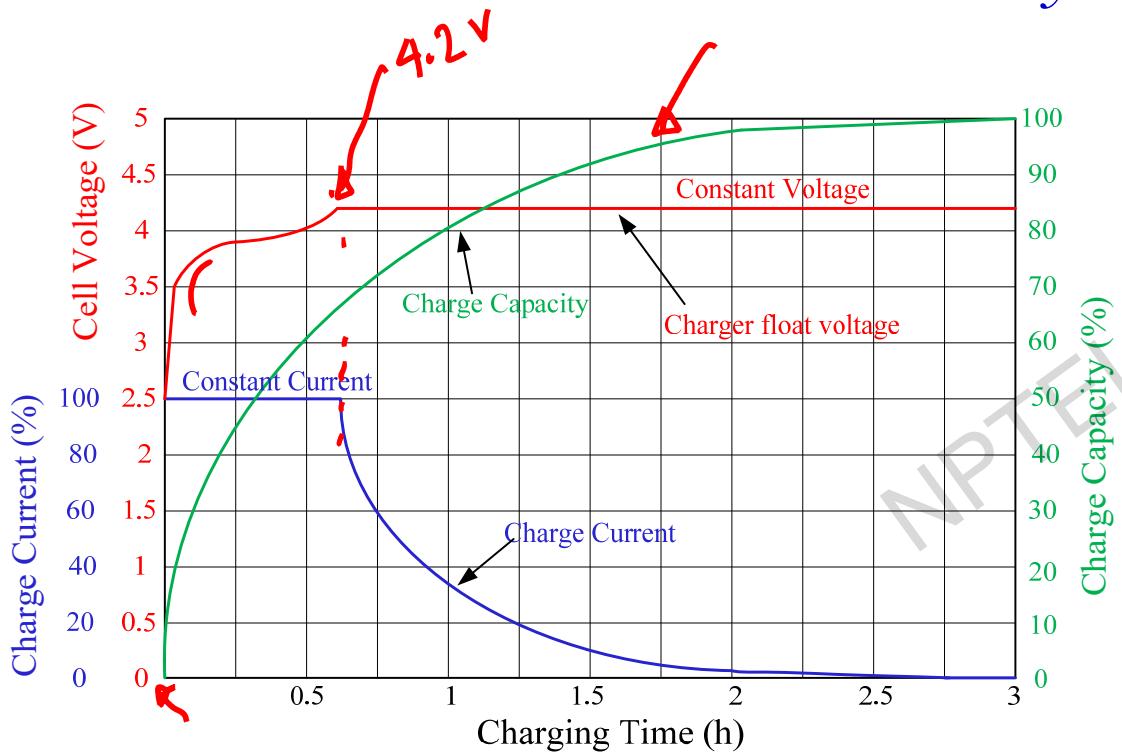
## *DC Power Conversion in Fast Battery Charging*



*(Volts/capacity vs. time when charging lithium-ion)*

- Constant current charge/ discharge
- Constant voltage charging
- Need for seamless transition  
from CC to CV mode

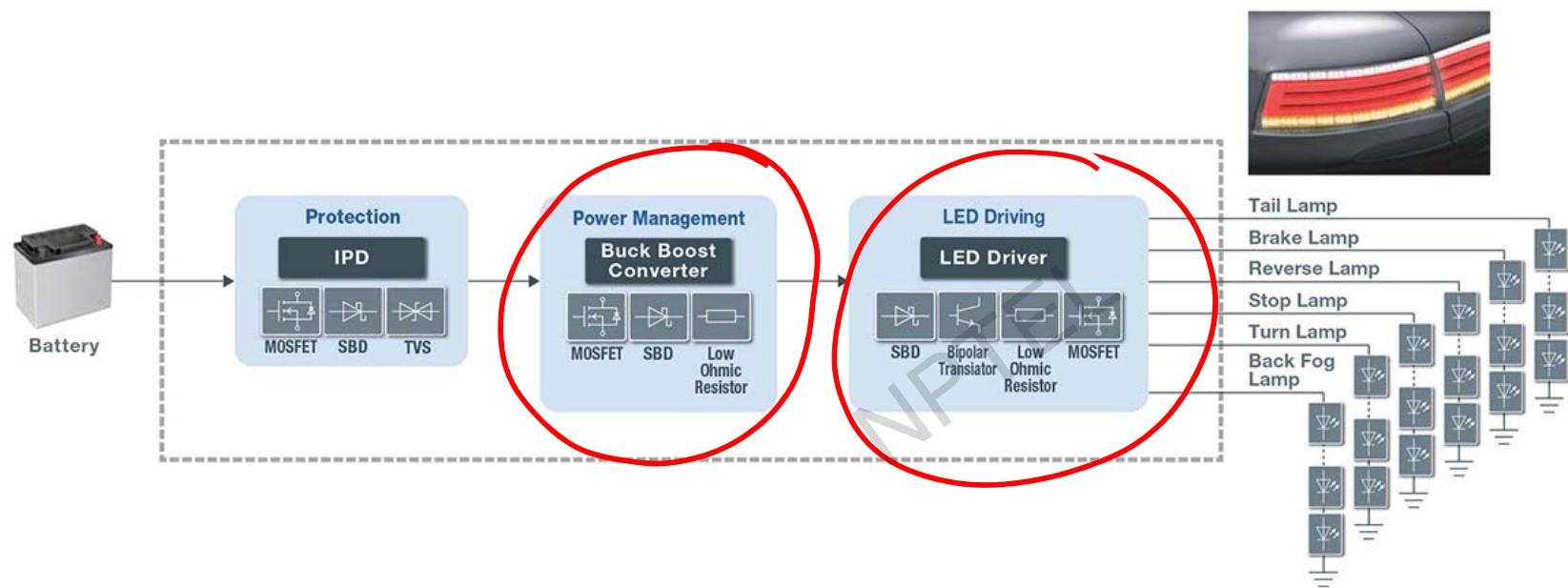
# DC Power Conversion in Automotive LED Driving




Source: [ROHM Semiconductor](#)

## DC Power Conversion in LED Driving

- Analog dimming

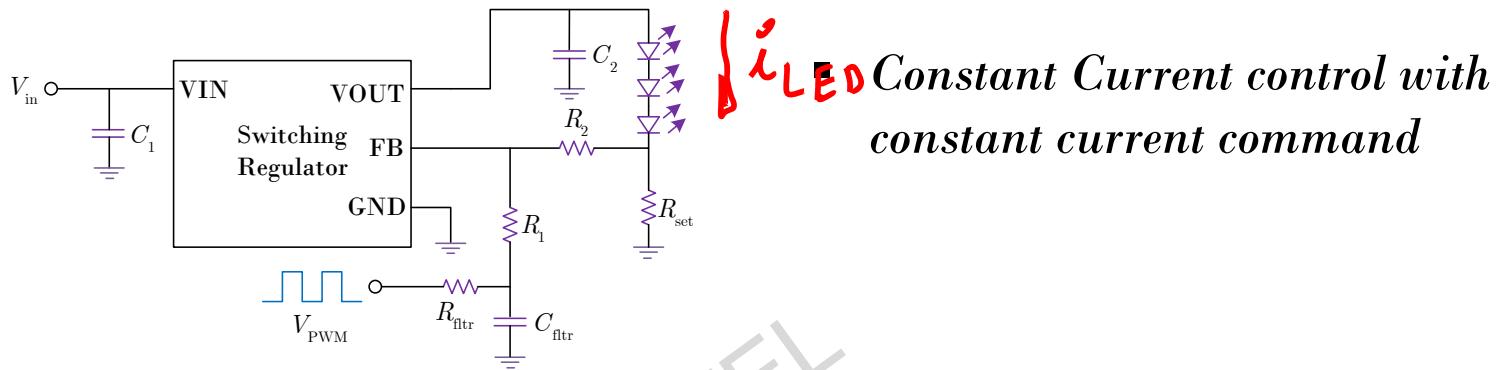

- PWM dimming

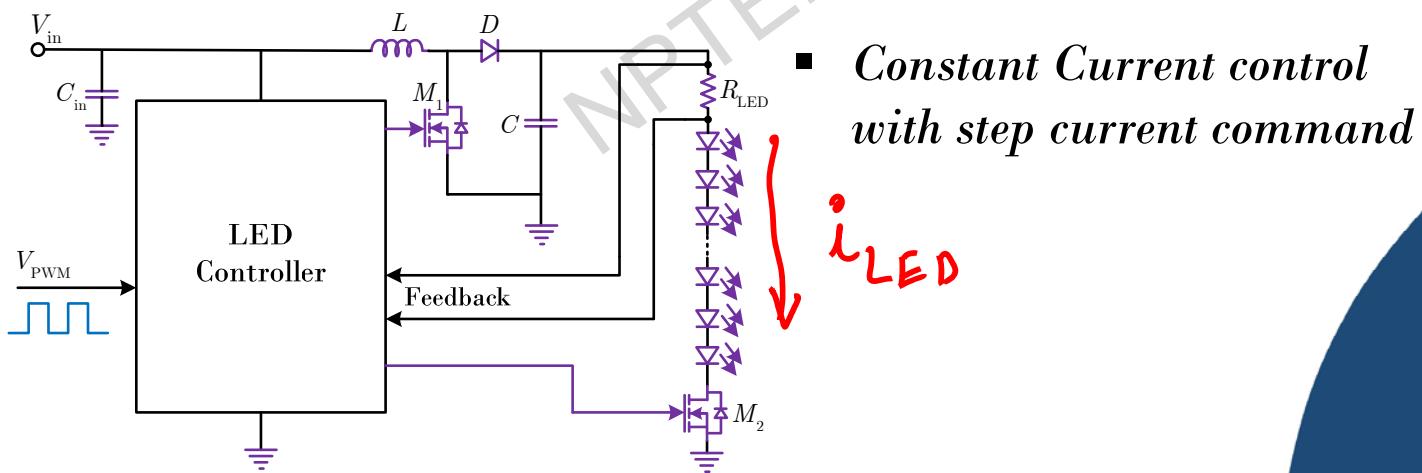


$i_{LED}$  Constant Current control with constant current command

■ Constant Current control with step current command

$i_{LED}$

## *Constant Current Source in LED Driving*


### Approach 1:

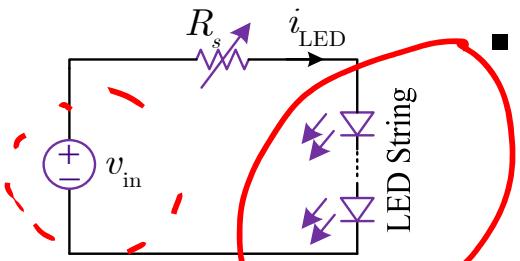

- Control of  $i_{LED}$  by varying  $R_s$

- Varying losses
- Poor efficiency
- Large heatsink

### Approach 2:

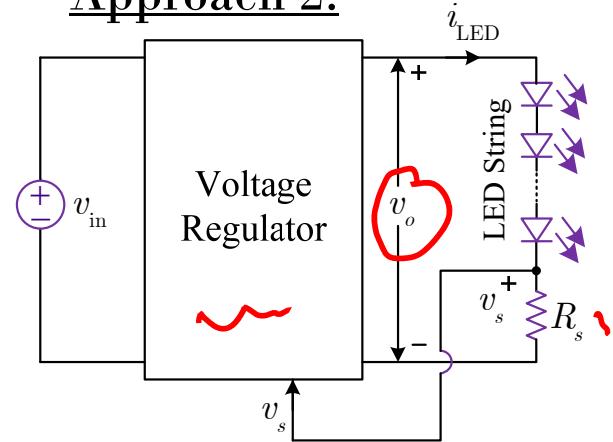


- Control of  $i_{LED}$  by adjusting  $v_o$

- Improved efficiency
- Efficiency of VR crucial
- Losses in series resistance

## *Constant Current Source in LED Driving*

### Approach 3:

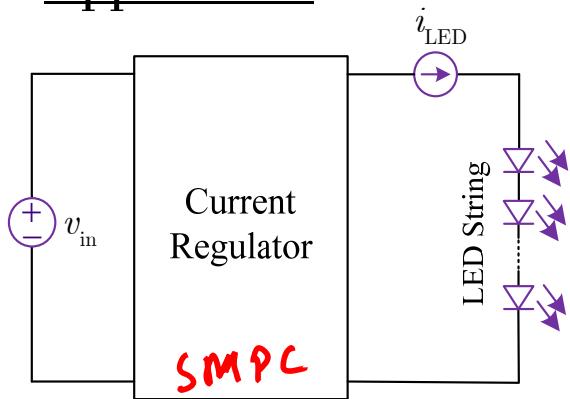


- Control of  $i_{LED}$  by varying using a current regulator

### Approach 4:



A combination of current source mode and voltage source mode configurations !!

## DC Power Conversion – Objectives

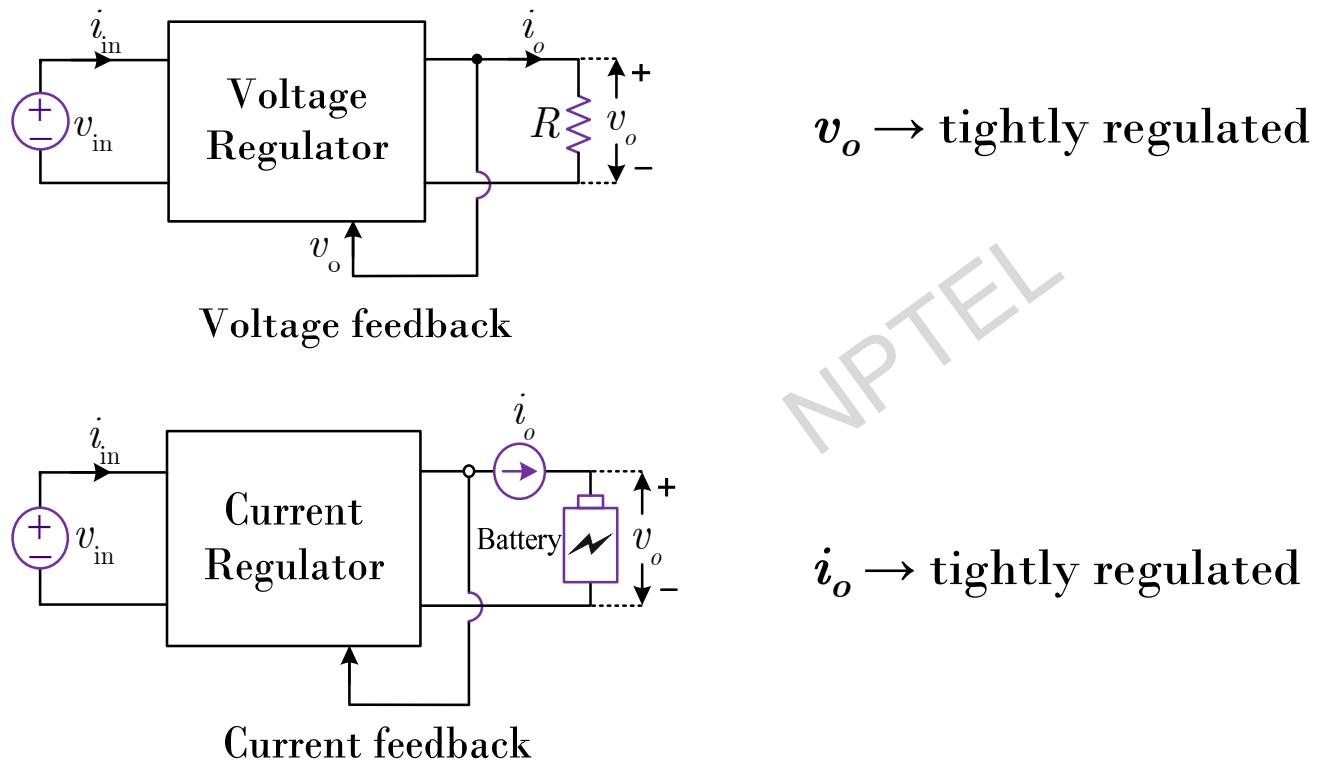
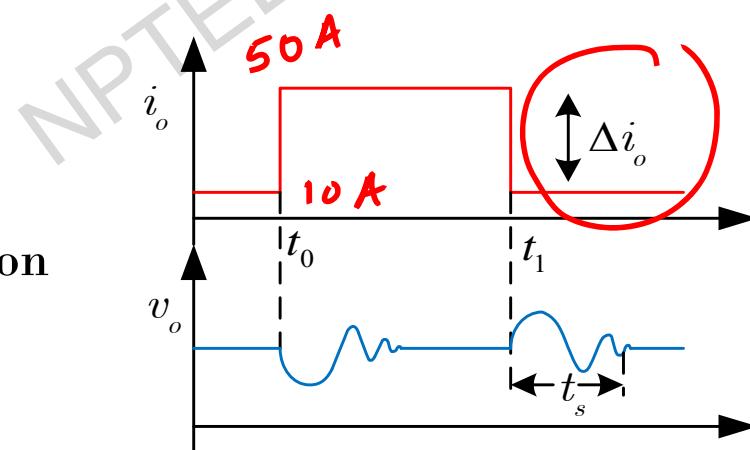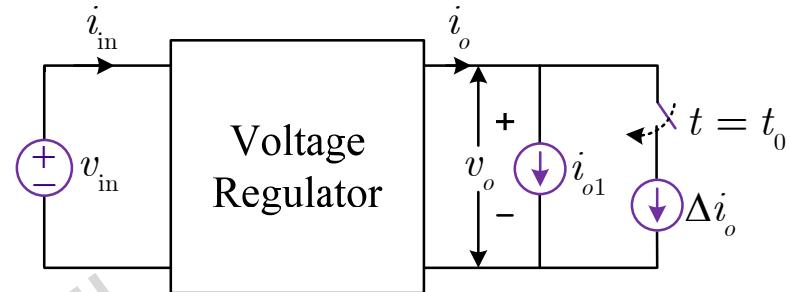
## *Transient Scenario in a Voltage Regulator*

- Typical load profile
  - Fast load slew rates
  - Frequent transients
  
- Challenges
  - Overshoot/ undershoot reduction
  - Fast transient recovery




## *DC Power Conversion System*




- Battery
- DC grid
- Ultra-cap
- Solar
- Step-down or  
step-up or both
- Without isolation or  
with isolation
- Mobile devices
- Cloud computing
- Automotive
- LED driving
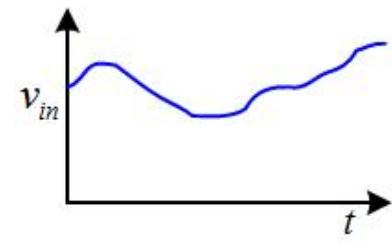
## DC Power Conversion – Primary Objectives



Source voltage  
variations

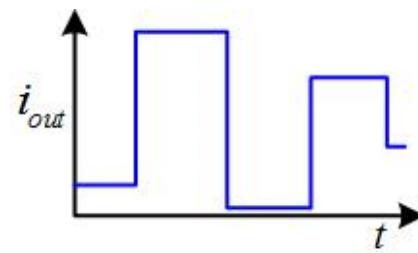- Tight voltage or current regulation
- High efficiency over a wide range
- Very fast transient performance
- High power density – smaller size
- Stable behavior – predictable ripple



Load current  
variations

## *Summary of Objectives*

- Suitable choice of voltage and current regulators – important
- Understanding behavior and estimating losses – crucial
- Size reduction of DC power conversion – growing trend
- High efficiency and fast transient performance – mandatory
- Selection of suitable modulation and control techniques – essential
- Design and control of voltage and/or current regulators – critical

# Overview of this course

- Brief introduction of switched mode power converters – primarily non-isolated
- Well-known fixed-frequency and variable-frequency modulation techniques
- Introduction to various feedback and feedforward control methods
- Overview of modeling and analysis techniques

# Overview of this course

- Small-signal and frequency response analysis
- Small-signal based controller design and tuning methods
- Understanding large-signal based modeling and control
- Large-signal based tuning methods and critical performance limits

# Reference

[1] S. Kapat and P. T. Krein, "A Tutorial and Review Discussion of Modulation, Control and Tuning of High-Performance DC-DC Converters based on Small-Signal and Large-Signal Approaches" *IEEE Open Journal of Power Electronics*, vol. 1, pp. 339 - 371, Aug. 2020.

[2] R. W. Erickson and D. Maksimovic, Fundamentals of Power Electronics, 3<sup>rd</sup> Ed., Springer, 2020.

[3] P. T. Krein, Elements of Power Electronics, Indian Edition, Oxford University Press, 2012

Prior NPTEL resources: For more detailed SMPC topologies, please refer to NPTEL course on "***Switched Mode Power Conversion***" – [Link here](#)





NPTEL ONLINE CERTIFICATION COURSES

# CONTROL AND TUNING METHODS IN SMPCs

Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR


**Module 01: Switched Mode Power Converters and Simulation**

**Lecture 02: Overview of voltage regulators**

# Concepts Covered

- Overview of linear voltage regulators
- Introduction to switched capacitor converters
- Understanding hybrid switched capacitor converters
- Basics switched mode power converters

## Voltage Regulator – Simplest Form

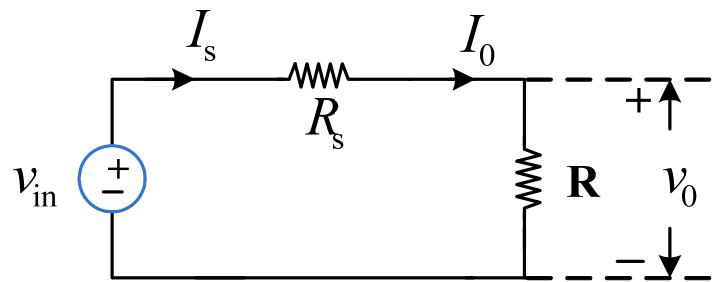



Voltage gain

$$k_v = \frac{v_o}{v_{in}} = \frac{R}{R + R_s}$$

Theoretical efficiency

$$\eta = k_v$$

## Voltage Regulator – LDO

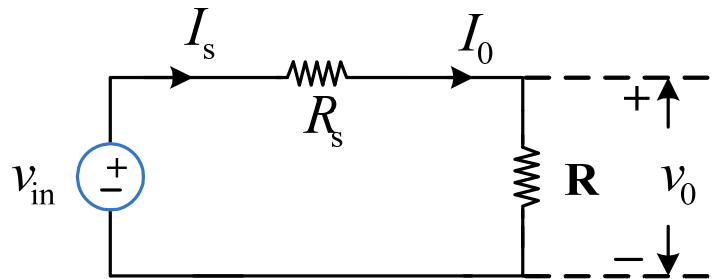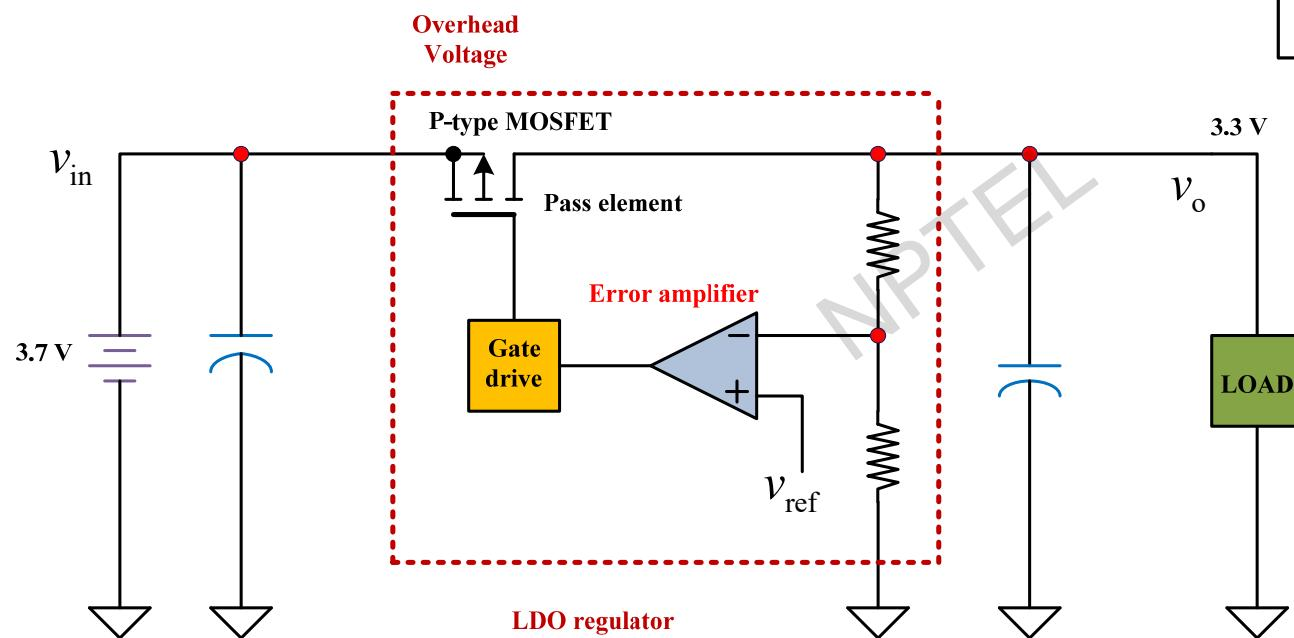

## Advantages and Limitations of Linear Voltage Regulators


### Advantages

- Simple to analyze and design
- Ultra-low power applications
- Negligible switching noise, low EMI
- Compact design using IC

### Limitations


- Low efficiency at high dropout voltage
- Poor current handling capability
- Higher losses at higher power level
- Step-up operation not possible
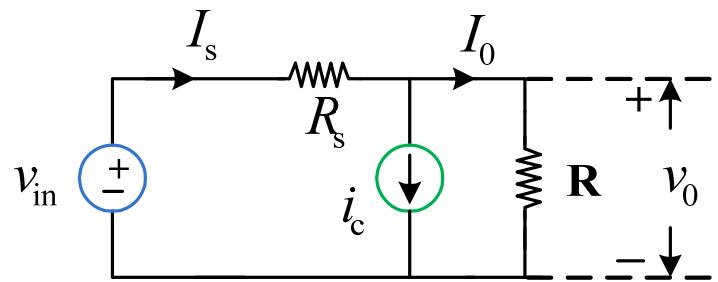
## Shunt Voltage Regulators – Simplest Form



$$k_v = \frac{v_o}{v_{in}} = \frac{R}{R + R_s} \times \left( 1 - \frac{R_s i_c}{v_{in}} \right)$$
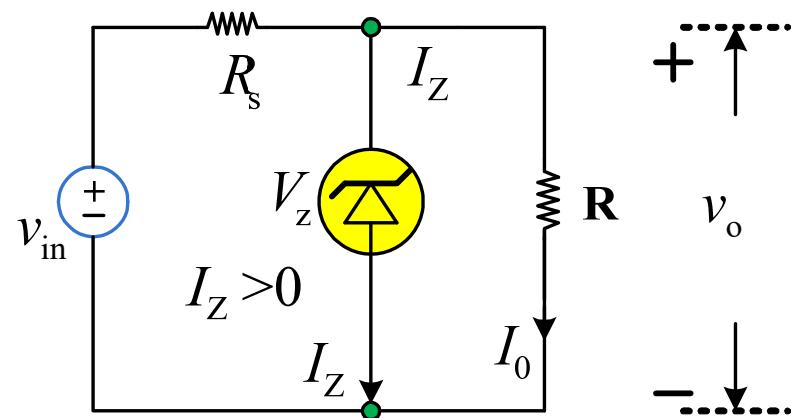
$$\eta = k_v \times \left( 1 - \frac{R_s i_c}{v_{in}} \right) / \left( 1 + \frac{R i_c}{v_{in}} \right)$$



## Advantages and Limitations of Shunt Voltage Regulators


### Advantages

- ❑ Additional current sink path for better output voltage regulation - current source/sink applications
- ❑ Common in voltage ref. circuits

### Limitations

- ❑ Power losses in series & shunt paths
- ❑ Poor efficiency than series VR
- ❑ Non zero power loss for  $P_{out}=0$
- ❑ Step-up operation not possible
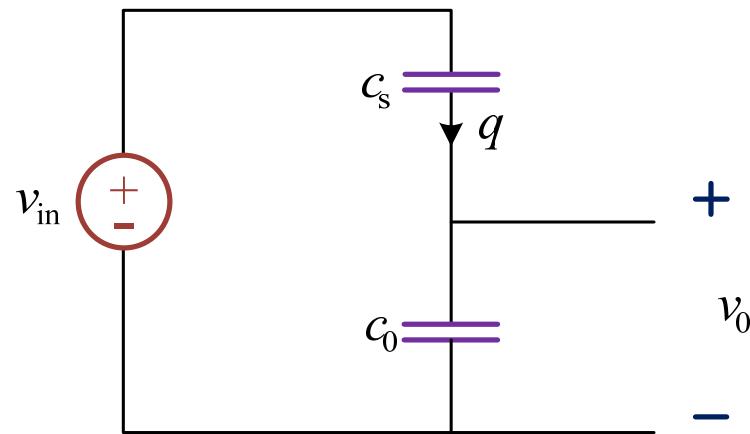
## Capacitor Voltage Regulators – Simplest Form




Under no load condition

$$q = C_o v_o = C_s (v_{in} - v_o)$$

$$v_o(\infty) = \frac{C_s}{C_s + C_o} \times v_{in}$$

What happens after connecting load?
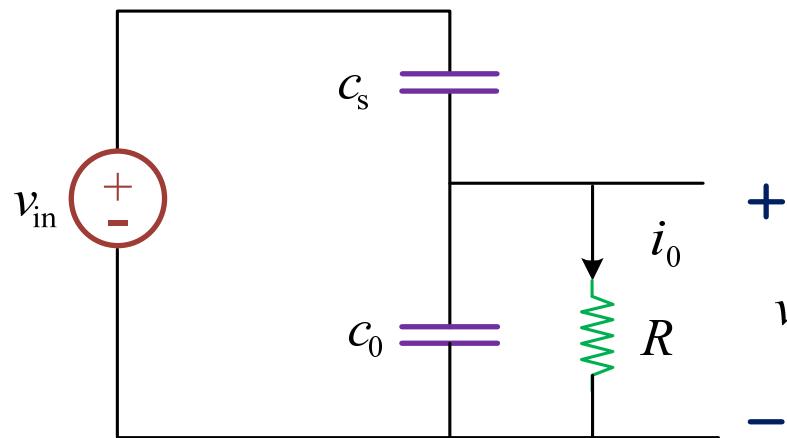
## Capacitor Voltage Regulators Contd ...



After connecting load resistance



$$v_o(t) = v_o(0) \times \exp\left(\frac{-t}{\tau_{eq}}\right),$$
$$\tau_{eq} = R \times (C_s + C_o)$$

$$v_o(\infty) = 0$$

Output voltage collapses!!

What is the next step?


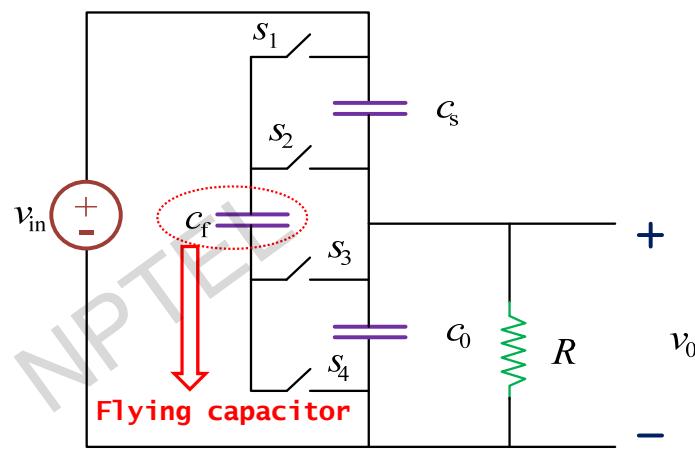
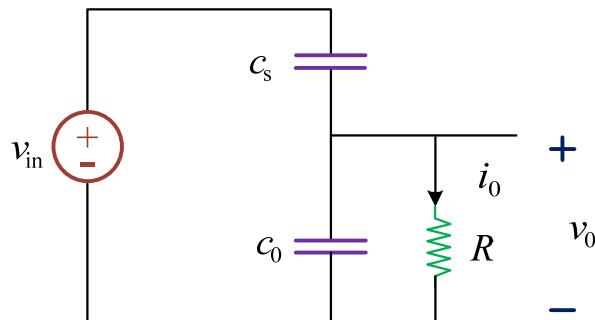
## Capacitor Voltage Regulators using Flying Capacitor




Charge balance can be achieved using a flying capacitor and by periodically switching among source and o/p Caps

Step-down switched capacitor VR
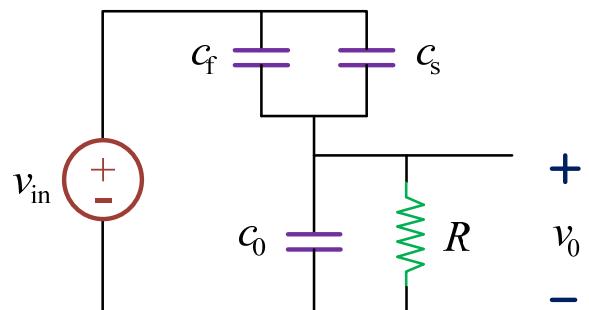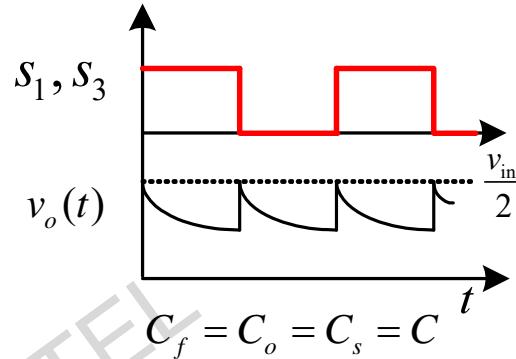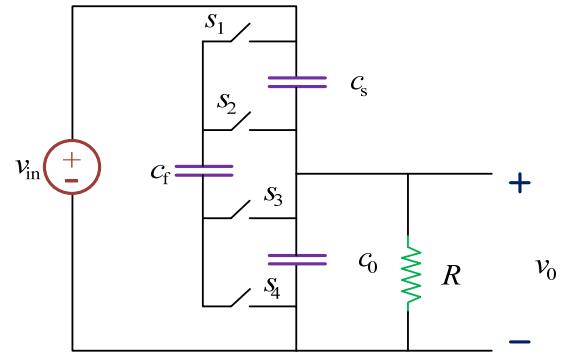
## Capacitor Voltage Regulators using Flying Capacitor




Charging phase of flying cap


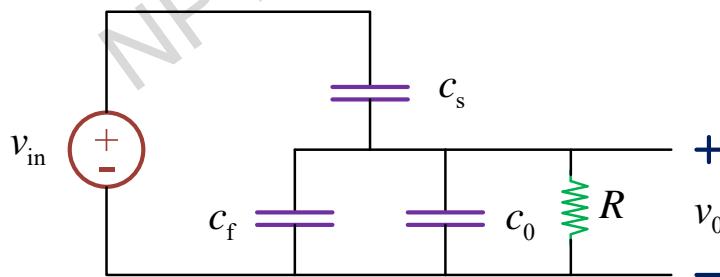


Discharging phase of flying cap
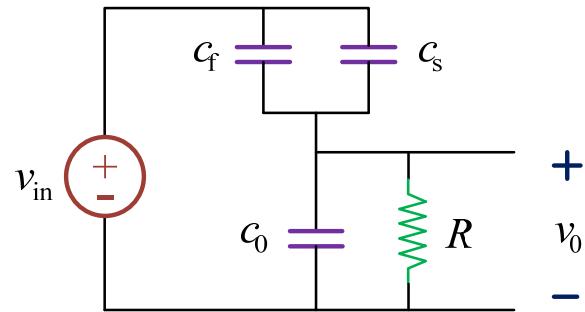
## Capacitor Voltage Regulators using Flying Capacitor




Charging phase of flying cap

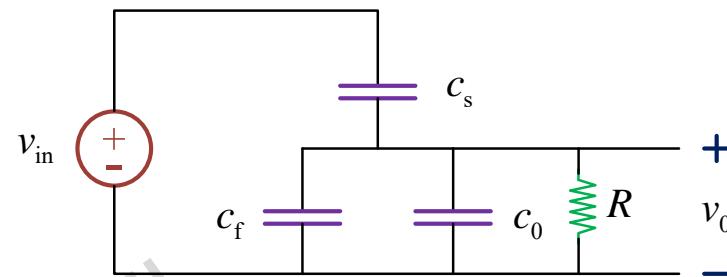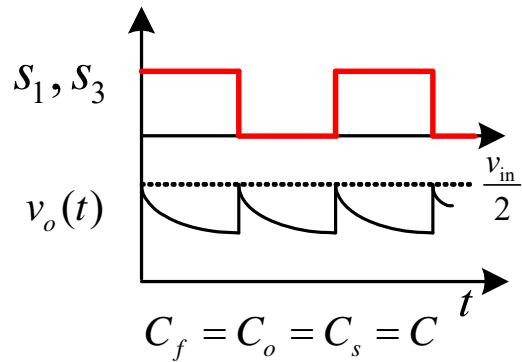


Discharging phase of flying cap

- ❑ Voltage ripple – load dependent
- ❑ Poor line & load regulation
- ❑ Inrush current during switching


## Basic Switch Capacitor Configurations

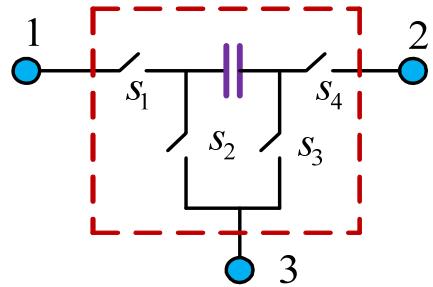

Basic switch cap cell

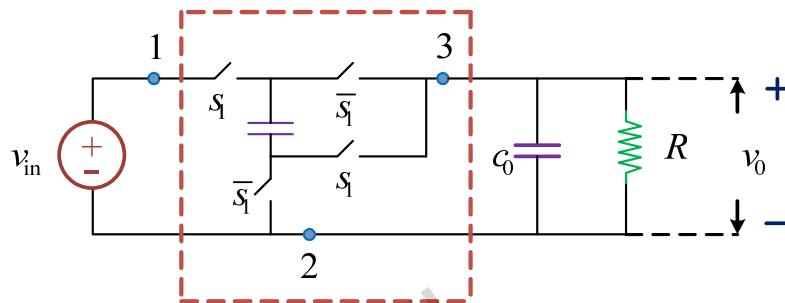

Step-down switch cap converter

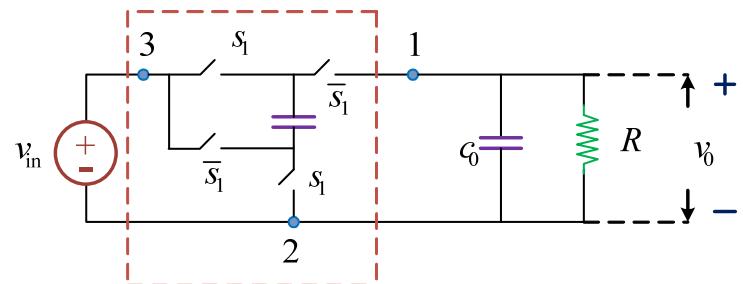


Step-up switch cap converter

❑ Step-up and step-down voltage


regulation possible, however,

voltage gain is factor of 2

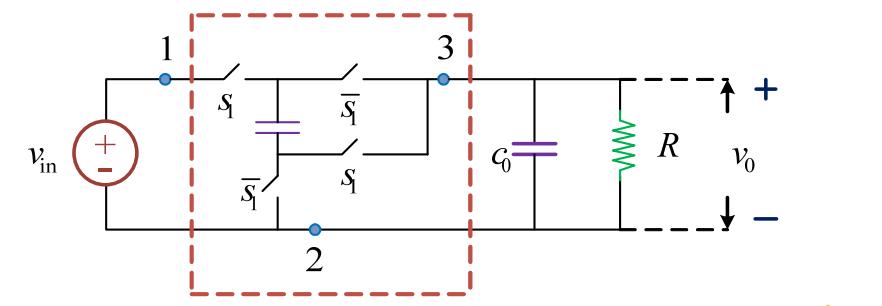
# Hybrid Step-down Switch Capacitor Converter



## Redrawing

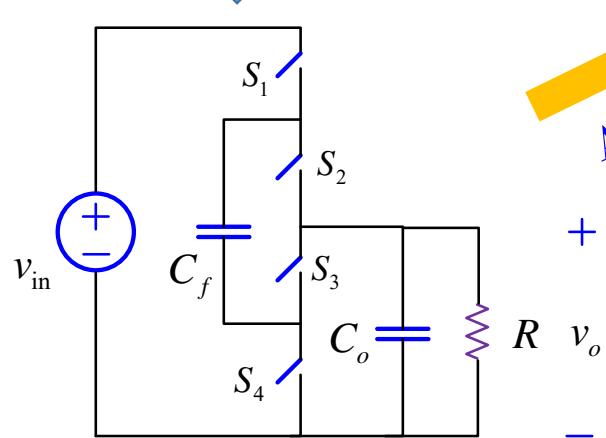


Adding a small  
inductor

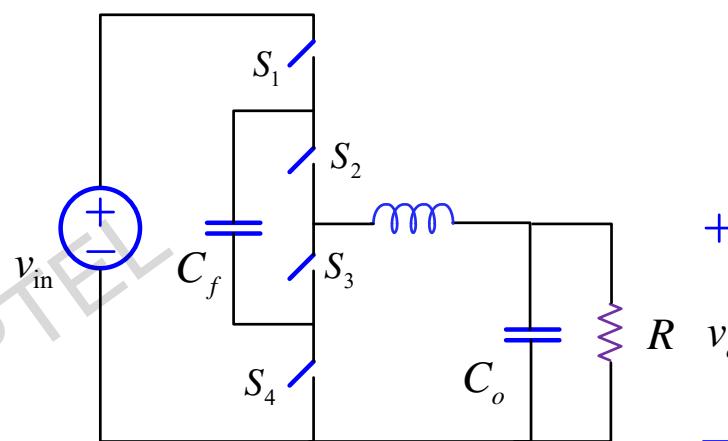


# Hybrid switch cap step-down converter

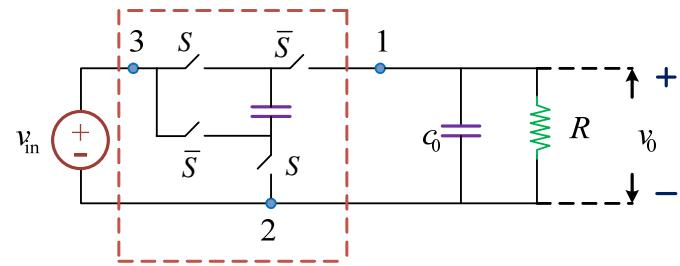
## Hybrid Step-up Switch Capacitor Converter



Redrawing

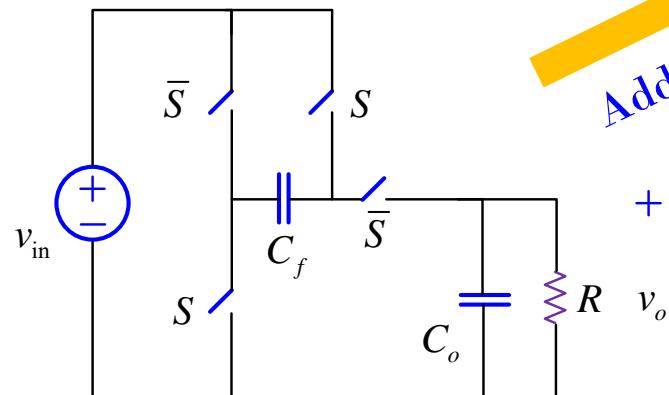

Adding a small  
inductor

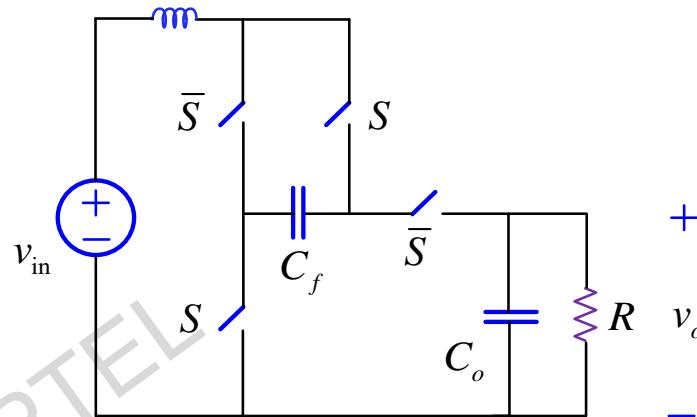


Hybrid switch cap  
step-up converter


## Switched Capacitor Voltage Regulators – Summary

- ❑ Switch cap VR – more efficient & higher power than LDO, step-up possible
- ❑ Switch cap VR – poor line/load regulation, poor efficiency for varying D
- ❑ Hybrid switch cap VR – superior efficiency/regulation, step-up/down conv.
- ❑ Hybrid switch cap VR – many switches, voltage balance control of  $C_f$
- ❑ Hybrid switch cap VR – research opportunities on control & optimization

## Inductive Step-down Converter

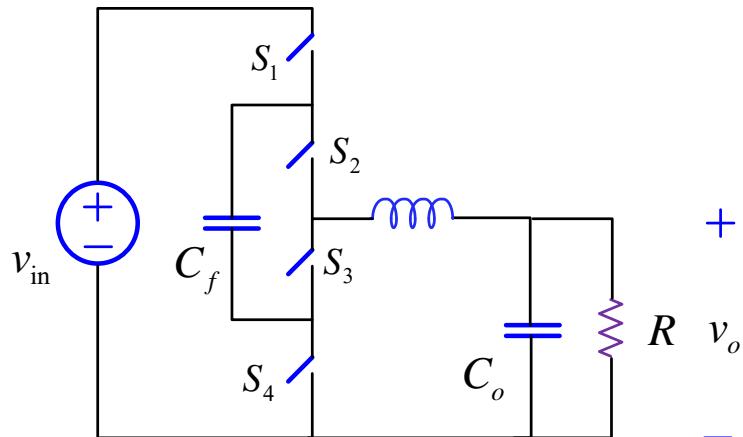


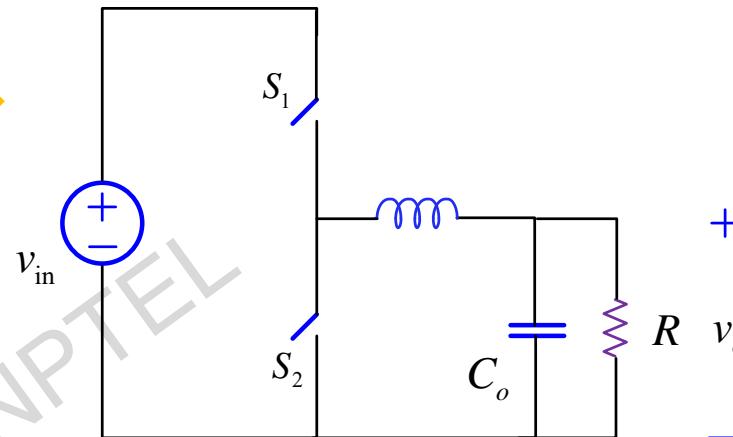Hybrid switch cap step-down  
converter with capacitive energy  
transfer and small inductor




Inductive step-down converter  
(known as buck converter) with  
inductive energy transfer

## Inductive Step-up Converter

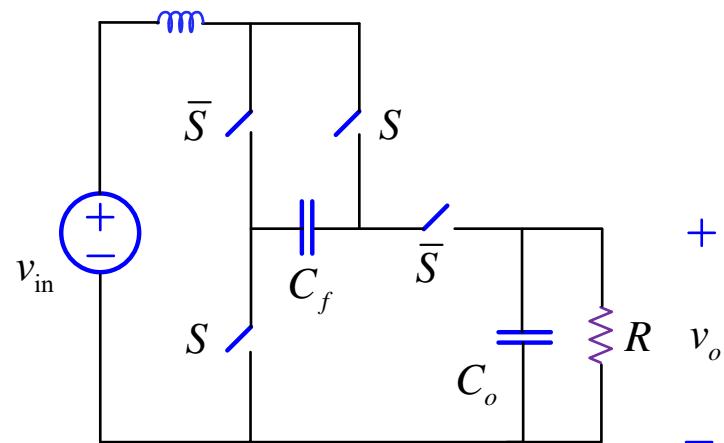

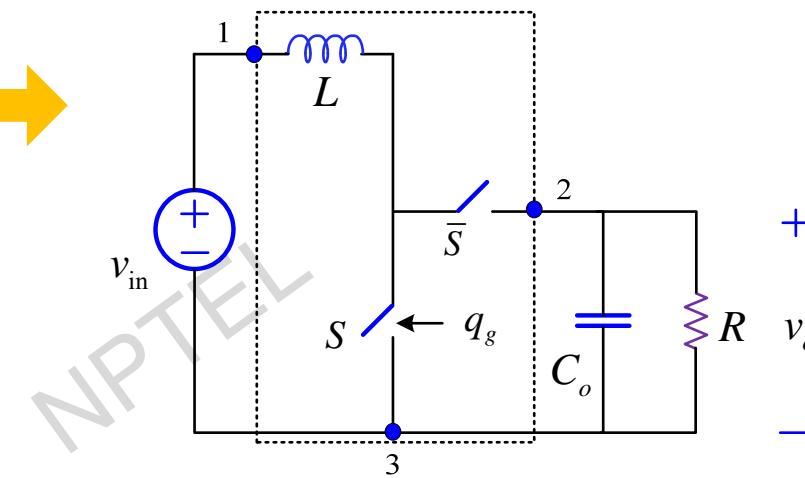Hybrid switch cap step – up  
converter with capacitive energy  
transfer and small inductor



Inductive step – up converter  
(known as boost converter) with  
inductive energy transfer

# Summary of Concepts

- Linear voltage regulators – suitable for ultra-low power applications
- Linear regulators – not suitable for higher power or step-up purposes
- Pure switched capacitor (SC) converters – not suitable at high power
- Hybrid SC converters – challenging, but emerging architectures
- Inductive converters – dominate in commercial products





NPTEL ONLINE CERTIFICATION COURSES

# CONTROL AND TUNING METHODS IN SMPCs

Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR

Module 01: Switched Mode Power Converters and Simulation


Lecture 03: Switched mode power converter (SMPC)

# Concepts Covered

- Basic DC-DC converters
- Step-down converter
- Step-up converter
- Step-up/down converter
- Basics of isolated DC-DC converters


NPTEL

## Step-down Converter (Buck Converter)

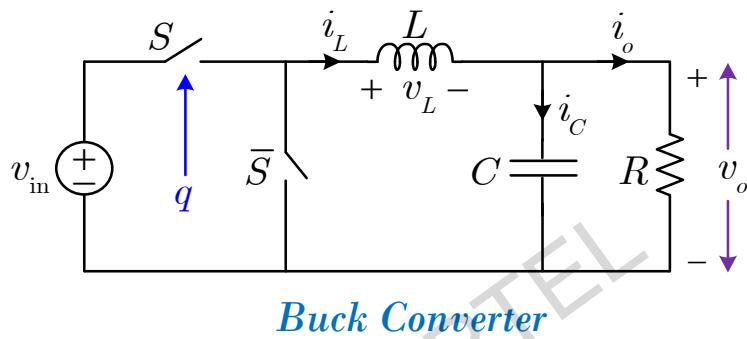


- $S$  and  $\bar{S}$  → single-pole single throw switches
- $S$  and  $\bar{S}$  → in complementary fashion
- $q \rightarrow$  command signal to turn ON or OFF of  $S$


If S on and  $\bar{S}$  off

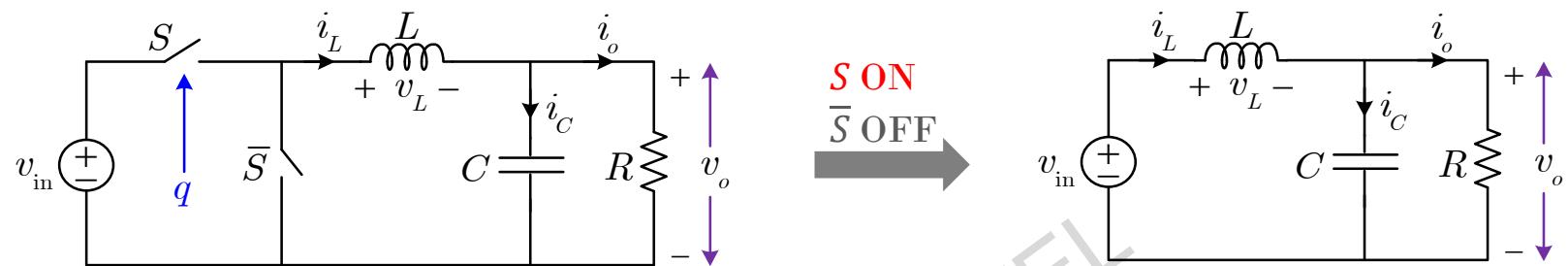


If S off and  $\bar{S}$  on

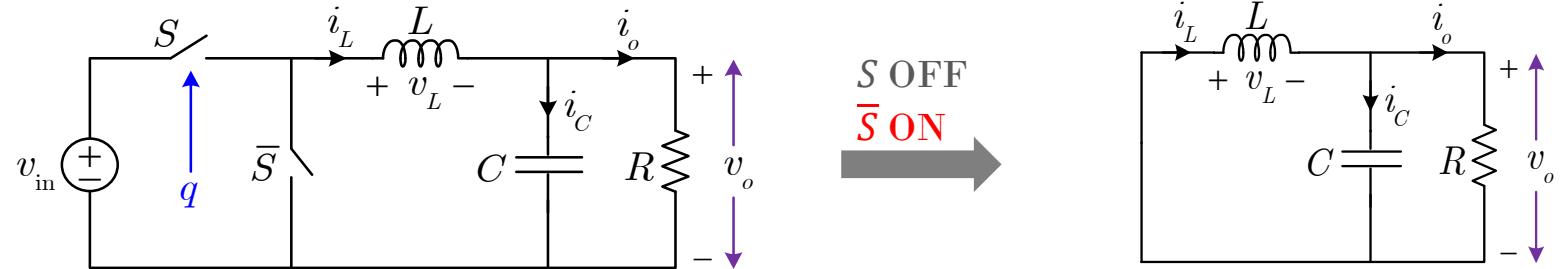

## Overall Operation

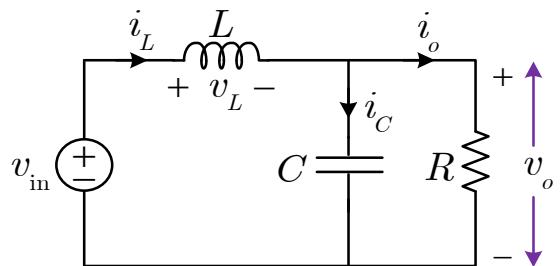


Mode 1:  $S$  - ON

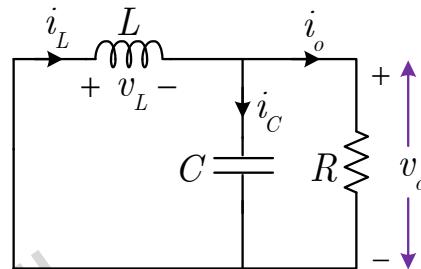

Mode 2:  $S$  - OFF

- None of the above configurations alone can achieve  $0 < v_o < v_{in}$
- ❑ Question: How can we achieve  $0 < v_o < v_{in}$  in finite time?

## Switching between Two Configurations

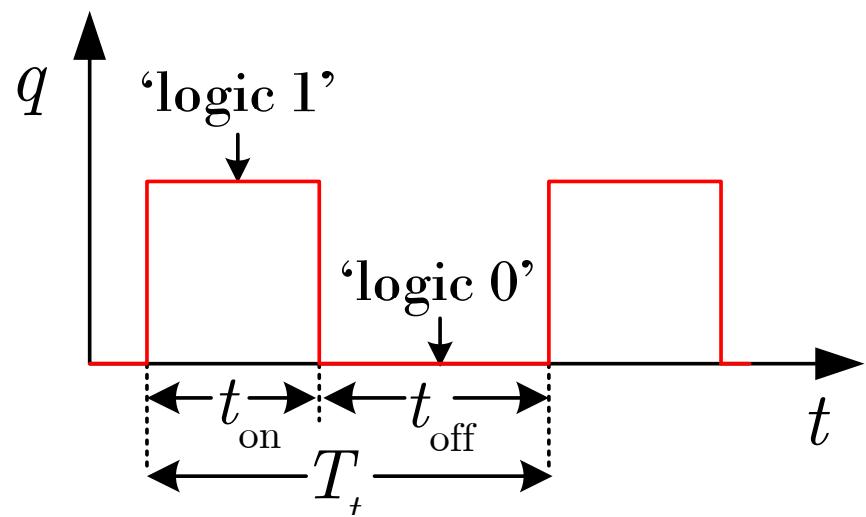


$t_{\text{on}} \rightarrow$  On-time of switch  $S$

$t_{\text{off}} \rightarrow$  Off-time of switch  $S$

$T_t \rightarrow$  total time in a periodic cycle

$$T_t = t_{\text{on}} + t_{\text{off}}$$
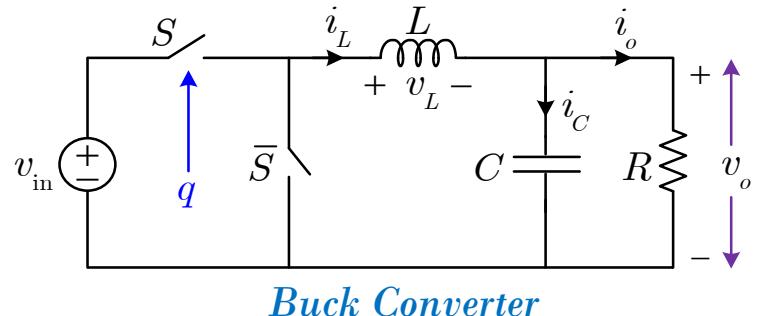
## Volt-Second Balance in a Buck Converter



$$v_L = \begin{cases} v_{\text{in}} - v_o & (q = 1) \\ -v_o & (q = 0) \end{cases}$$

$$\langle v_L \rangle_{T_t} = \frac{1}{T_t} \int_0^{T_t} v_L(t) dt$$

Steady-state notations:

$$\langle v_L \rangle_{T_t} \triangleq V_L \quad t_{\text{on}} \triangleq T_{\text{on}}$$

$$\langle v_{\text{in}} \rangle_{T_t} \triangleq V_{\text{IN}} \quad t_{\text{off}} \triangleq T_{\text{off}}$$

$$\langle v_o \rangle_{T_t} \triangleq V_o \quad T_t \triangleq T_{\text{sw}}$$

$$\langle i_L \rangle_{T_t} \triangleq I_L \quad f_{\text{sw}} = \frac{1}{T_{\text{sw}}}$$

$$\langle i_o \rangle_{T_t} \triangleq I_o$$

## Volt-Second Balance and Charge Balance (contd...)



- At steady-state:

$$V_L = \frac{1}{T_{\text{sw}}} [ (V_{\text{IN}} - V_O) T_{\text{on}} + (-V_O) T_{\text{off}} ] = 0$$


$$\Rightarrow V_O = \left( \frac{T_{\text{on}}}{T_{\text{on}} + T_{\text{off}}} \right) \times V_{\text{IN}}$$

$$I_C = (I_L - I_O) = 0$$

$$\Rightarrow I_L = I_O$$

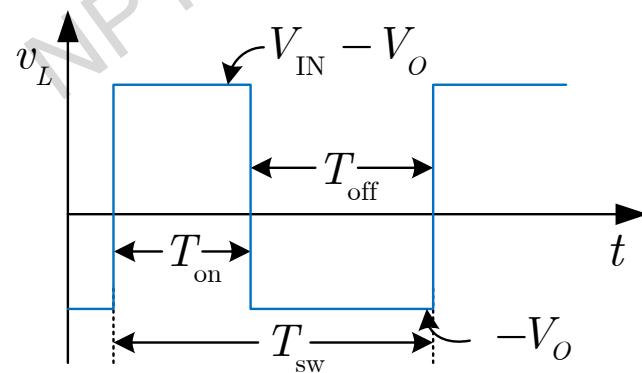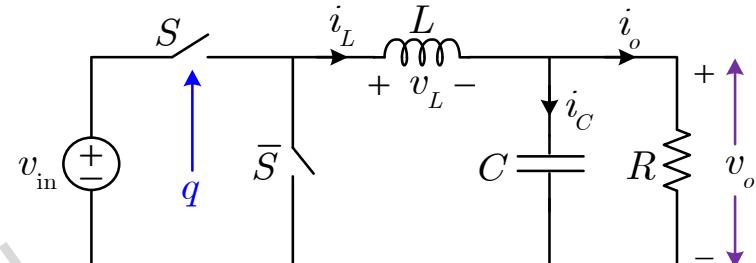


## Step-up (Boost) Converter

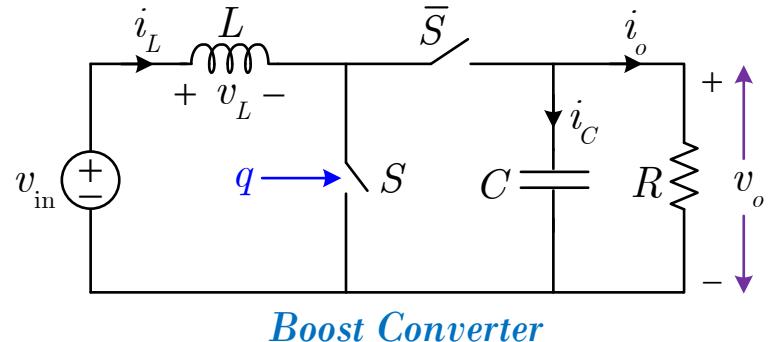

$$v_L = \begin{cases} v_{\text{in}} & (q = 1) \\ v_{\text{in}} - v_o & (q = 0) \end{cases}$$
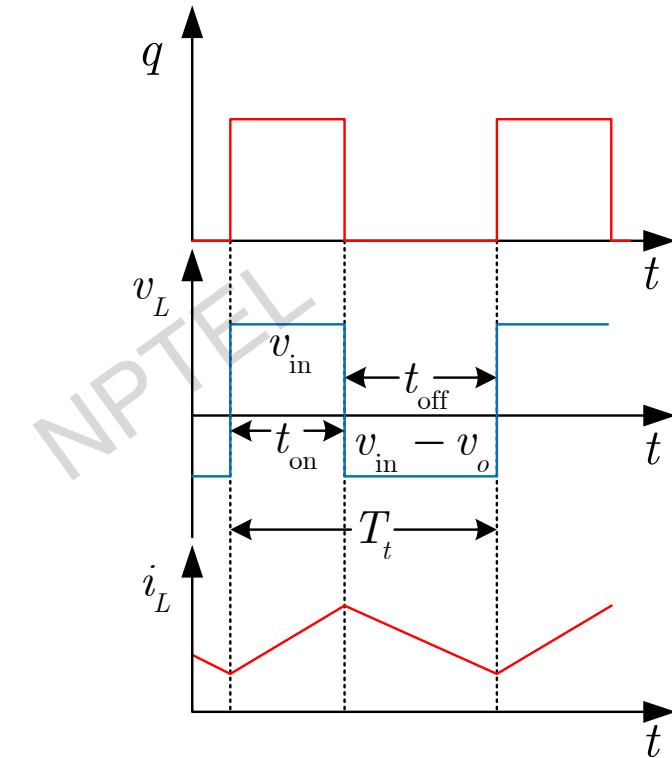
$$i_c = \begin{cases} -i_o & (q = 1) \\ i_L - i_o & (q = 0) \end{cases}$$



## Boost Converter (contd...)

Steady-state notations:


$$\langle v_L \rangle_{T_t} \triangleq V_L \quad t_{on} \triangleq T_{on}$$

$$\langle v_{in} \rangle_{T_t} \triangleq V_{IN} \quad t_{off} \triangleq T_{off}$$

$$\langle v_o \rangle_{T_t} \triangleq V_o \quad T_t \triangleq T_{sw}$$

$$\langle i_L \rangle_{T_t} \triangleq I_L \quad f_{sw} = \frac{1}{T_{sw}}$$
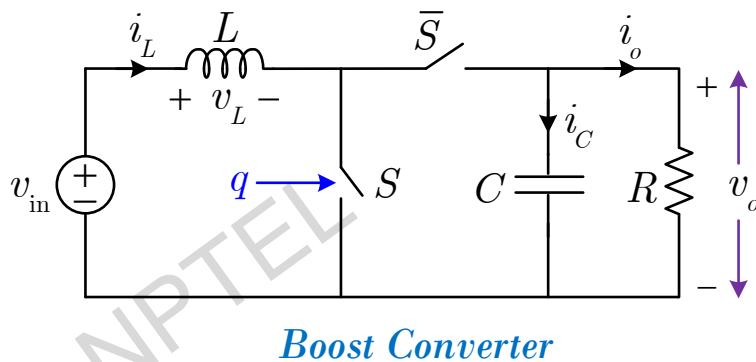
$$\langle i_o \rangle_{T_t} \triangleq I_o$$



*Boost Converter*

## Boost Converter (contd...)



- At steady-state:

$$V_L = \frac{1}{T_{\text{sw}}} \left[ (V_{\text{IN}}) T_{\text{on}} + (V_{\text{IN}} - V_O) T_{\text{off}} \right] = 0$$

$$\Rightarrow V_O = \left( \frac{T_{\text{on}} + T_{\text{off}}}{T_{\text{off}}} \right) \times V_{\text{IN}}$$



$$I_C = \frac{1}{T_{\text{sw}}} \left[ (-I_O) T_{\text{on}} + (I_L - I_O) T_{\text{off}} \right] = 0$$
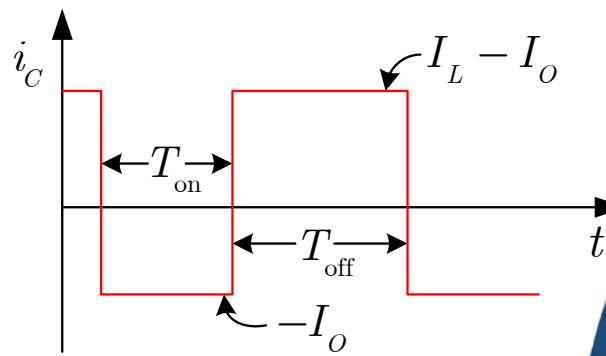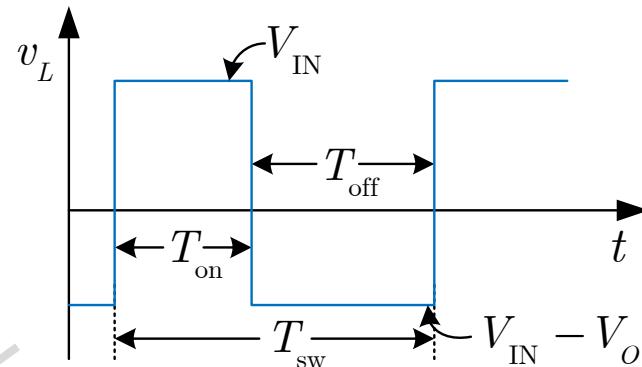
$$\Rightarrow I_L = \left( \frac{T_{\text{on}} + T_{\text{off}}}{T_{\text{off}}} \right) \times I_O$$


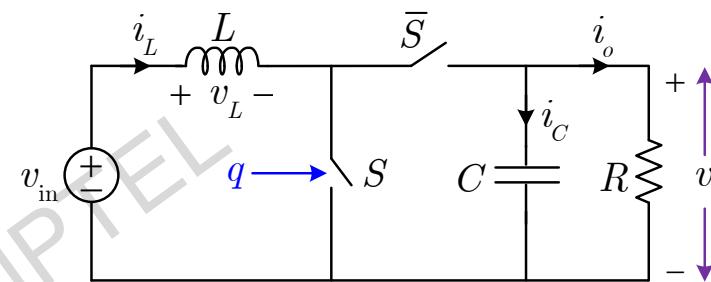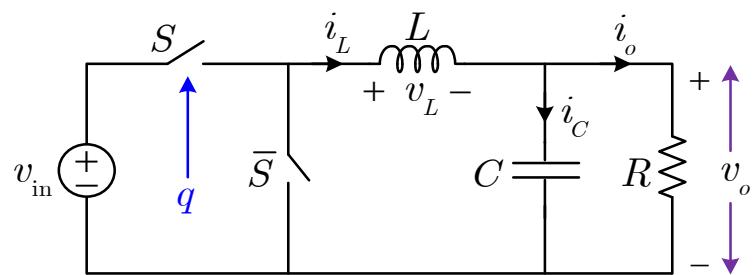
## Voltage Gain and Voltage Regulation

- Steady-state voltage gain,  $K_V = \frac{V_o}{V_{IN}}$



$$K_V = \left( \frac{T_{on}}{T_{on} + T_{off}} \right)$$

$$K_V = \left( \frac{T_{on} + T_{off}}{T_{off}} \right)$$

## Voltage Regulation — Degree of Freedom

- Voltage regulation in both cases is achieved by
  - a) Adjusting  $T_{\text{on}}$  by keeping  $T_{\text{sw}}$  constant
    - Control variable  $\frac{T_{\text{on}}}{T_{\text{sw}}} = D$  (duty ratio)
    - Known as pulse width modulation (PWM)

## Voltage Regulation — Degree of Freedom (contd...)

b) Adjusting  $T_{\text{on}}$  by keeping  $T_{\text{off}}$  constant

- Off-time constant i.e.  $T_{\text{off}} \triangleq T_c$
- Control variable  $\rightarrow t_{\text{on}}$
- Time period,  $T_{\text{sw}} = T_{\text{on}} + T_c$ , varies with voltage gain as


$$T_{\text{sw}} = \begin{cases} \frac{1}{1 - K_V} \times T_{\text{off}} & \text{Buck} \\ K_V \times T_{\text{off}} & \text{Boost} \end{cases}$$

- Known as constant off-time modulation

## Voltage Regulation — Degree of Freedom (contd...)


- c) Adjusting  $T_{\text{off}}$  by keeping  $T_{\text{on}}$  constant
  - o On-time constant i.e.  $T_{\text{on}} \triangleq T_c$
  - o Control variable  $\rightarrow t_{\text{off}}$
  - o Time period  $T_{\text{sw}} = T_{\text{off}} + T_c$ , varies with voltage gain as
$$T_{\text{sw}} = \begin{cases} \frac{1}{K_V} \times T_{\text{on}} & \text{Buck} \\ \frac{K_V}{K_V - 1} \times T_{\text{on}} & \text{Boost} \end{cases}$$
  - o Known as constant on-time modulation

## Buck-boost Converter

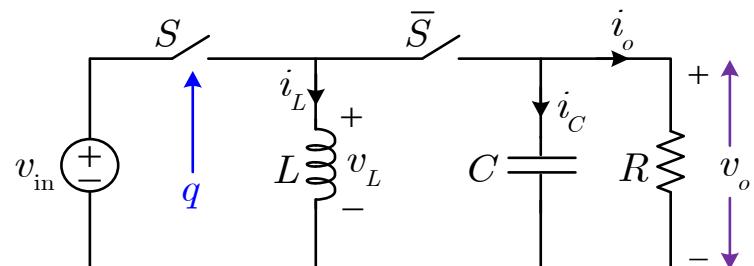

*Buck-Boost Converter*
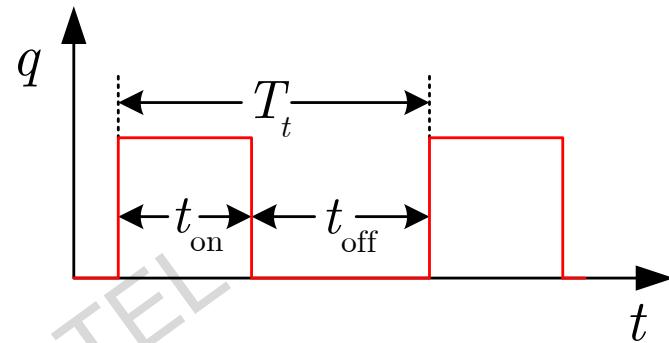
$$v_L = \begin{cases} v_{in} & (q = 1) \\ v_o & (q = 0) \end{cases}$$



Steady-state notations:

$$\begin{aligned} \langle v_L \rangle_{T_t} &\triangleq V_L & t_{on} &\triangleq T_{on} \\ \langle v_{in} \rangle_{T_t} &\triangleq V_{IN} & t_{off} &\triangleq T_{off} \\ \langle v_o \rangle_{T_t} &\triangleq V_O & T_t &\triangleq T_{sw} \end{aligned}$$



## Buck-boost Converter (contd...)

- At steady-state:

$$V_L = \frac{1}{T_{\text{sw}}} [V_{\text{IN}} T_{\text{on}} + V_O T_{\text{off}}] = 0 \quad \Rightarrow V_O = - \left( \frac{T_{\text{on}}}{T_{\text{off}}} \right) \times V_{\text{IN}}$$

- Output voltage is negative
- Magnitude of  $V_O$  can be higher, lower or equal to  $V_{\text{IN}}$
- Other buck-boost converters available with positive output voltage
- Non-inverting buck-boost  $\rightarrow$  a potential low power candidate

## Non-inverting Buck-boost Converter

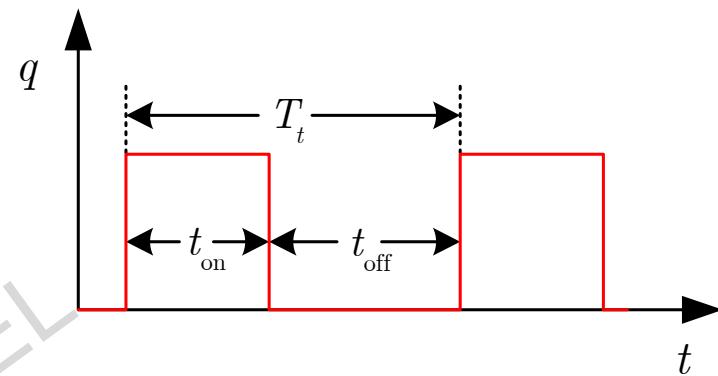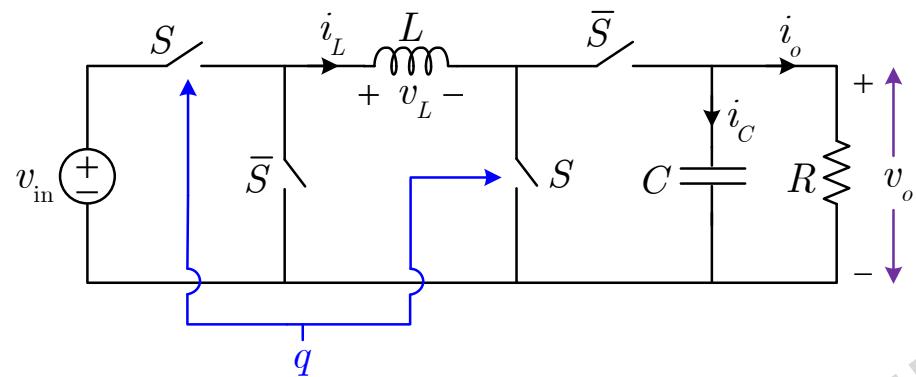


- Voltage across the inductor

$$v_L = \begin{cases} v_{in} & \text{for } q = 1 \\ -v_o & \text{for } q = 0 \end{cases}$$




Derive steady-state  
voltage gain

## Introduction to Isolated SMPC

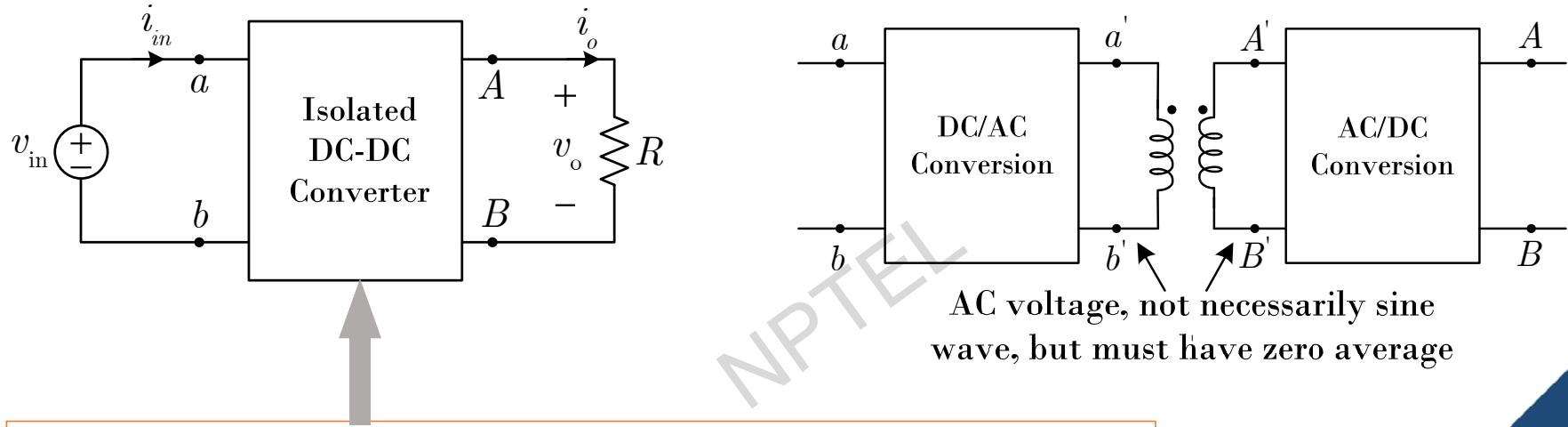


- Transformer used for galvanic isolation
- Transformer can not be directly used with a DC source

## Possible DC/ AC Configurations

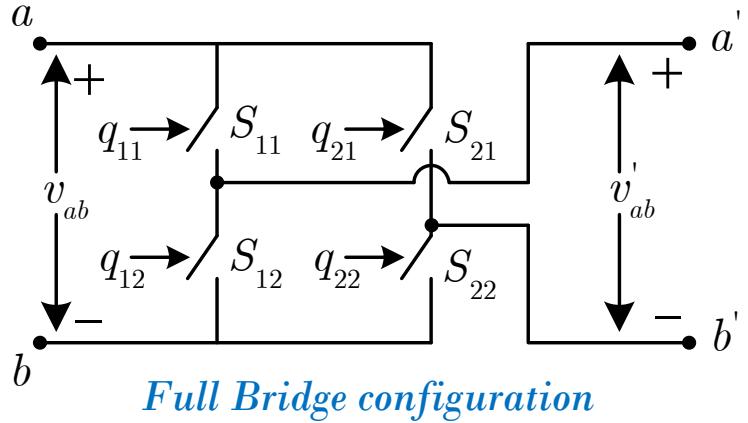

*Full Bridge configuration*
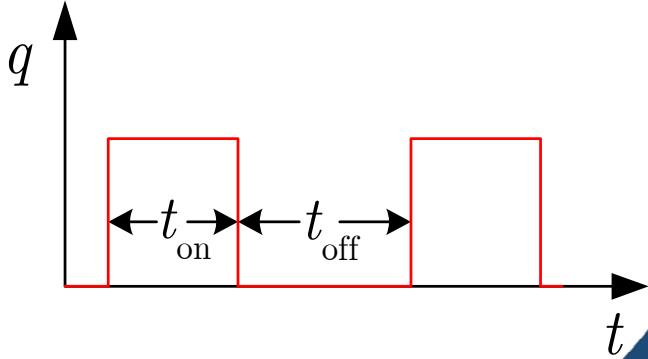
$$\begin{aligned} q_{12} &= \bar{q}_{11} \\ q_{22} &= \bar{q}_{21} \\ q_{11} = q_{22} &\triangleq q \end{aligned}$$




$$\text{For } q=1: \quad v'_{ab} = v_{ab}$$


$$\text{For } q=0: \quad v'_{ab} = -v_{ab}$$
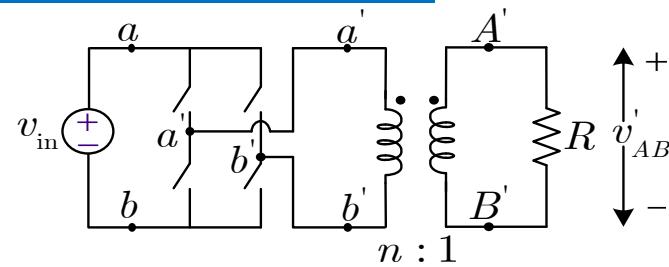
## Connect to the Transformer


Consider a diode bridge rectifier in the secondary side of the transformer




Consider an output filter

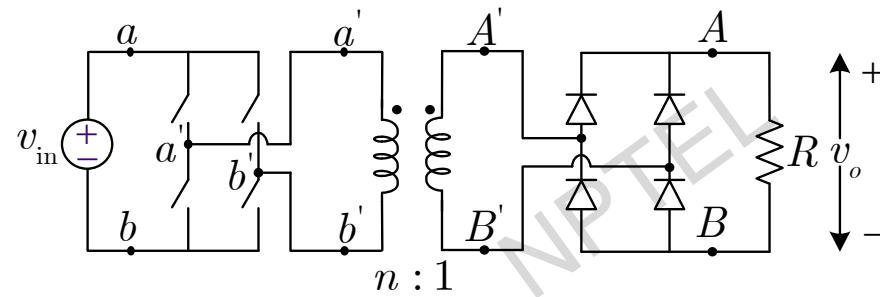

Full Bridge DC-DC Converter

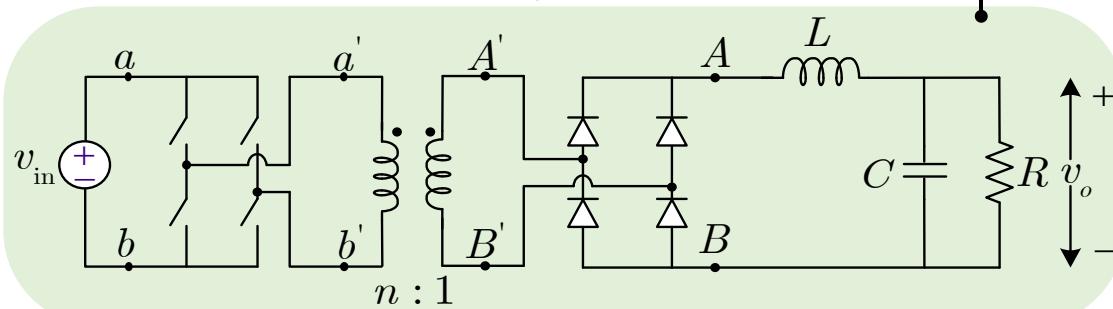


## Buck-boost Converter Isolated Version

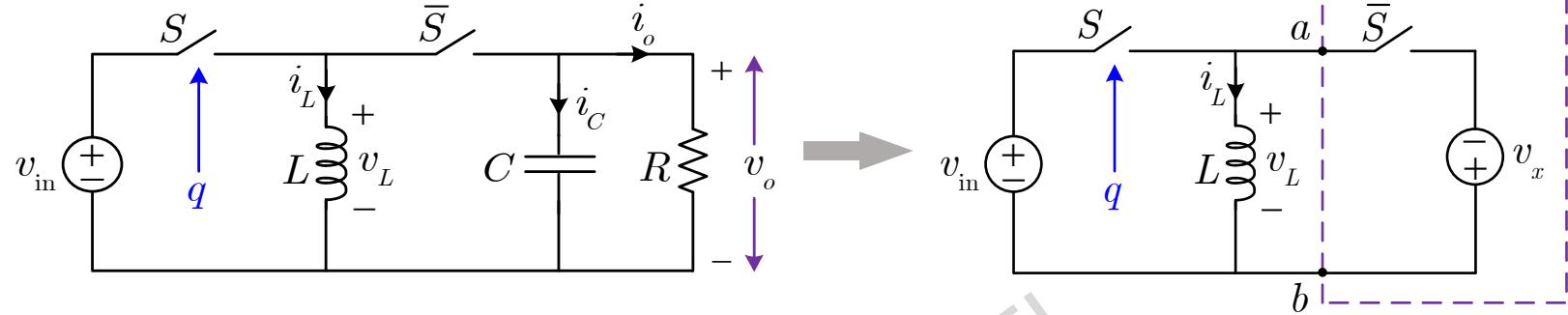


1. Start with a buck-boost converter
2. Replace capacitor and resistance at the output side with a floating voltage  $v_x$

Can be replaced by a pulsating voltage
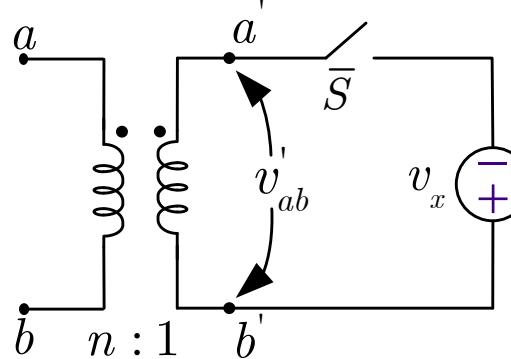
## Buck-boost Converter Isolated Version (contd...)



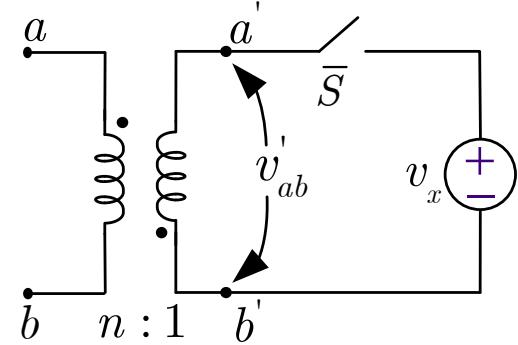Polarity of  $v_x$  can be changed by changing dot convention



When  $S$  ON ( $\bar{S}$  OFF)



$$v_{ab} = v_{in} \Rightarrow v'_{ab} = \frac{v_{ab}}{n}$$

$$v_L = \begin{cases} v_{in} & \text{for } q = 1 \\ -v_o & \text{for } q = 0 \end{cases}$$

When  $S$  OFF ( $\bar{S}$  ON)

$$v'_{ab} = -v_x \Rightarrow v_{ab} = -nv_x$$

## Overall Circuit

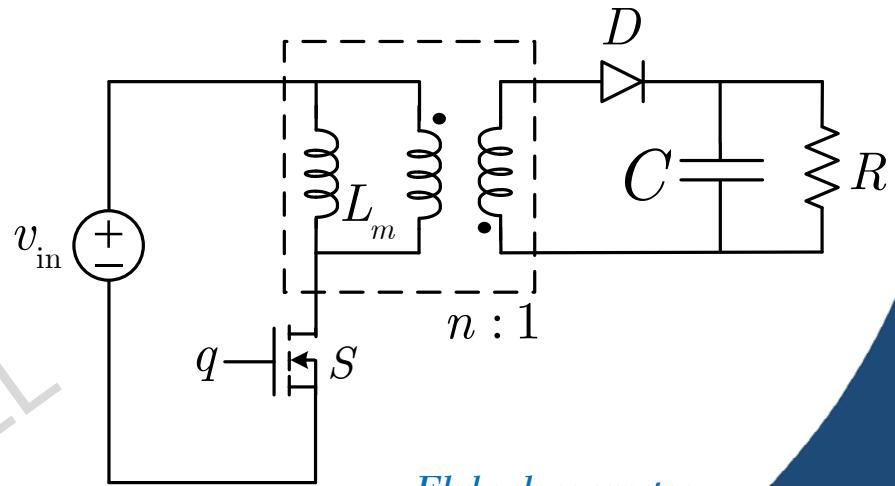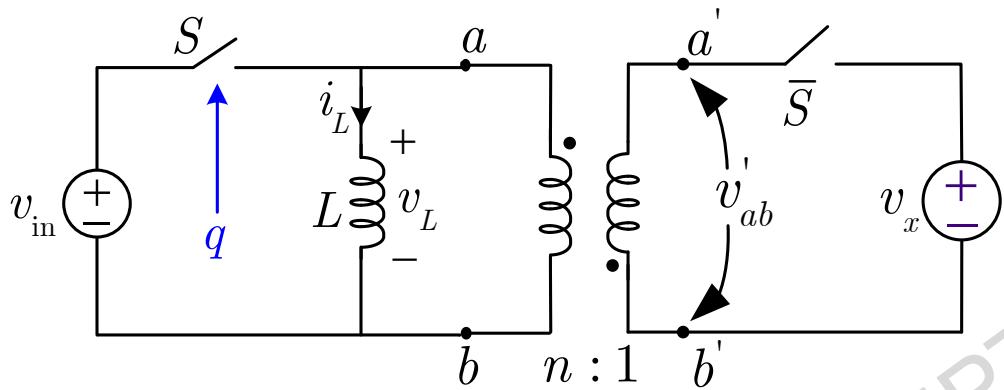

Flyback converter

- High side switch to low side switch
- Complementary switch replaced with a diode
- $v_x$  replaced by capacitor and resistance in parallel
- Inductor integrated as the magnetizing reactance

# Summary

- Buck converter → step down purpose
- Boost converter → step-up purpose
- Buck-boost converter → both step-up and step-down, but –ve polarity
- Non-inverting buck-boost → both step-up and step-down
- Flyback converter → Isolated buck-boost converter with +ve output





NPTEL ONLINE CERTIFICATION COURSES

# CONTROL AND TUNING METHODS IN SMPCs

Dr. Santanu Kapat

DEPARTMENT NAME, IIT KHARAGPUR

**Module 01: Switched Mode Power Converters and Simulation**

**Lecture 04: Model Development for MATLAB Simulation**

# Concepts Covered

- Modeling of a series RL circuit and block diagram for simulation
- Modeling of series and parallel RLC circuits along with parasitic
- Modeling of parallel RLC circuits with parasitic components
- Modeling of conventional and synchronous buck converters
- Modeling of a boost converter and model generalization

## Series RL Circuit


- Voltages

$$v_L = v_{\text{in}} - v_R \quad v_R = i_L \times R$$

$$v_L = (v_{\text{in}} - v_R) = (v_{\text{in}} - i_L R)$$

- Dynamics
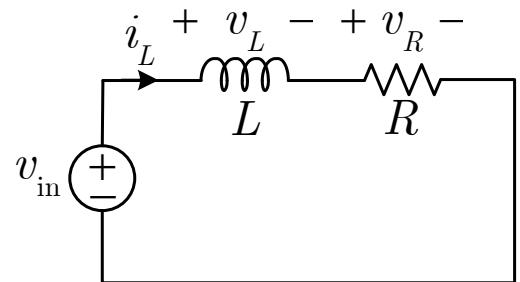
$$L \frac{di_L}{dt} = v_L = (v_{\text{in}} - i_L R)$$



## Series RL Circuit – Implementation




- Voltages

$$v_R = i_L \times R \quad \rightarrow \quad i_L \rightarrow R \rightarrow v_R$$

$$v_L = (v_{\text{in}} - v_R) \quad \rightarrow \quad v_{\text{in}} \rightarrow + \rightarrow v_L$$

- Dynamics
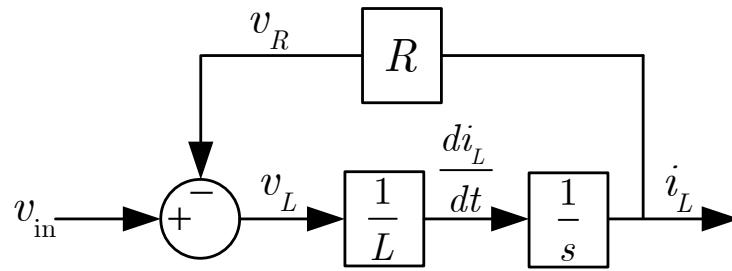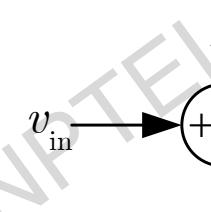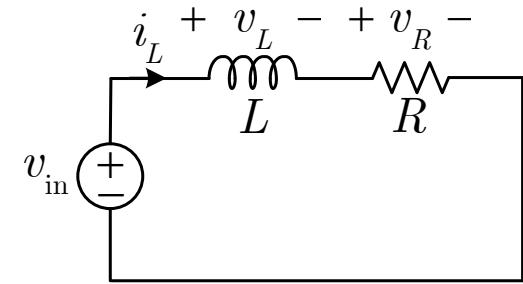
$$\frac{di_L}{dt} = \frac{1}{L} \times (v_{\text{in}} - i_L R) \quad \rightarrow \quad v_{\text{in}} \rightarrow + \rightarrow v_L \rightarrow \frac{1}{L} \rightarrow \frac{di_L}{dt} \rightarrow \frac{1}{s} \rightarrow i_L$$




## Series RLC Circuit

- Dynamics

$$\frac{di_L}{dt} = \frac{1}{L} \times (v_{\text{in}} - v_R - v_C)$$

$$\frac{di_L}{dt} = \frac{1}{L} \times (v_{\text{in}} - i_L R - v_C)$$

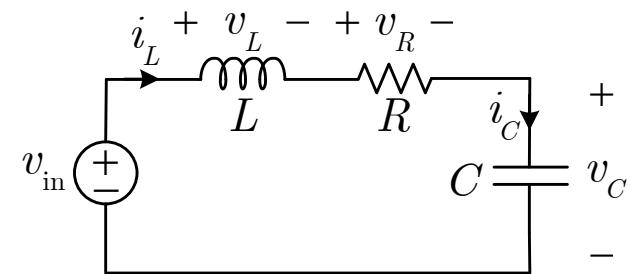
$$\frac{dv_C}{dt} = \frac{1}{C} \times i_L$$



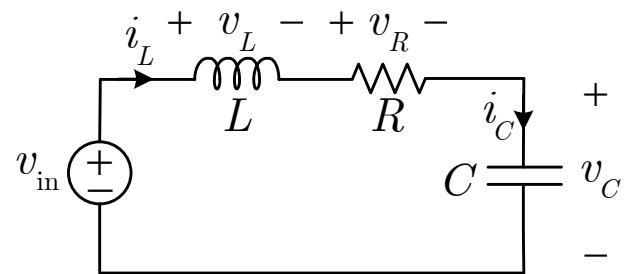
## Series RLC Circuit – Implementation

- Dynamics

$$\frac{dv_C}{dt} = \frac{1}{C} \times i_L \quad \rightarrow \quad i_L \rightarrow \left[ \frac{1}{C} \right] \frac{dv_C}{dt} \rightarrow \left[ \frac{1}{s} \right] \rightarrow v_C$$





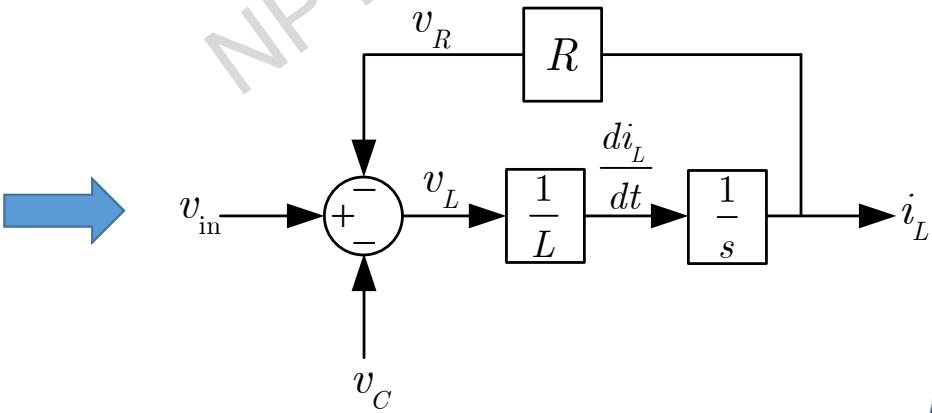
$$\frac{di_L}{dt} = \frac{1}{L} \times (v_{\text{in}} - i_L R - v_C) \quad \rightarrow \quad v_{\text{in}} \rightarrow + \text{ terminal} \rightarrow v_L \rightarrow \left[ \frac{1}{L} \right] \frac{di_L}{dt} \rightarrow \left[ \frac{1}{s} \right] \rightarrow i_L$$



## Series RLC Circuit – Implementation

- Complete Dynamics

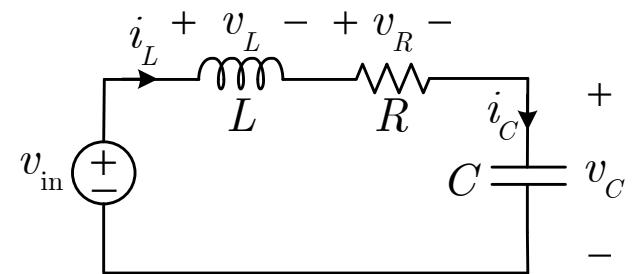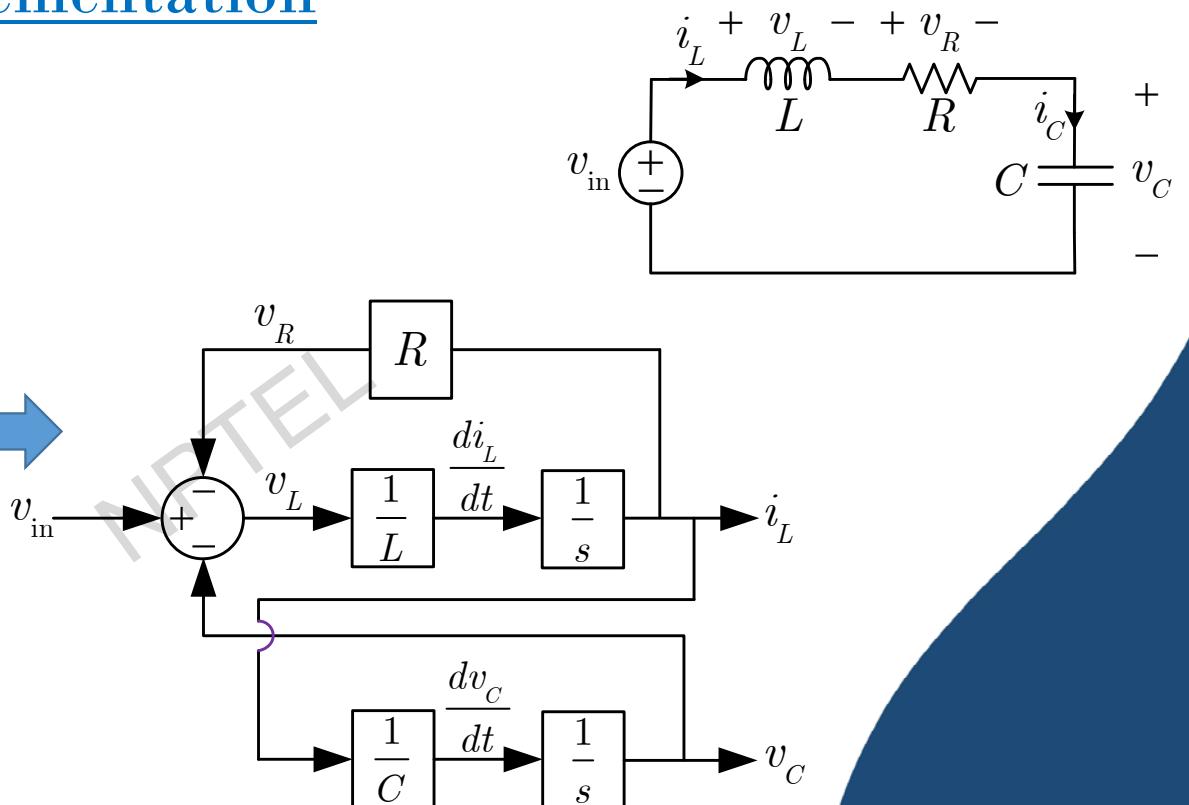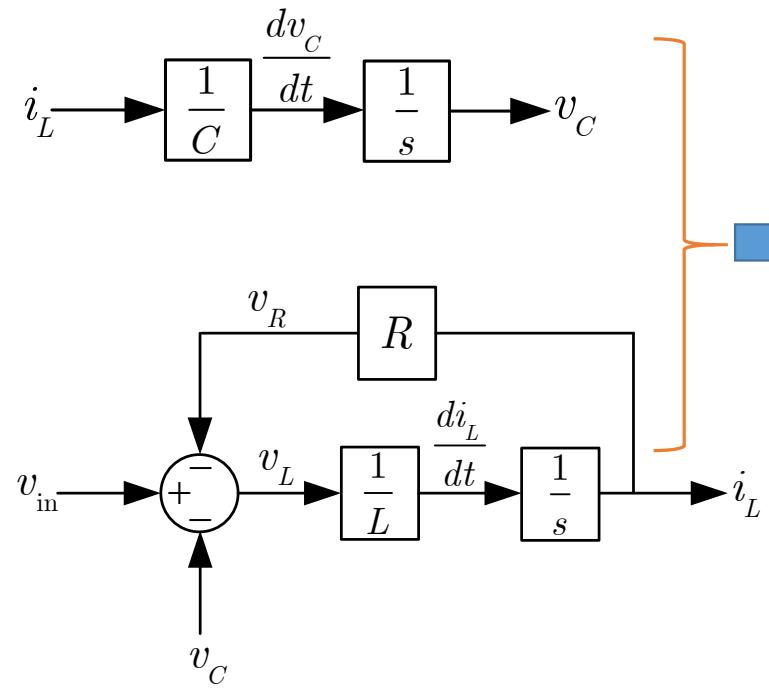



## Parallel RLC Circuit – Implementation

$$\frac{di_L}{dt} = \frac{1}{L} \times v_L = \frac{1}{L} \times (v_{\text{in}} - v_C)$$

$$\frac{dv_C}{dt} = \frac{1}{C} \times (i_L - i_o) \quad i_C$$

$$v_o = v_C$$

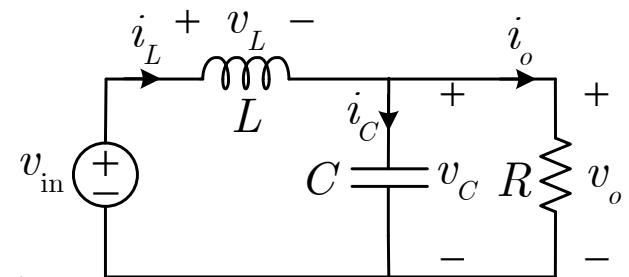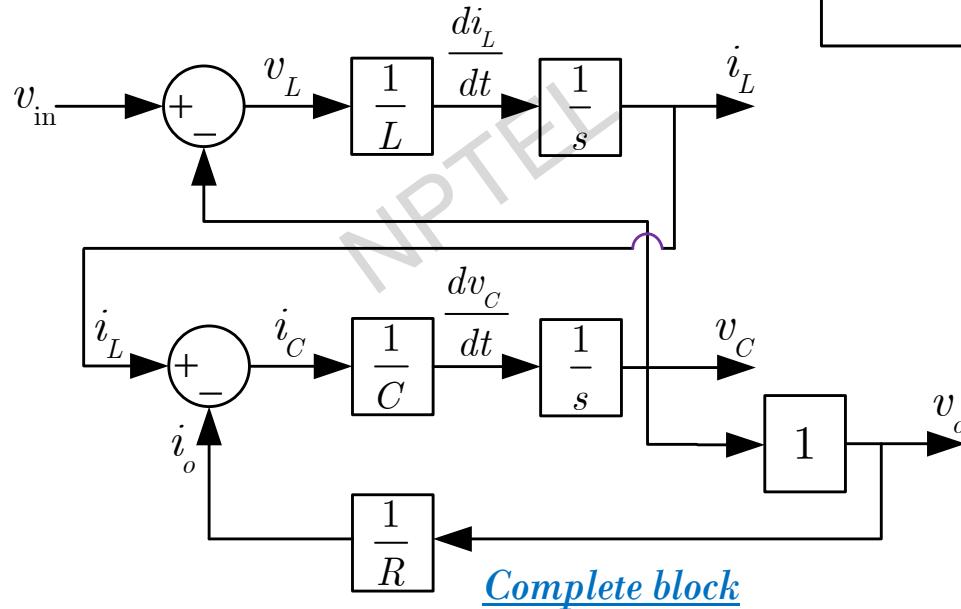
$$i_o = \left(\frac{1}{R}\right) \times v_o$$





## Parallel RLC Circuit with Parasitic Components

$$\frac{di_L}{dt} = \frac{1}{L} \times (v_{\text{in}} - i_L r_L - v_o)$$

$v_L$

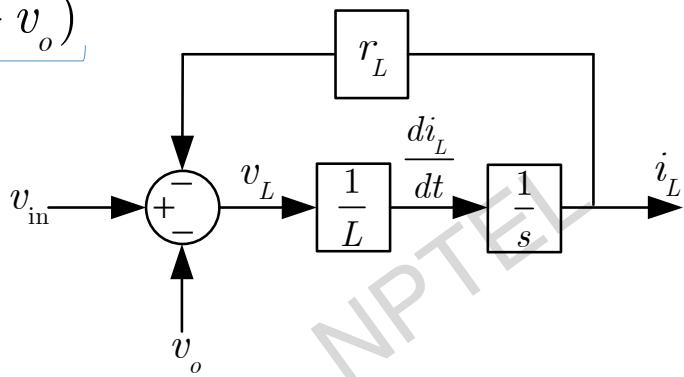
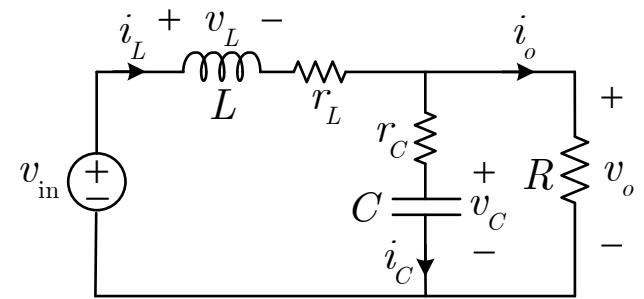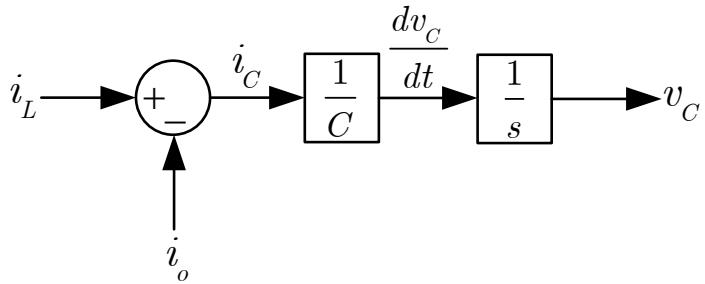
$$\frac{dv_C}{dt} = \frac{1}{C} \times (i_L - i_o)$$




## Parallel RLC Circuit with Parasitic Components


$$v_o = i_C r_C + v_C$$

$$i_C = i_L - i_o$$



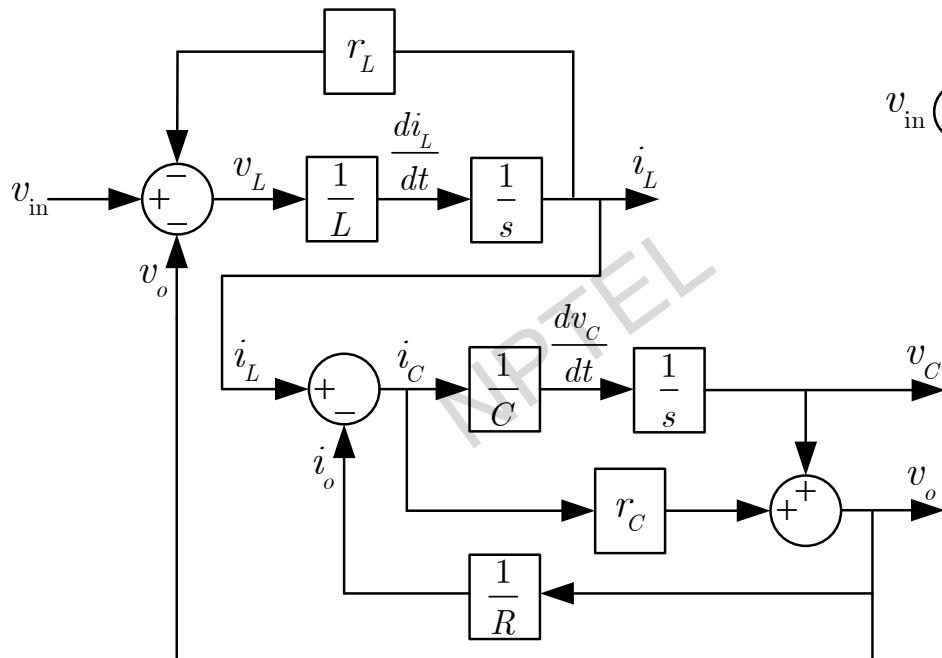
$$i_o = \left(\frac{1}{R}\right) \times v_o$$



Complete block


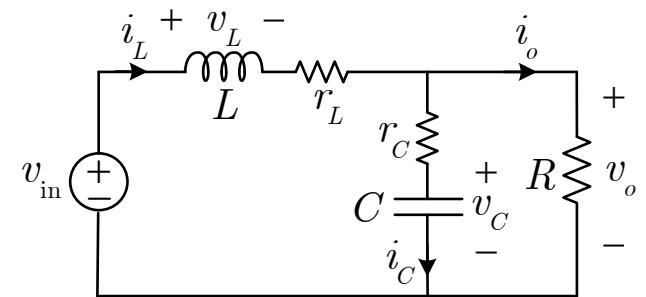


## Synchronous Buck Converter

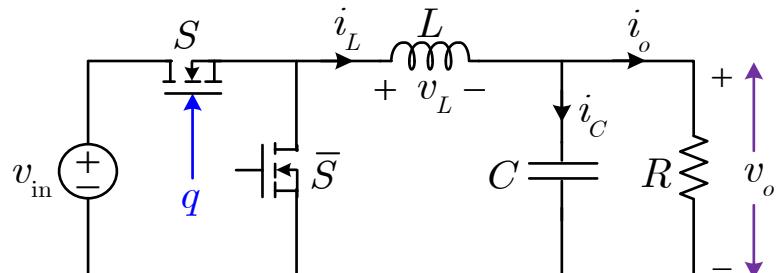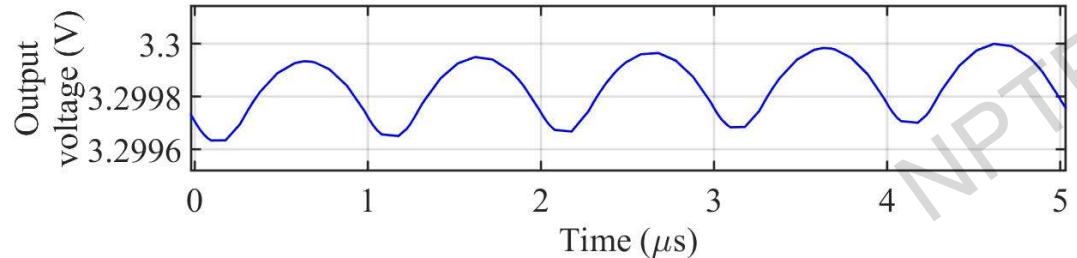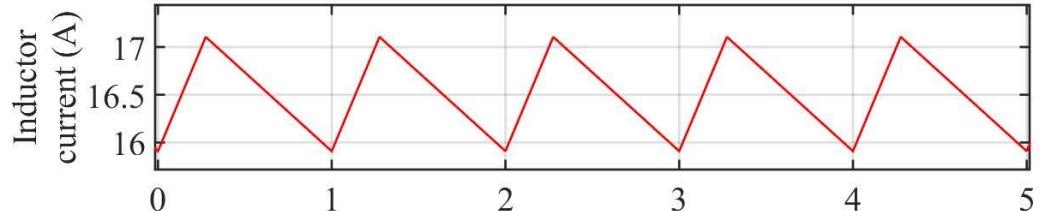

- ❑ Synchronous buck converter – always in continuous conduction mode (CCM)
- ❑ Inductor current can be negative under light load conditions

## Synchronous Buck Converter

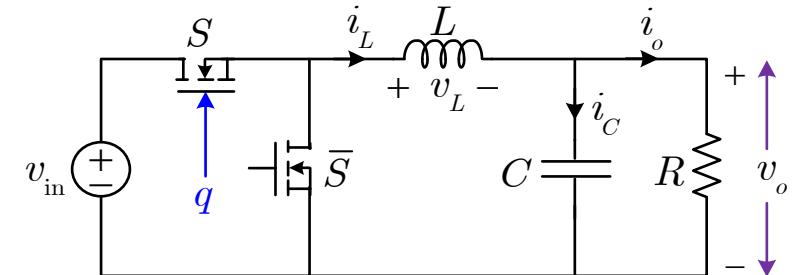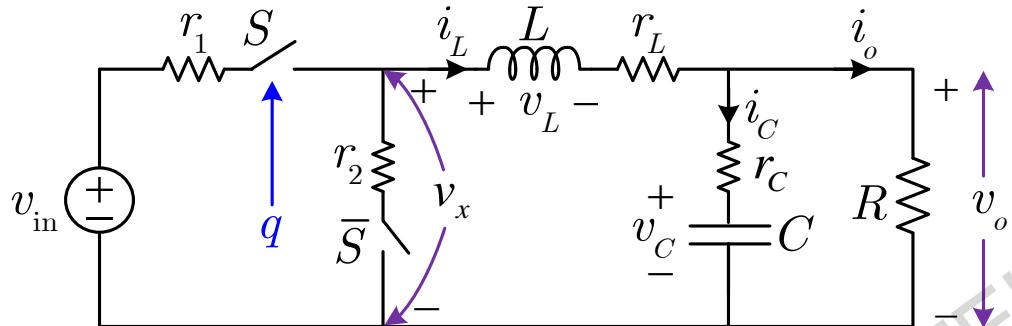

Replace real components  
with parasitic

$$\frac{di_L}{dt} = \frac{1}{L} \times \underbrace{(v_x - i_L r_L - v_o)}_{v_L}$$


$$i_C = i_L - i_o$$

$$v_x = q(v_{in} - i_L r_1) + (1 - q)(-i_L r_2)$$


$$\frac{dv_C}{dt} = \frac{1}{C} \times i_C$$

$$v_o = i_C r_C + v_C$$

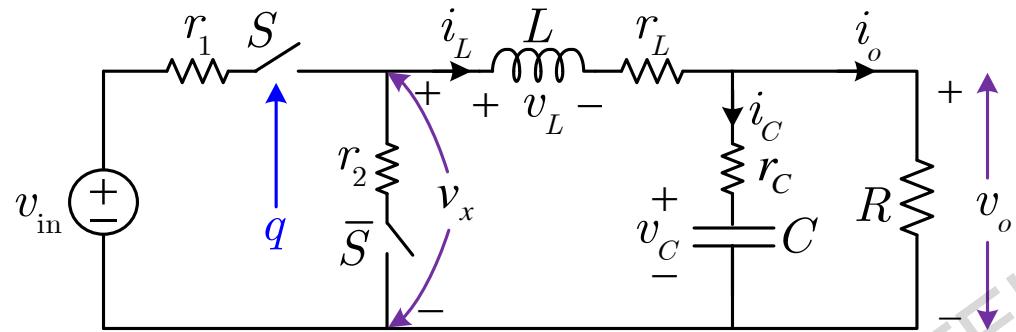
## Synchronous Buck Converter – Implementation


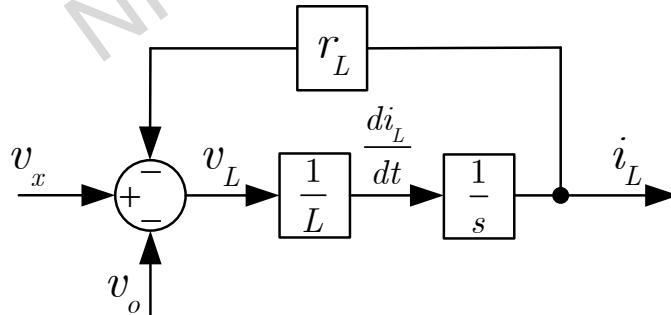
$$\frac{di_L}{dt} = \frac{1}{L} \times \underbrace{(v_x - i_L r_L - v_o)}_{v_L}$$


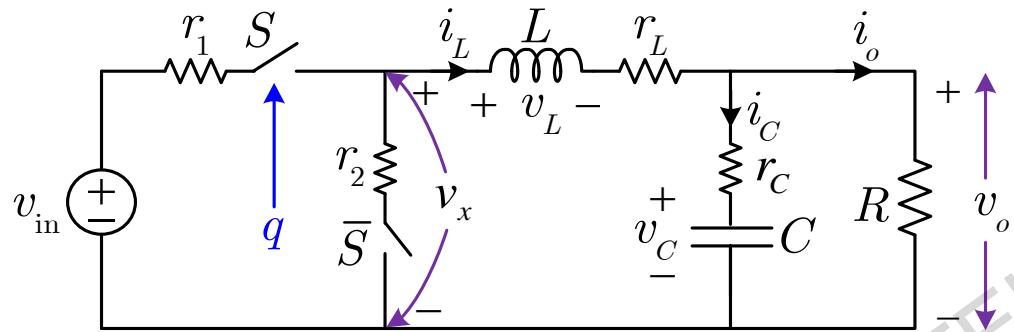
## Synchronous Buck Converter – Implementation



$$\frac{dv_C}{dt} = \frac{1}{C} \times i_C$$


$$i_C \rightarrow \left[ \frac{1}{C} \right] \frac{dv_C}{dt} \rightarrow \left[ \frac{1}{s} \right] v_C \rightarrow v_C$$

$$i_C = i_L - i_o$$


$$i_L \rightarrow + \quad i_C \rightarrow -$$

$i_o$


$$v_o = i_C r_C + v_C$$

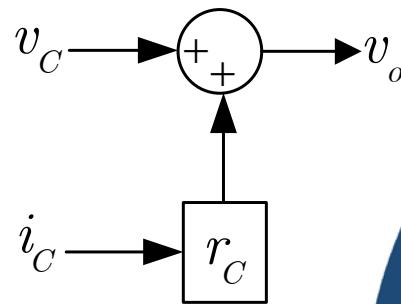
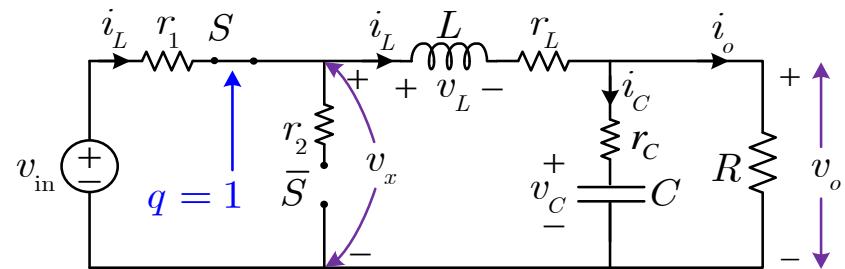
## Synchronous Buck Converter – Implementation




$$v_x = (v_{\text{in}} - i_L r_1)$$

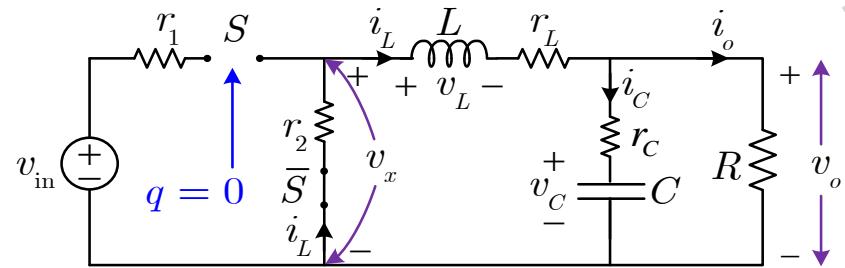


$$v_x = (-i_L r_2)$$


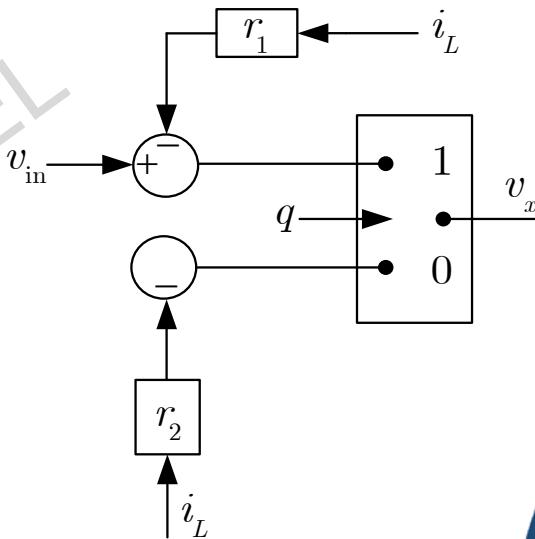
$$v_x = q(v_{\text{in}} - i_L r_1) + (1 - q)(-i_L r_2)$$


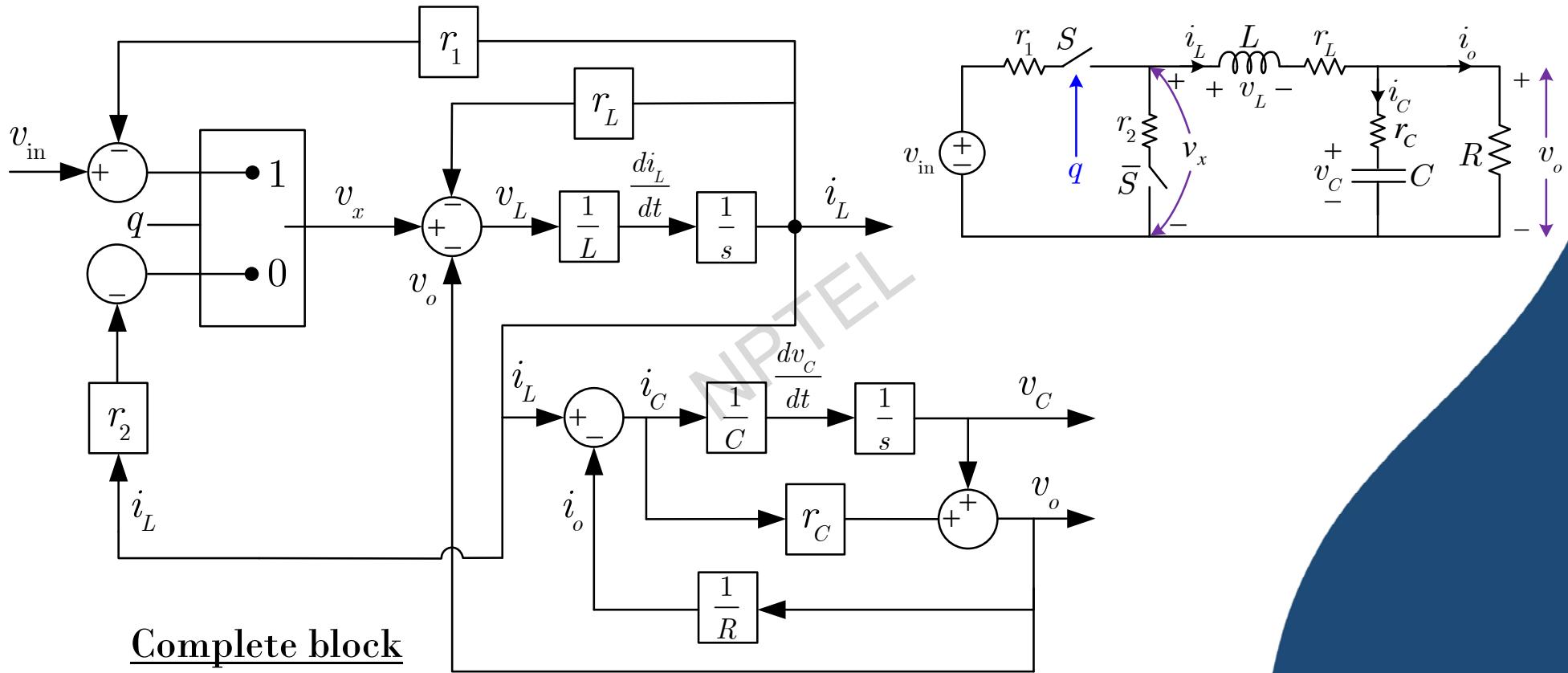
## Synchronous Buck Converter – Complete Implementation



## Conventional Buck Converter

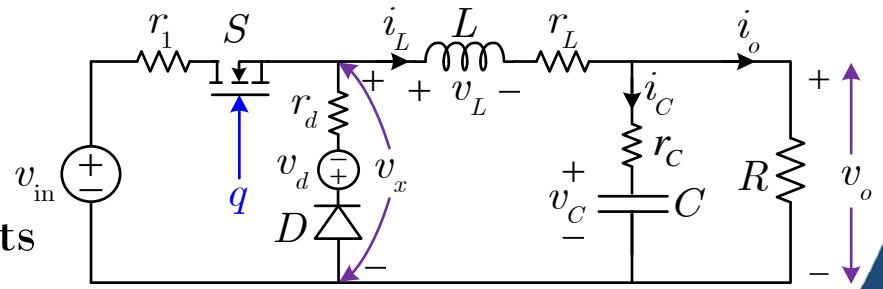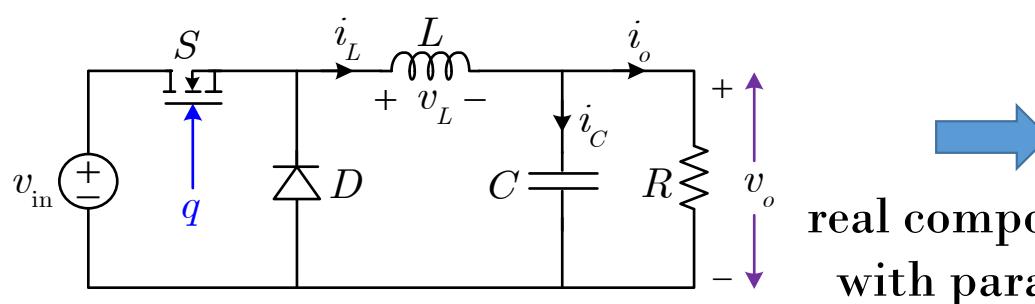

$$\frac{di_L}{dt} = \begin{cases} \frac{1}{L} \times (v_x - i_L r_L - v_o) & \text{for } i_L > 0 \\ 0 & \text{for } i_L \leq 0 \end{cases}$$


$$i_C = i_L - i_o$$

$$v_o = i_C r_C + v_C$$


$$\frac{dv_C}{dt} = \frac{1}{C} \times i_C$$

$$v_x = q(v_{in} - i_L r_1) + (1 - q)(-v_d - i_L r_d)$$
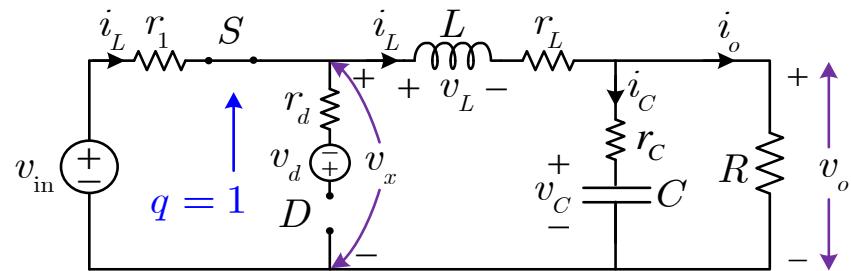
## Conventional Buck Converter – Implementation




$$v_x = (v_{in} - i_L r_1)$$

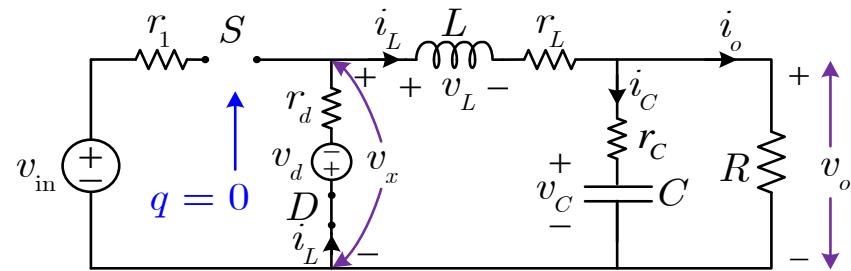


$$v_x = (-v_d - i_L r_d)$$
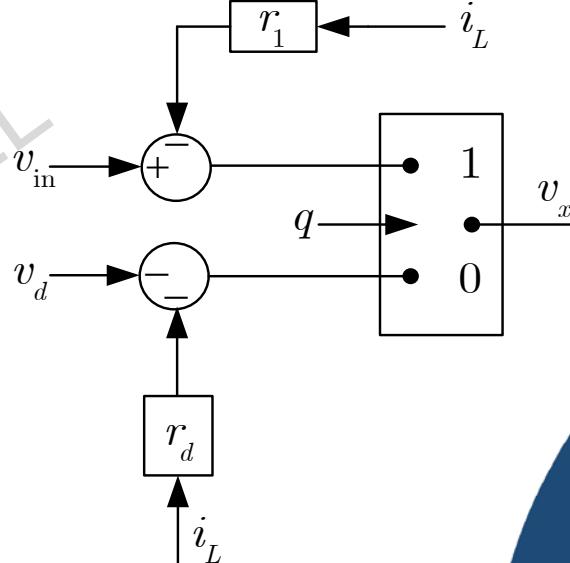
$$v_x = q(v_{in} - i_L r_1) + (1 - q)(-v_d - i_L r_d)$$



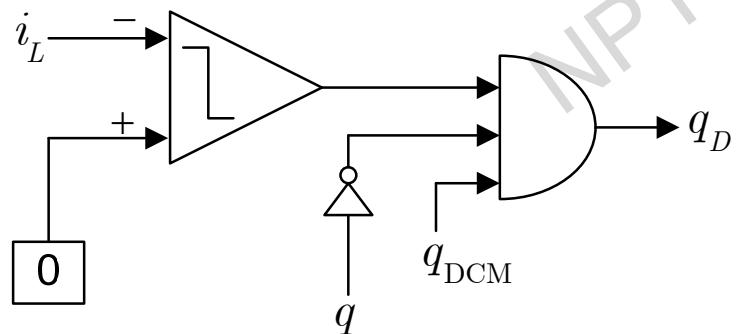
## Conventional Buck Converter – Implementation


$$\frac{di_L}{dt} = \begin{cases} \frac{1}{L} \times (v_x - i_L r_L - v_o) & \text{for } i_L > 0 \\ 0 & \text{for } i_L \leq 0 \end{cases}$$



DCM Enable Active high

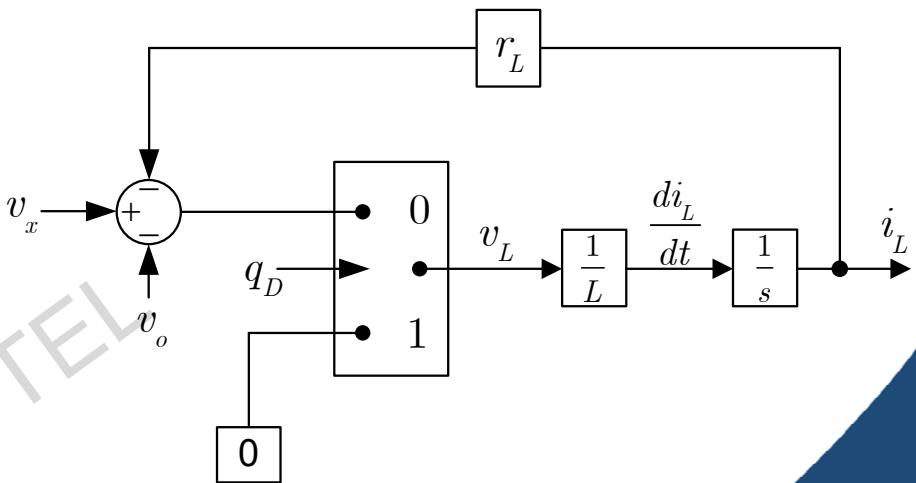
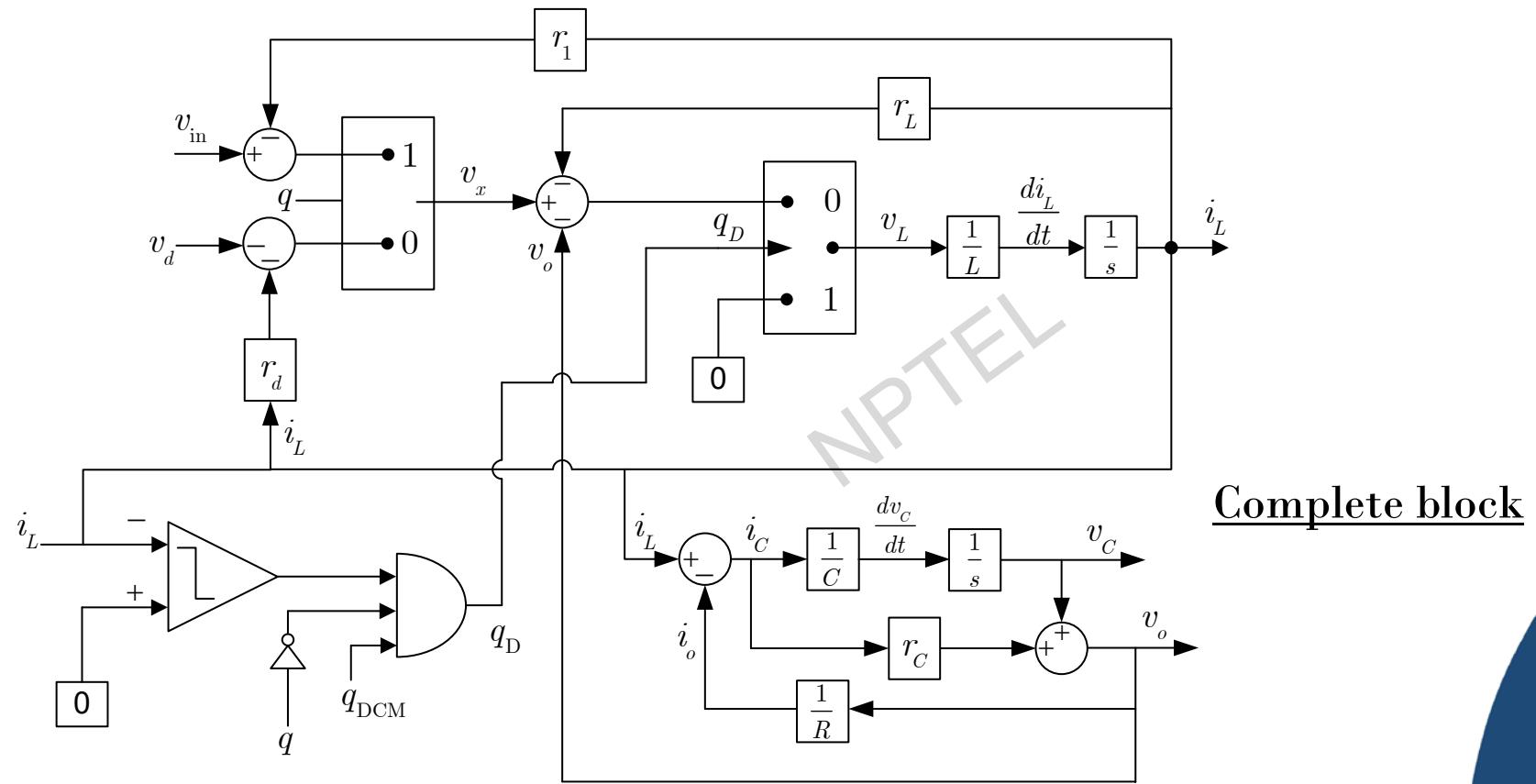
## Conventional Buck Converter – Implementation




## Model Generalization

- The previous block can be used for synchronous buck by setting

$$q_{DCM} = 0$$

$$r_d = r_2$$

$$v_d = 0$$


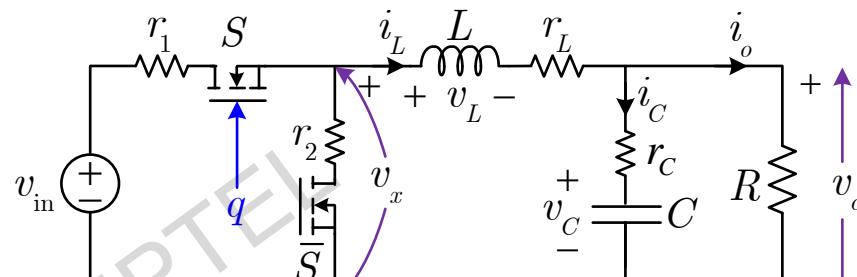


- For Constant current load,

$i_o \rightarrow$  Can be directly used as a load current
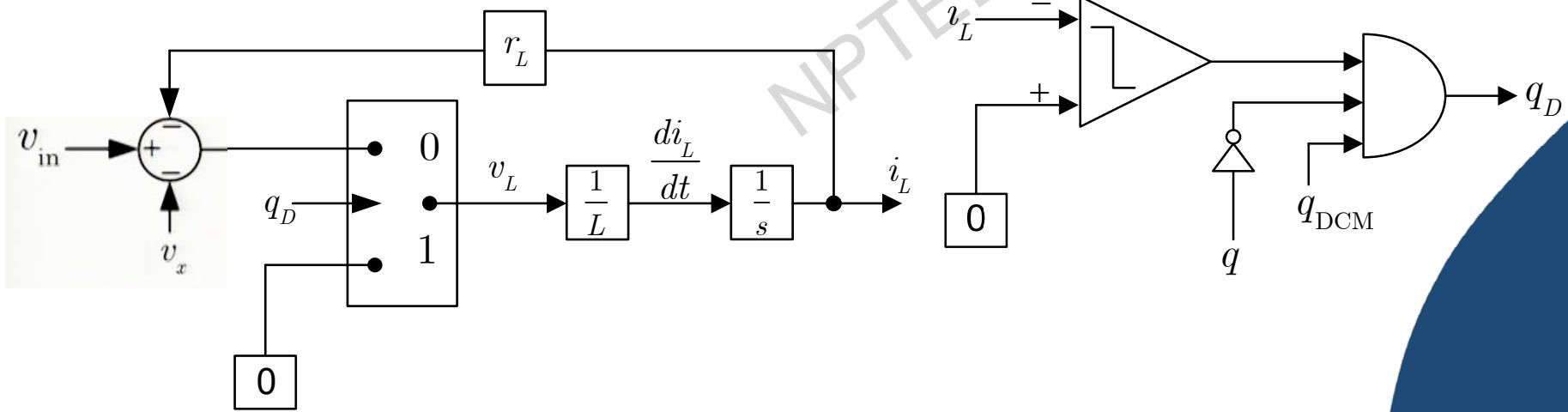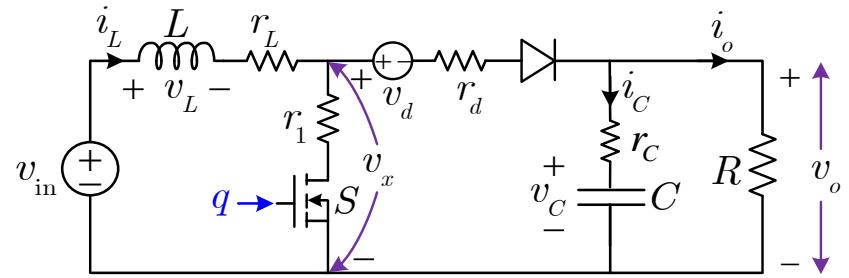
## Generic Form of a Boost Converter

$$\frac{di_L}{dt} = \begin{cases} \frac{1}{L} \times (v_{\text{in}} - i_L r_L - v_x) & \text{for } i_L > 0 \\ 0 & \text{for } i_L \leq 0 \end{cases}$$




## Boost Converter Implementation


$$\frac{dv_C}{dt} = \frac{1}{C} \times [(1 - q) \times i_L - i_o] = \frac{1}{C} \times i_C$$

$$i_C = [(1 - q) \times i_L] - i_o$$


$$v_o = (i_C \times r_C) + v_C$$

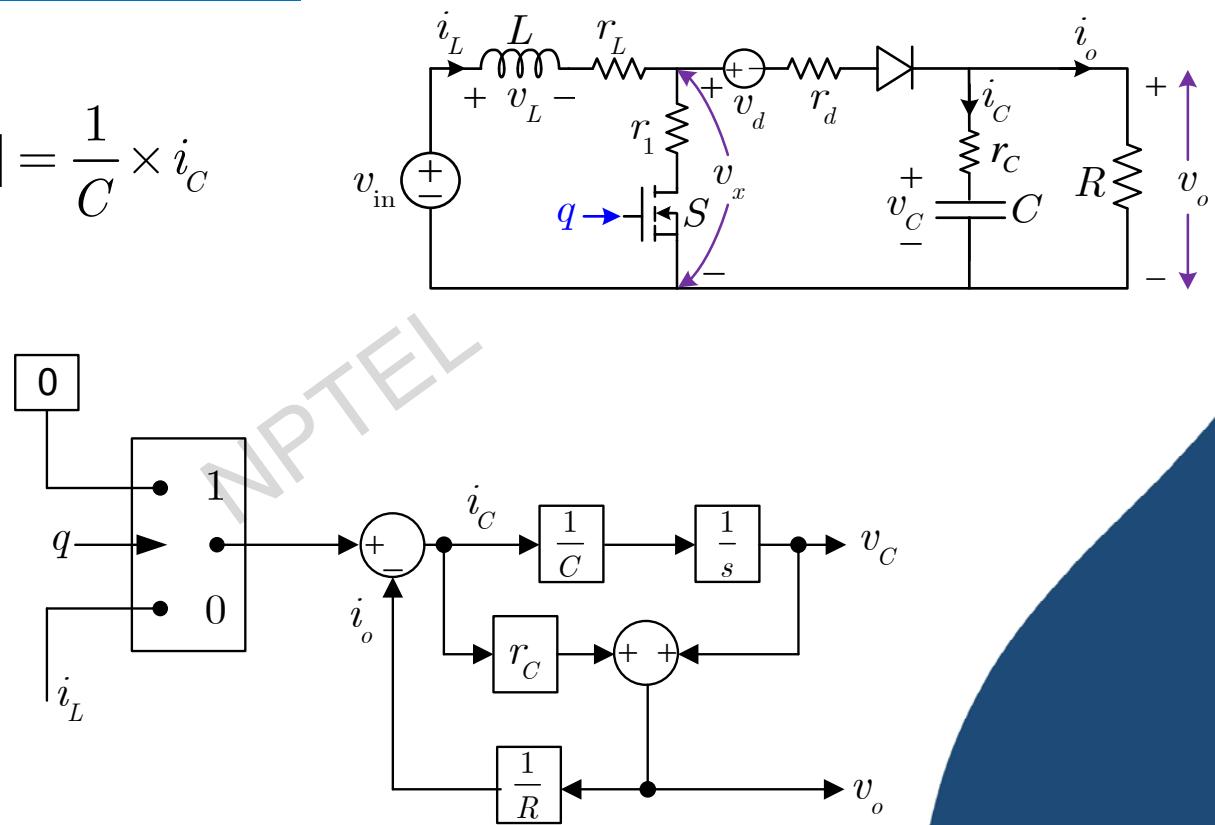

## Boost Converter Implementation

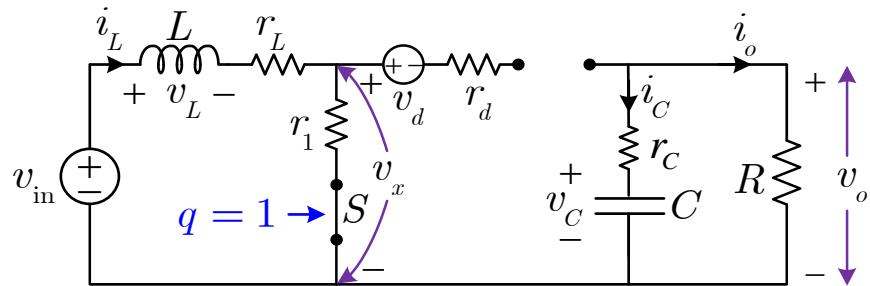


$$v_x = i_L r_1$$

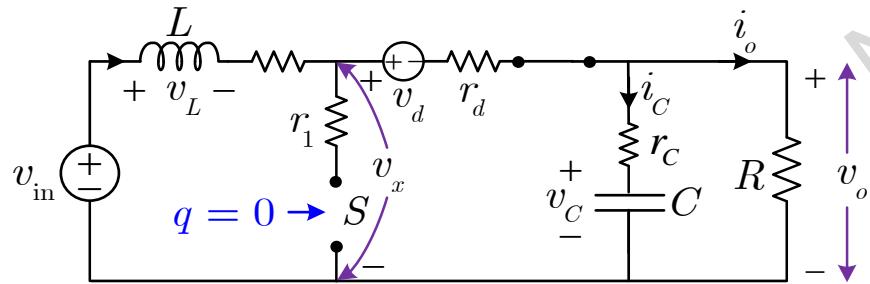

$$v_x = (v_d + i_L r_d + v_o)$$
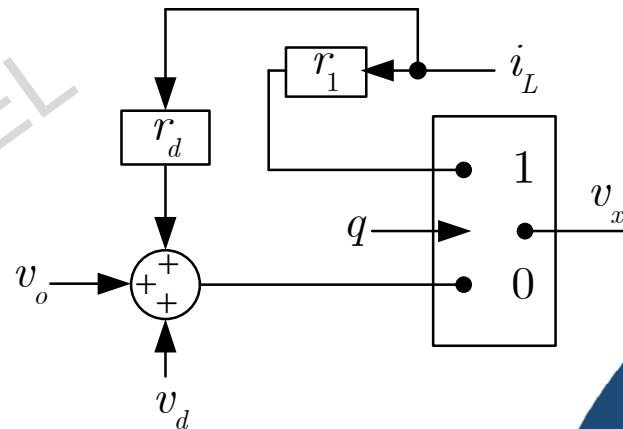
$$v_x = q(i_L r_1) + (1 - q)(v_d + i_L r_d + v_o)$$



# Summary

- Model development for simulation – versatile for reconfigurations
- MATLAB Simulink sufficient – no specialized toolbox needed
- Sync MATLAB code and Simulink – design oriented simulation
- Plug-and-play with modular configurations
- MATLAB demonstration to be shown



**THANK  
YOU !**



NPTEL ONLINE CERTIFICATION COURSES

# CONTROL AND TUNING METHODS IN SMPCs

Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR


**Module 01: Switched Mode Power Converters and Simulation**

**Lecture 05: Demonstration of MATLAB Simulation**


# Concepts Covered

- Introduction to MATLAB simulation
- Introduction to source, sink, dynamics, and ALU operations
- Development of Simulink models for various SMPCs
- Syncing with MATLAB coding and Simulink
- Data processing, data plotting, figure exporting – case studies


## Series RLC Circuit – Implementation

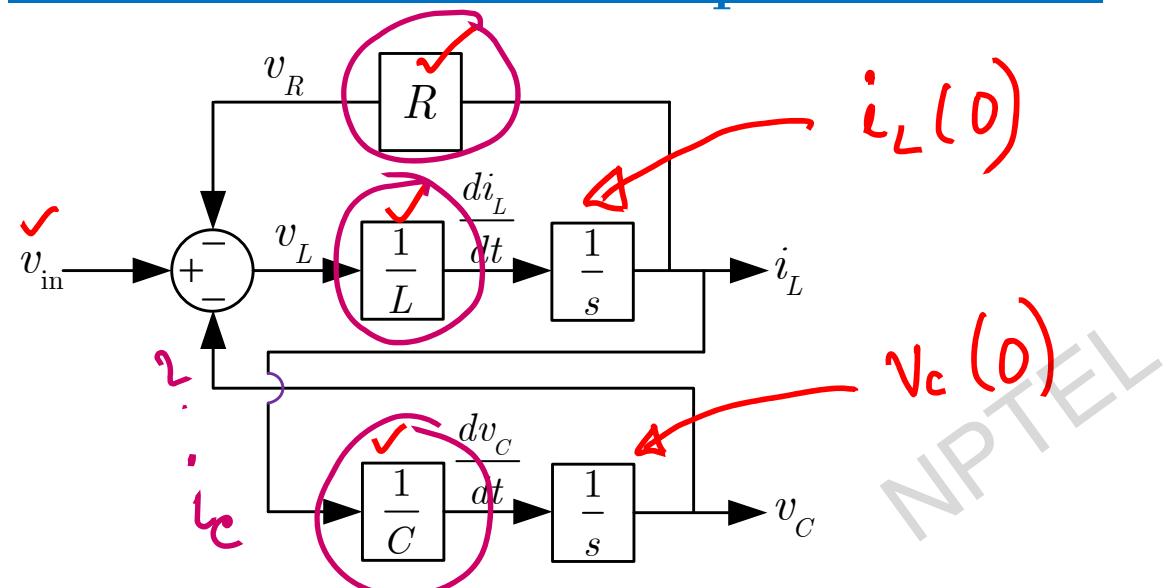

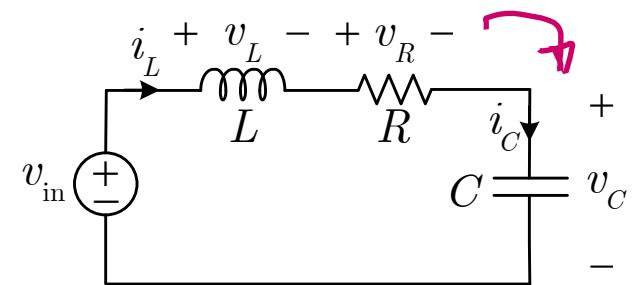- Select parameter symbols while building Simulink models
- Use a separate script (.m) file; define parameter notation, use consistent parameter symbols and specify parameter values



## Series RLC Circuit – Implementation

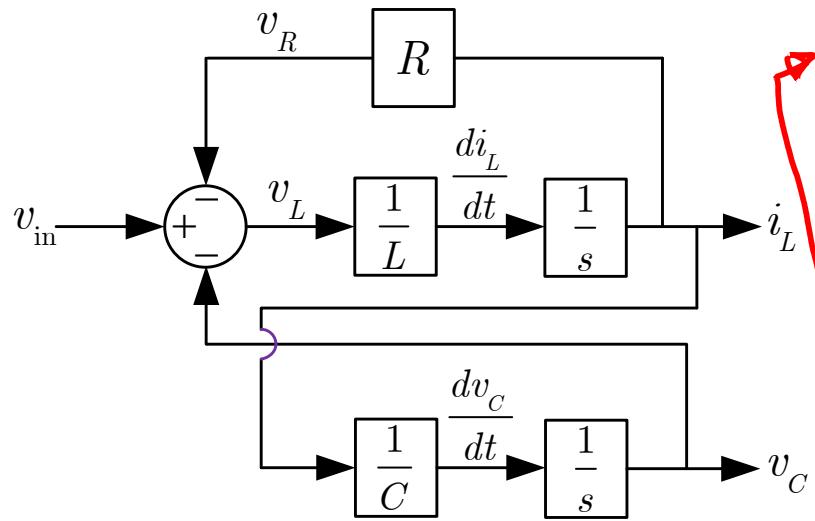



```
L=2e-6; % Inductor in Henry  
C=100e-6; % Capacitor in Farad  
R=1; % Resistance in Ohm  
I_L_int=0; % Initial condition of inductor current  
V_c_int=0; % Initial condition of capacitor voltage
```

**series\_RLC\_parameter.m**


$$= 2 \times 10^{-6} \text{ H}$$

$$= 2e - 6 \text{ H}$$

## Series RLC Circuit – Implementation

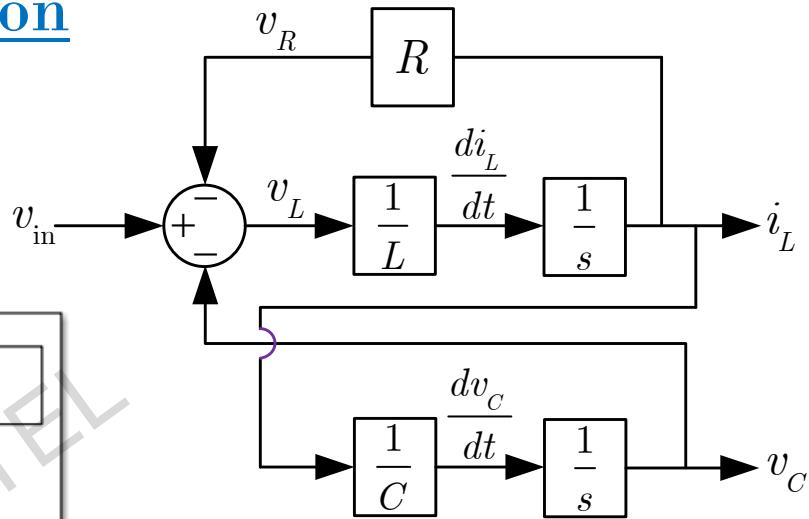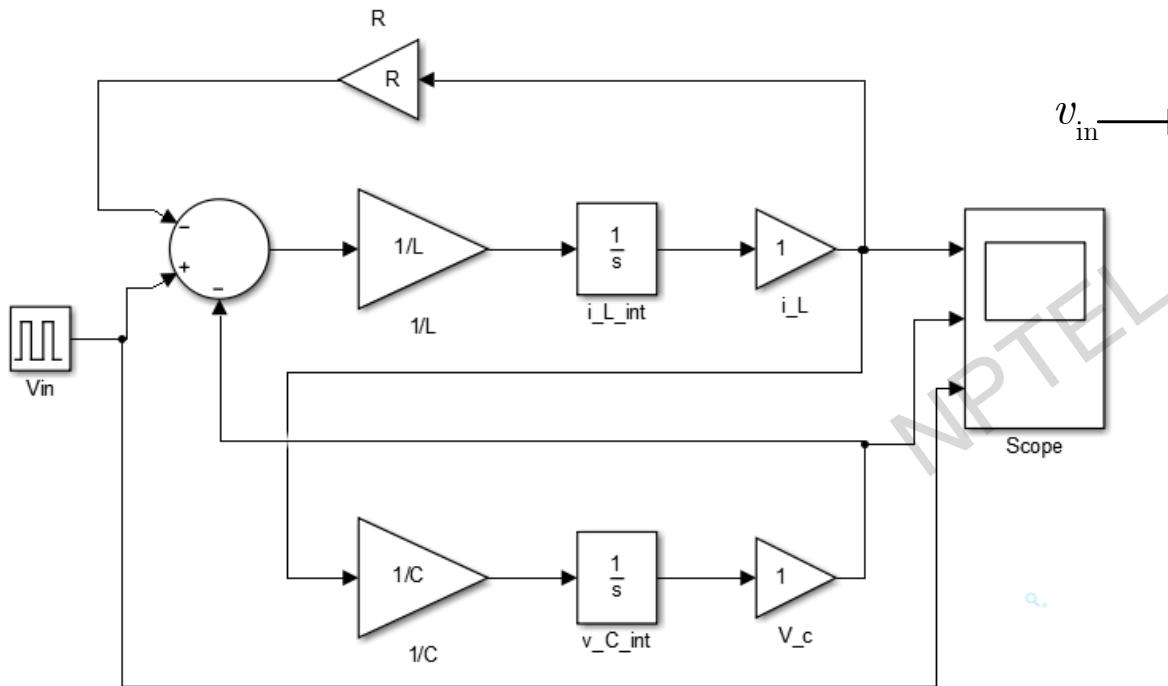


# Data Processing and Plotting


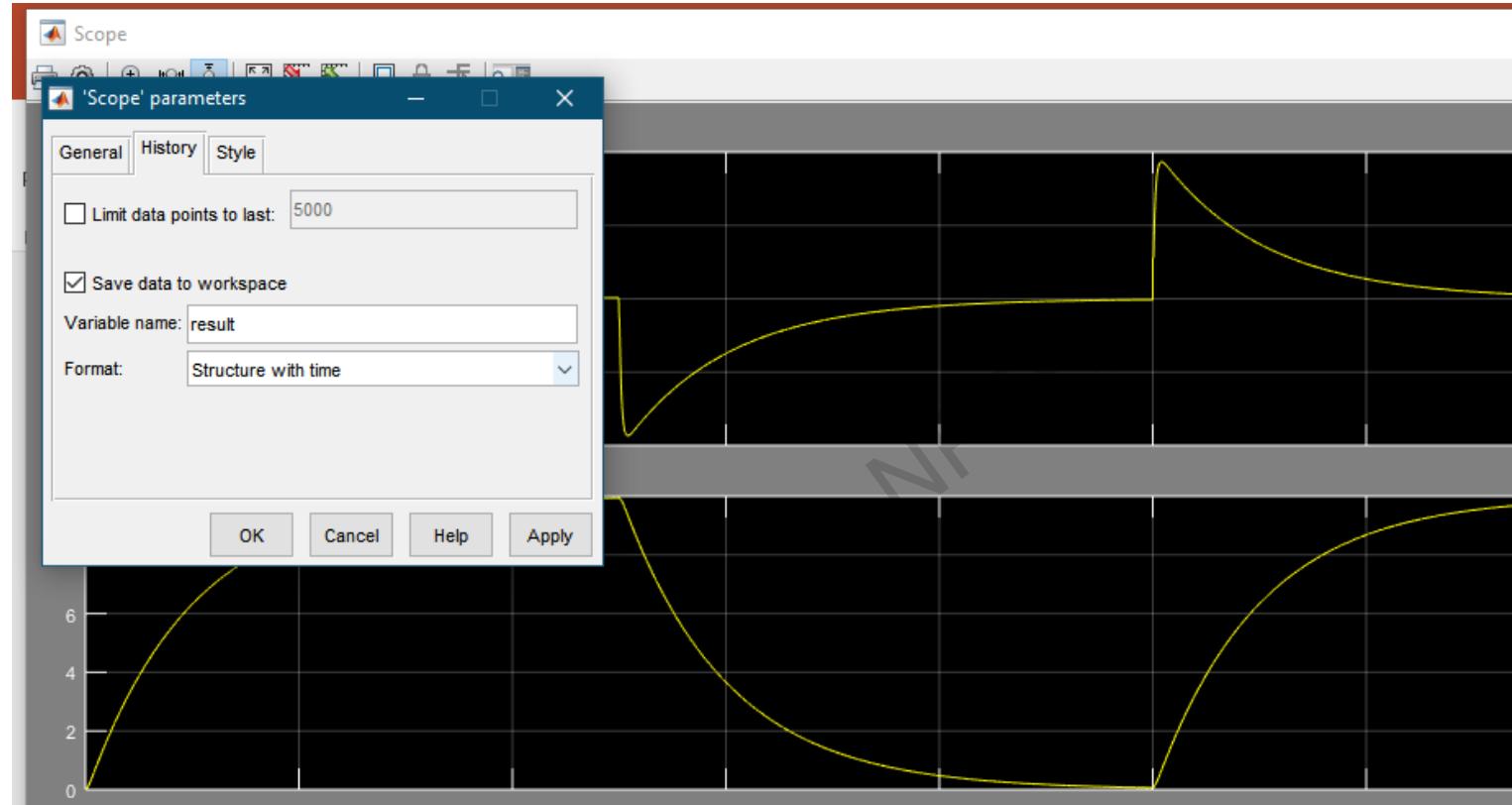

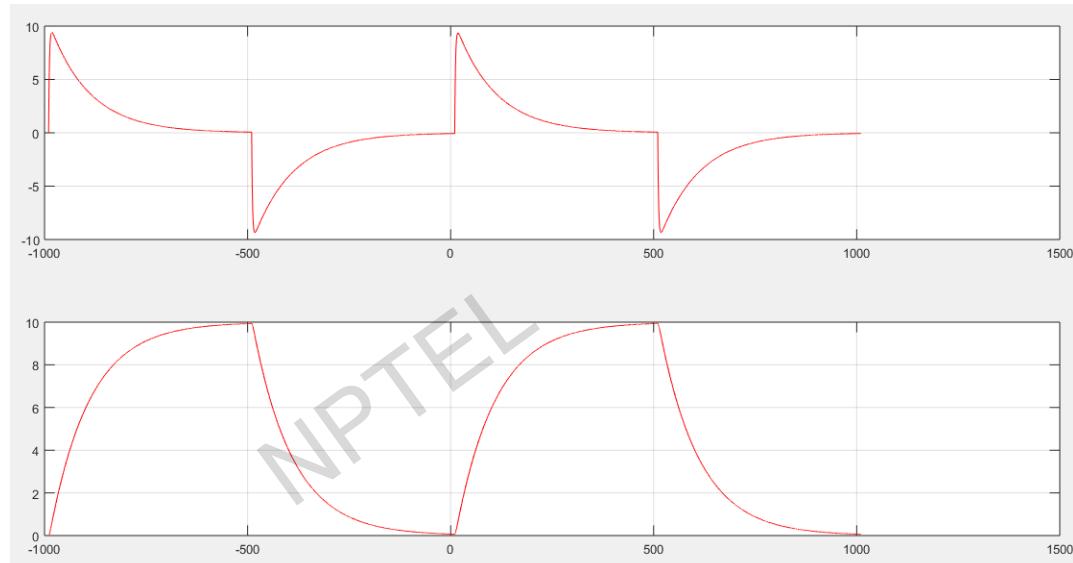
## Data Processing and Plotting

```
t=result.time;  
i_L=result.signals(1).values;  
v_o=result.signals(2).values;  
Vin=result.signals(3).values;  
  
subplot(2,1,1)  
plot(t,i_L,'r')  
hold on;  
grid;  
  
subplot(2,1,2)  
plot(t,v_o,'r')  
hold on;  
grid;
```




## Parallel RLC Circuit – Implementation

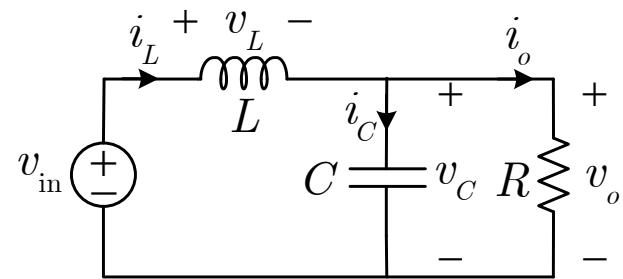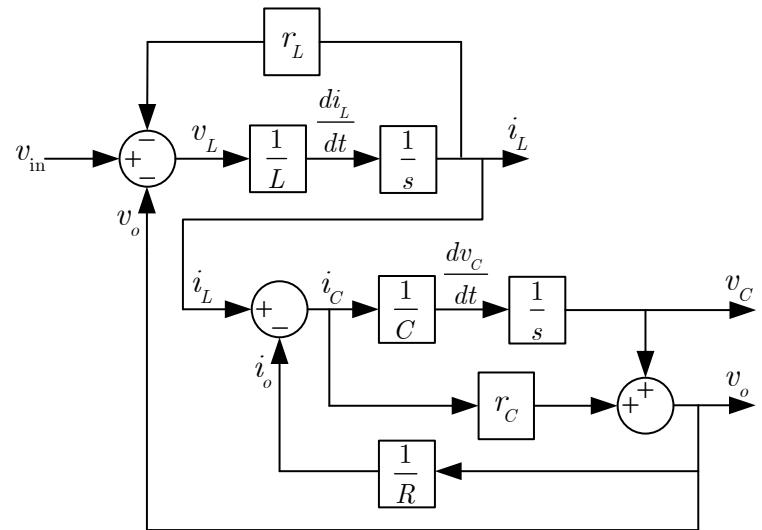

- Select parameter symbols while building Simulink models
- Use a separate script (.m) file; define parameter notation, use consistent parameter symbols and specify parameter values




## Parallel RLC Circuit with Parasitic

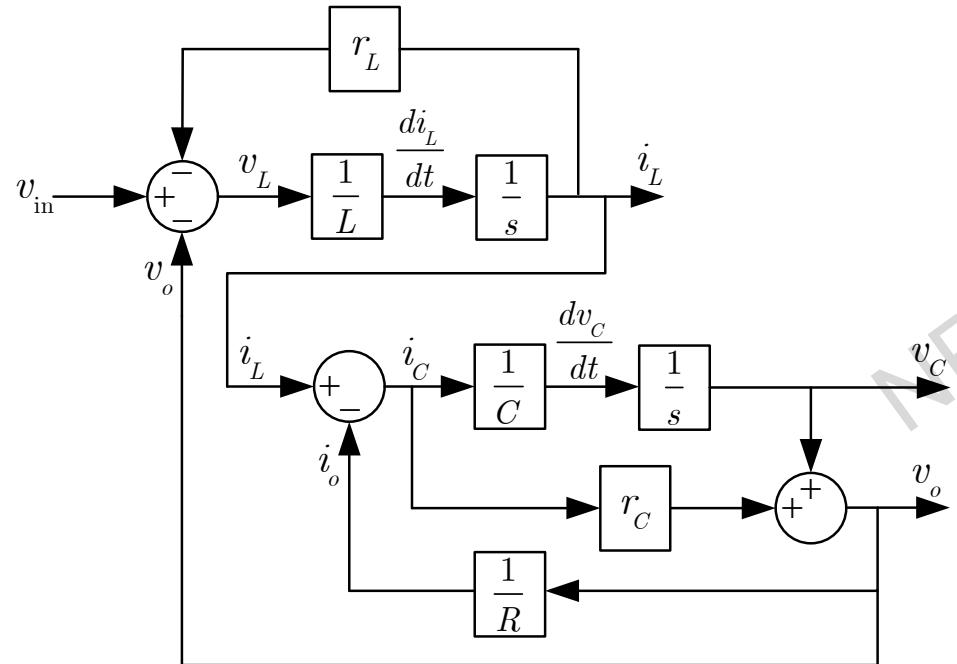



$L=2e-6;$   
 $C=100e-6;$   
 $R=0.5;$   
 $r_L=10e-3;$   
 $r_C=5e-3;$   
 $I_L\_int=0;$   
 $V_c\_int=0;$

**parallel\_RLC\_parameter.m**


## Parallel RLC Circuit – Implementation

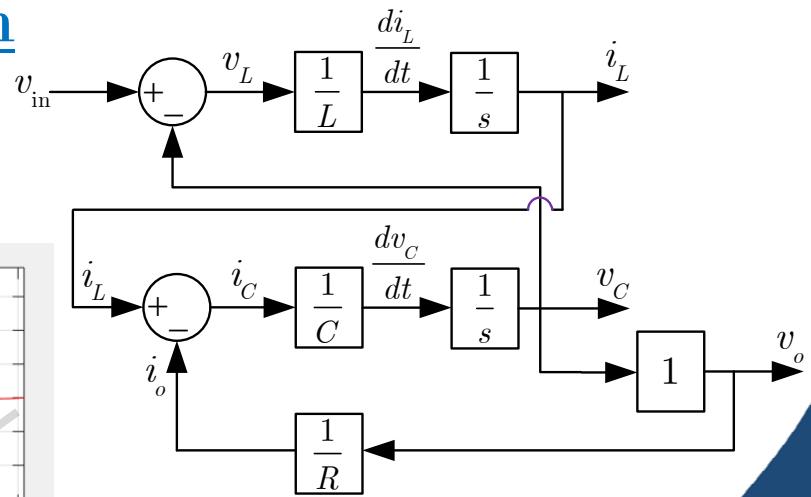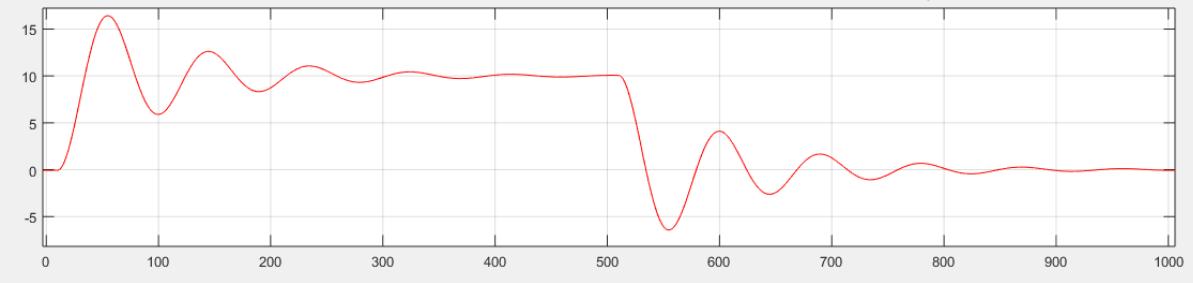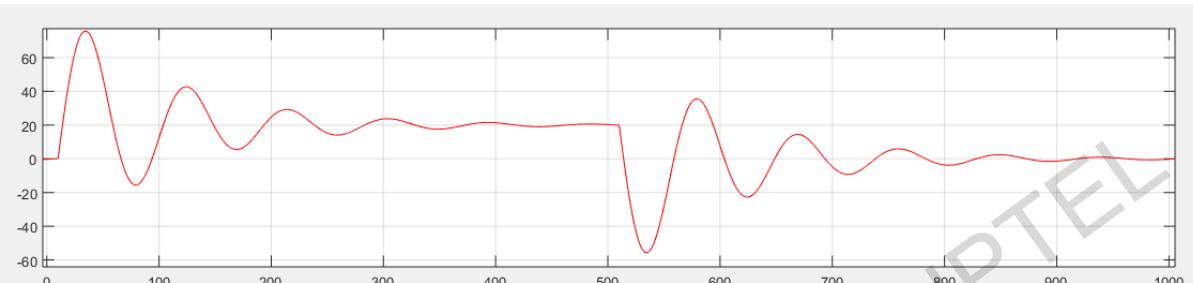


## Conventional Buck Converter

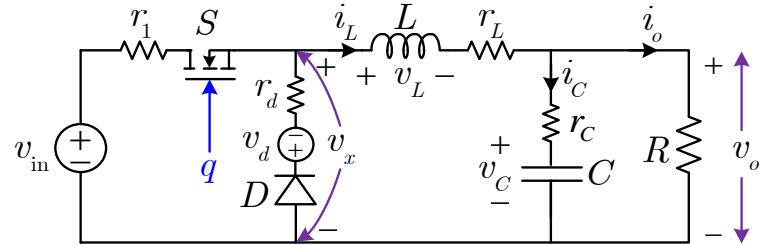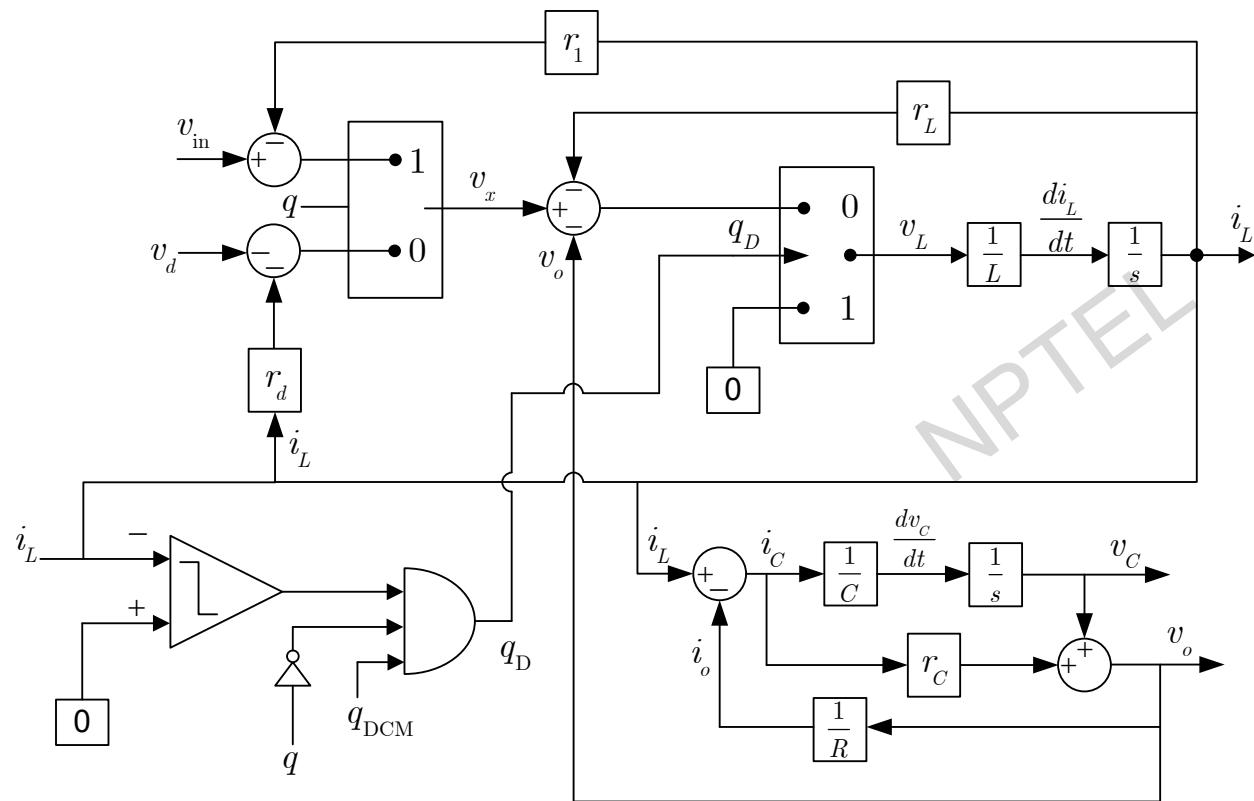
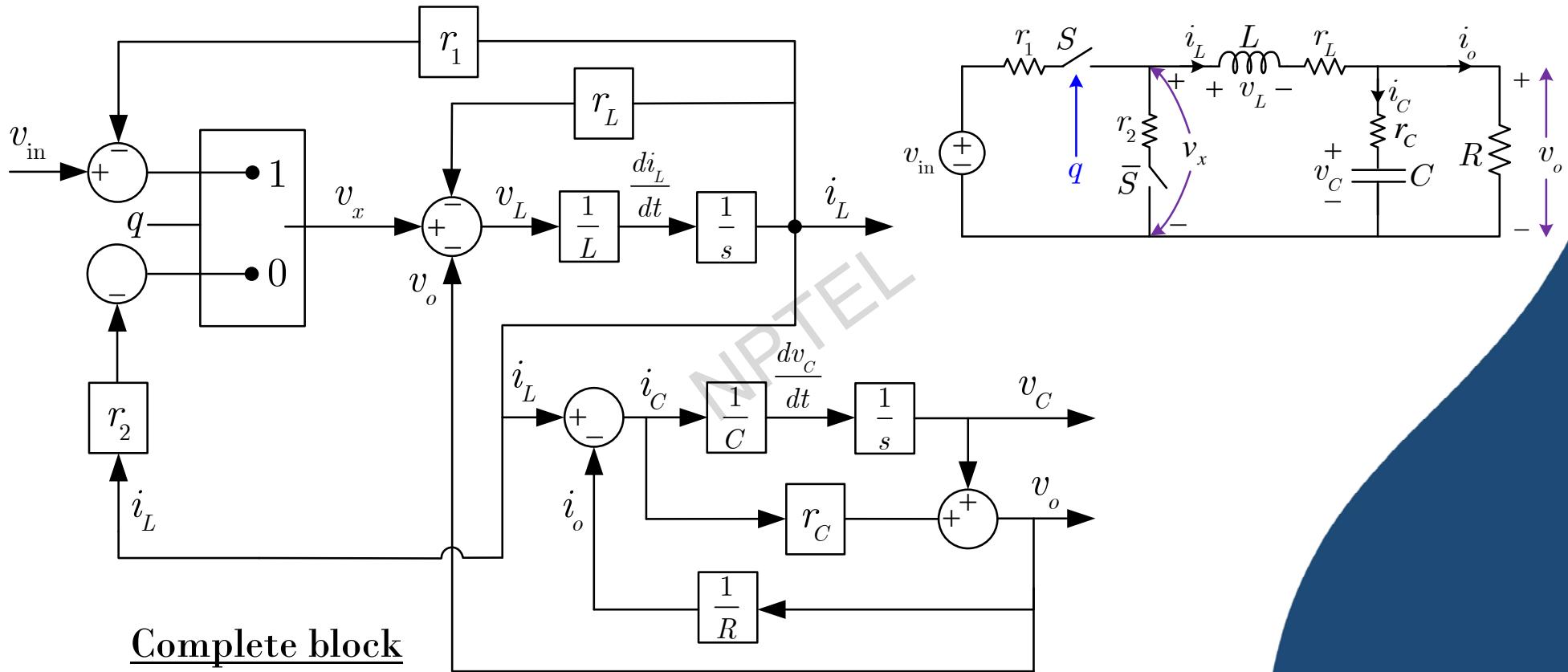
## Synchronous Buck Converter – Complete Implementation


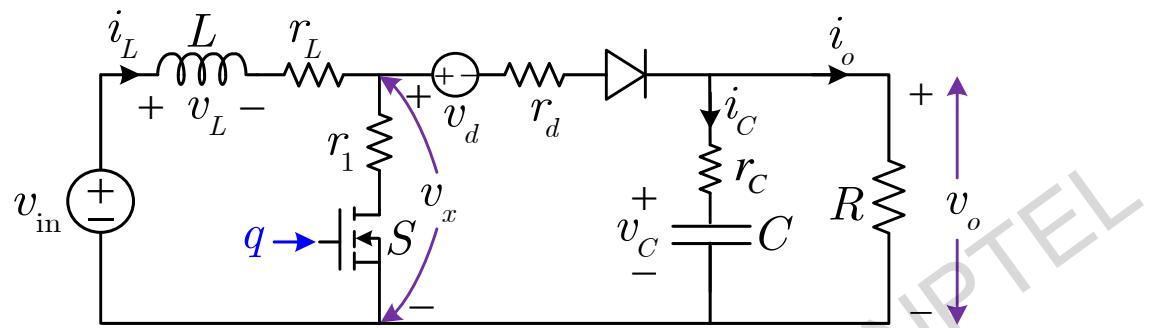
## Implementation of Boost Converter using Simulink



# Summary

- Model development for simulation – versatile for reconfigurations
- MATLAB Simulink sufficient – no specialized toolbox needed
- Sync MATLAB code and Simulink – design oriented simulation
- Plug-and-play with modular configurations
- MATLAB demonstration to be shown





NPTEL ONLINE CERTIFICATION COURSES

# CONTROL AND TUNING METHODS IN SMPCs



Dr. Santanu Kapat

Electrical Engineering Department, IIT KHARAGPUR

**Module 01: Switched Mode Power Converters and Simulation**


**Lecture 06: Demonstration of MATLAB Simulation (Contd ...)**

## Parallel RLC Circuit – Implementation

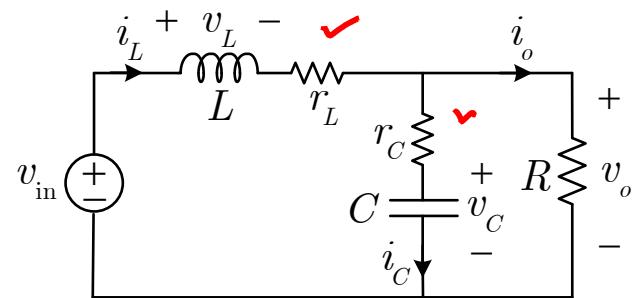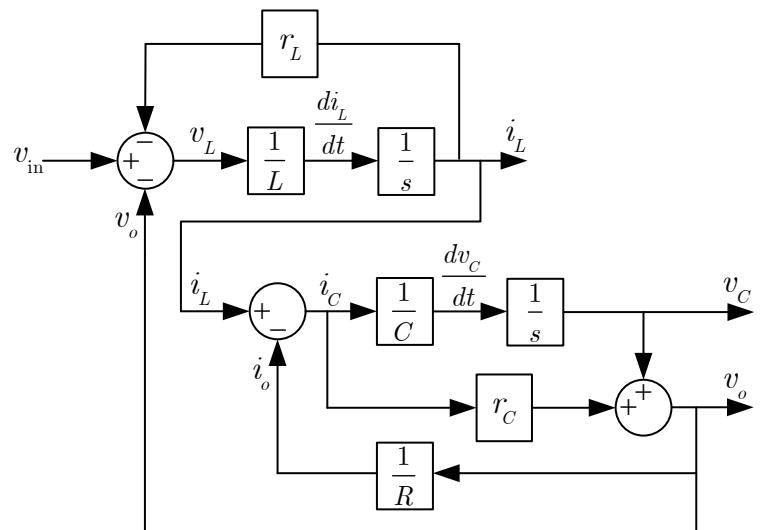

- Select parameter symbols while building Simulink models
- Use a separate script (.m) file; define parameter notation, use consistent parameter symbols and specify parameter values




## Parallel RLC Circuit with Parasitic

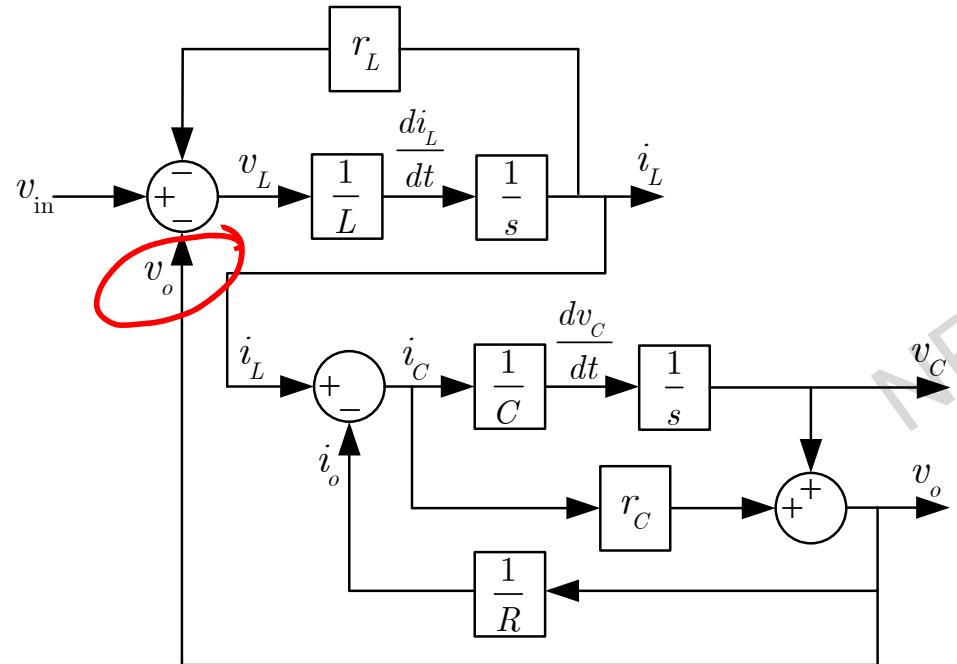



$L=2e-6;$  ✓  
 $C=100e-6;$  ✓  
 $R=0.5;$  ✓  
 $r_L=10e-3;$  ✓  
 $r_C=5e-3;$  ✓  
 $I_L\_int=0;$  ✓  
 $V_c\_int=0;$  ✓

parallel\_RLC\_parameter.m


## Parallel RLC Circuit – Implementation

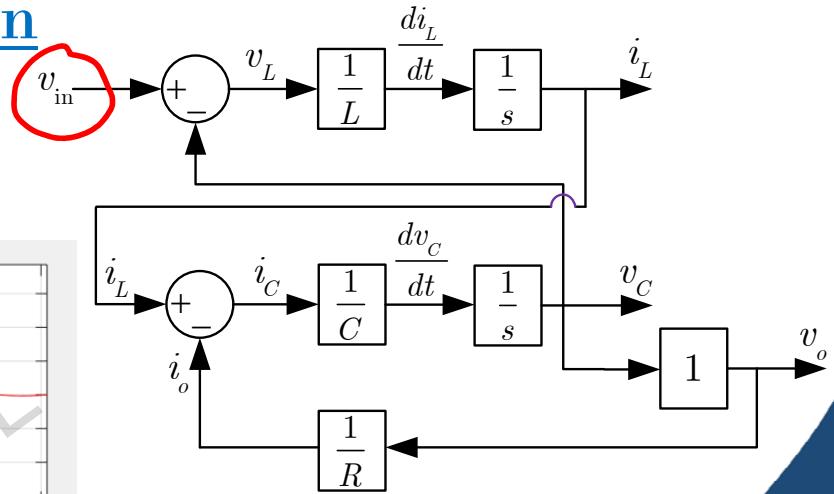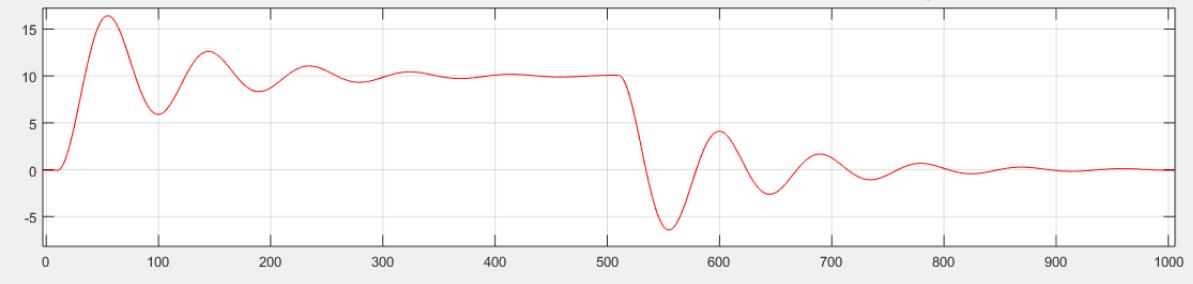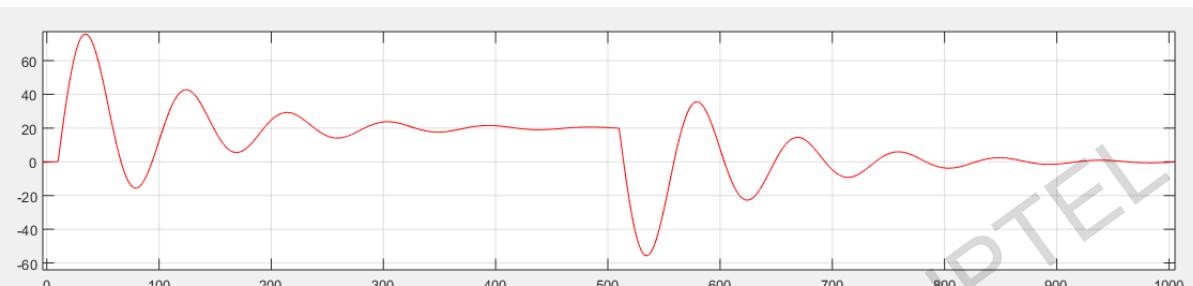


## Conventional Buck Converter

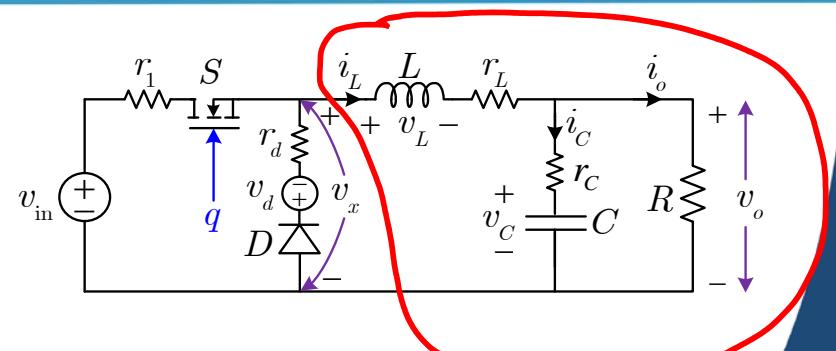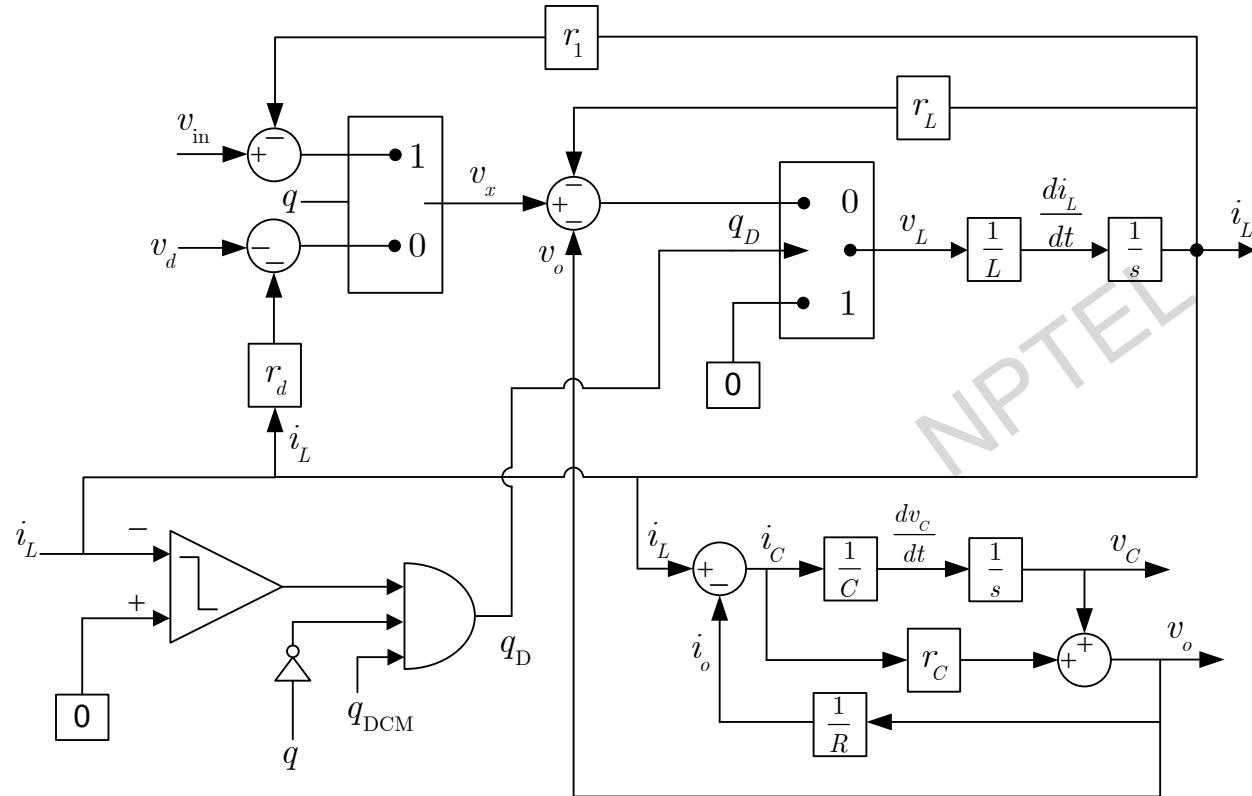
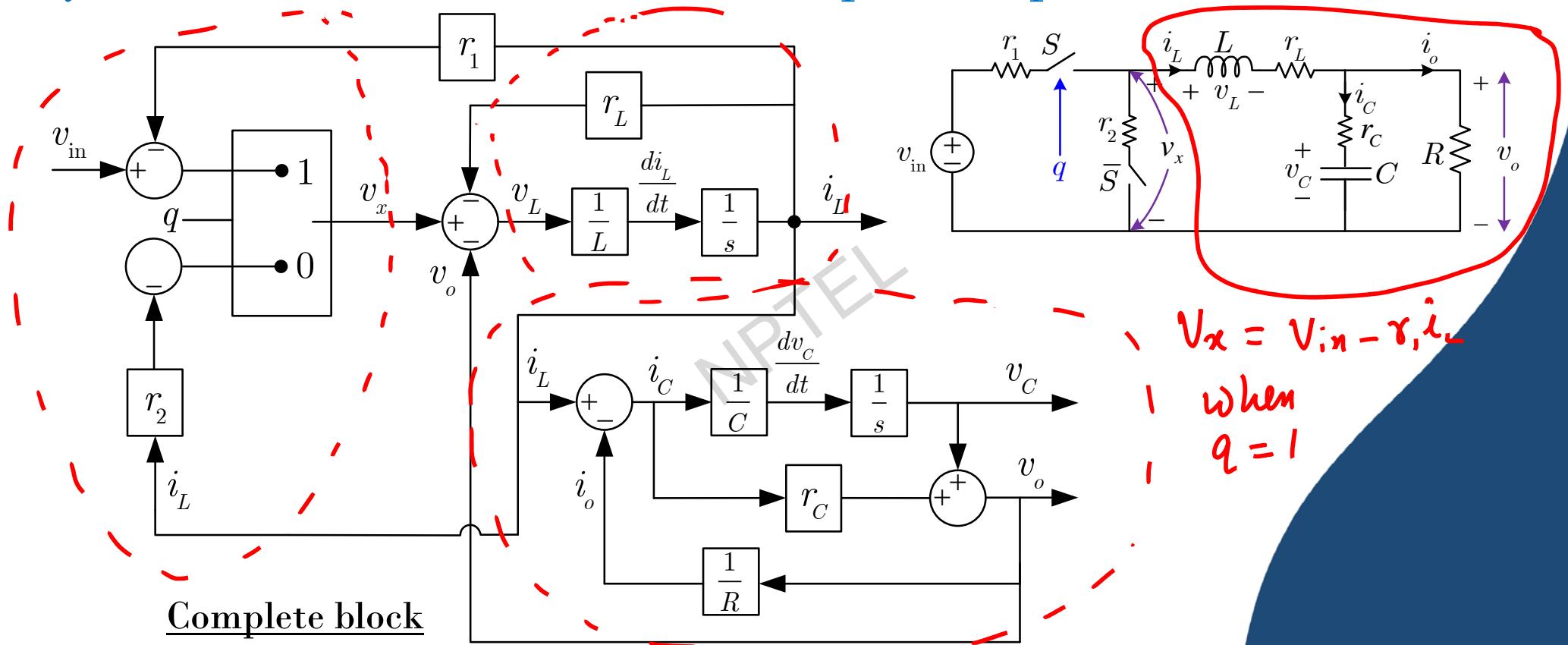
## Synchronous Buck Converter – Complete Implementation


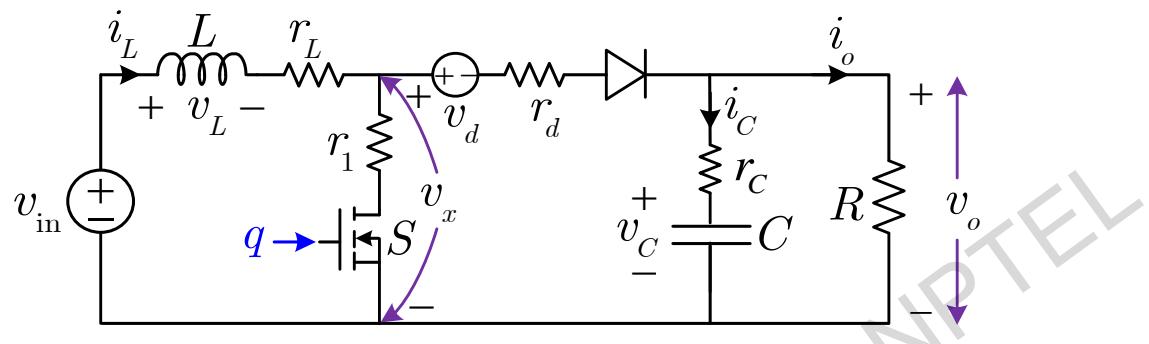
## Implementation of Boost Converter using Simulink



# Summary

- Model development for simulation – versatile for reconfigurations
- MATLAB Simulink sufficient – no specialized toolbox needed
- Sync MATLAB code and Simulink – design oriented simulation
- Plug-and-play with modular configurations
- MATLAB demonstration to be shown

